

Microelectronic Circuits I (Midterm)

date: 2008/11/13 (Thur)

time: 15:30 ~ 17:20

1. (20%) A p^+-n diode is one in which the doping concentration in the p region is much greater than that in the n region. In such a diode, the forward current is mostly due to hole injection across the junction. Show that

$$I \approx I_p = Aq n_i^2 \times \frac{D_p}{L_p N_D} (e^{\frac{V}{V_T}} - 1)$$

For the specific case in which $N_D = 3 \times 10^{16} / \text{cm}^3$, $D_p = 10 \text{ cm}^2 / \text{s}$, $\tau_p = 0.05 \mu\text{s}$,

and $A = 10^4 \mu\text{m}^2$, find I_s and the voltage V obtained when $I = 0.2 \text{ mA}$.

Assume operation at 300K where $n_i = 1.5 \times 10^{10} / \text{cm}^3$. Also, calculate the excess minority-carrier charge and the value of the diffusion capacitance at $I = 0.2 \text{ mA}$.

2. (20 pts) An ideal differentiator is implemented as Fig (a). Note that $R_F C_1 = 1 \mu\text{s}$.
- (1) With such input waveform, please draw the output waveform. Please label all of the voltage and time information in your waveform. Note that transition time means that the time that it needs to take for the input voltage to change from 0V to 1V, 1V to 2V and 2V to 0V. Also, assume the input voltage stays at 0V, 1V and 2V for a time much longer than $1 \mu\text{s}$. (6 pts)
 - (2) Now, the circuit in Fig (a) is modified as that in Fig (b), please repeat part (1). (2 pts)
 - (3) The slew rate of the op amp is only $0.5 \text{ V}/\mu\text{s}$, repeat part (1). You don't need to consider the 50mV voltage in (b). (5 pts)
 - (4) The capacitor C_1 is not ideal such that it has a series resistor R_S (as Fig (c)), please repeat part (1). Here, $R_S C_1 = 0.1 \mu\text{s}$. (7 pts)

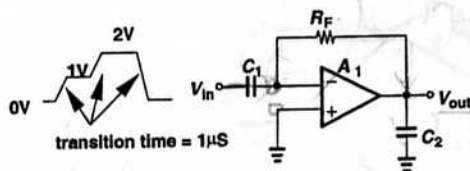


Fig (a)

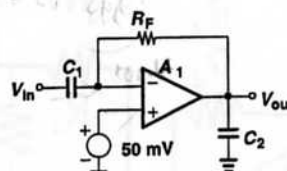


Fig (b)

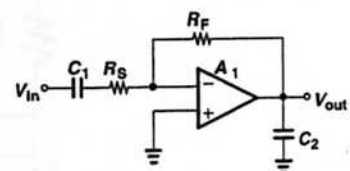


Fig (c)

$$\left| \frac{V_o}{V_i} \right| = -j\omega \cdot 10^{-6}$$

$$V_{in} + C = 0$$

$$V_{out} = -C_1 R_F V_{in}$$

3. (20%) For the circuit in Fig (d), the parameters are given as $V_S = 3\text{ V}$, $v_s = 0.1 \times \cos(100t)\text{ V}$, $R_1 = 2\text{ k}\Omega$, $R_2 = 1\text{ k}\Omega$, $R_3 = 2\text{ k}\Omega$, $n = 1$ (for all diodes), and the capacitors C_1 and C_2 are sufficiently large.

(1) For $I_0 = 0\text{ mA}$, find the total voltage $v_A(t)$ and $v_B(t)$. (14%)

(2) For $I_0 = 1\text{ mA}$, find the total voltage $v_A(t)$ and $v_B(t)$. (6%)

[Hint: Please use constant-voltage-drop model with $V_D = 0.7\text{ V}$ for DC analysis]

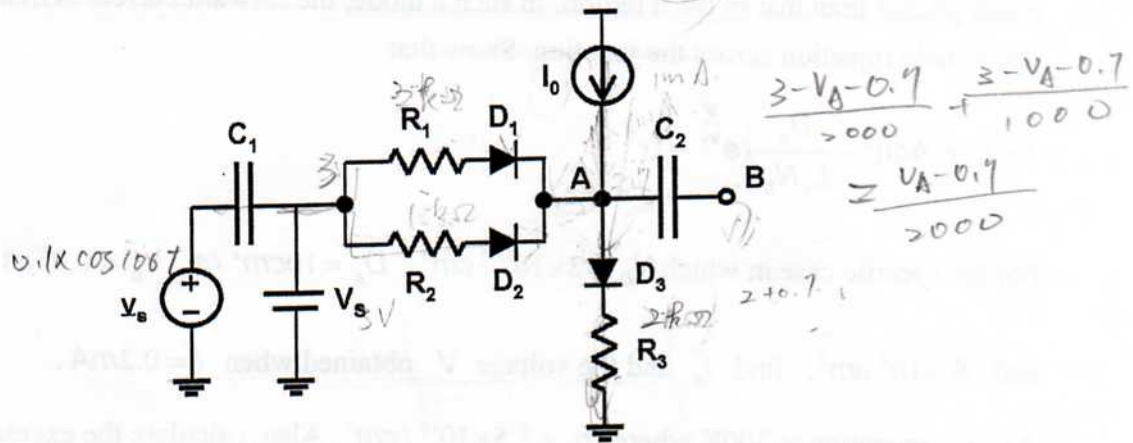


Fig (d)

4. (20%) The instrument amplifier, shown as Fig (e), is widely used in various applications especially in the interface circuit of sensors. Please answer the following questions and derive the expression.

(1) Please derive the differential gain of the instrument amplifier. (8%)

(2) Please write the input resistance and the output resistance of the instrument amplifier. (4%)

(3) If we want to measure the difference of ΔR shown as Fig (f), can we use the instrument amplifier to be its interface circuit? If so, please draw the connection and derive the output voltage, v_O , of the amplifier. (8%)

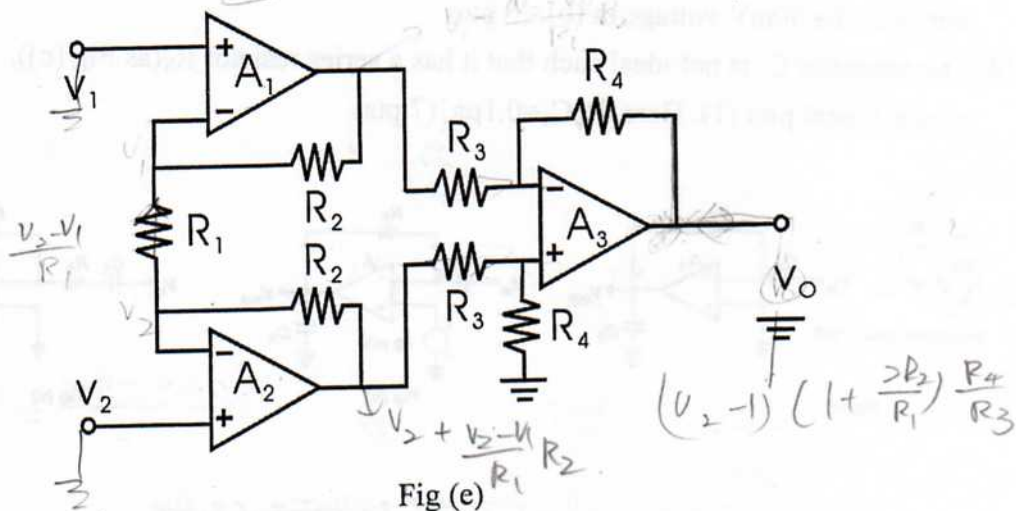


Fig (e)



- [illegible]