


991 Microelectronic Circuits I (Midterm)

date: 2010/11/11 (Thur)


time: 15:30 ~ 17:20

ps. 試題可帶回，可使用計算機。

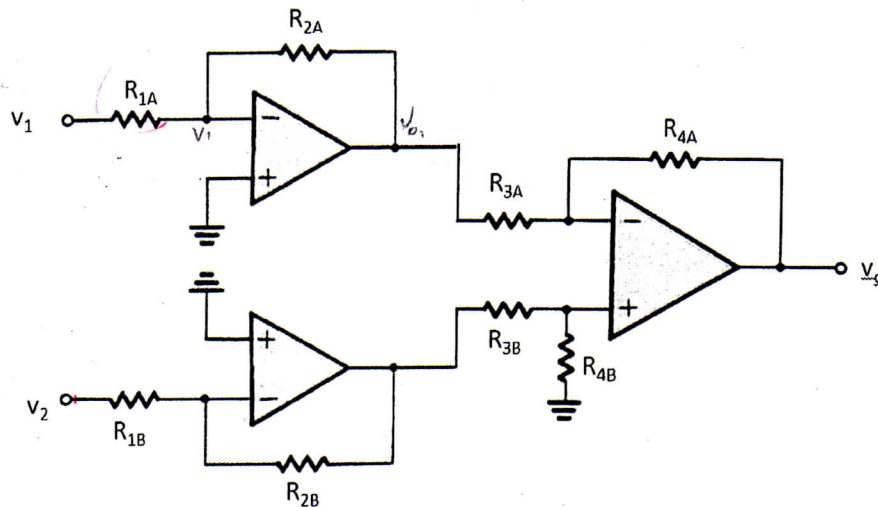1. Given that $R_{1A} = R_{1B} = 10\text{ K}\Omega$, $R_{2A} = R_{2B} = 50\text{ K}\Omega$, $R_{3A} = R_{3B} = 5\text{ K}\Omega$, $R_{4A} = R_{4B} = 15\text{ K}\Omega$.
 - (1) Assume the opamps are ideal, find the common-mode gain and differential-mode gain of the circuit. [5%]
 - (2) Assume the opamps have a finite open-loop gain of A_0 , find the common-mode gain and differential-mode gain of the circuit. [10%]
 - (3) If R_{1A} is $10.5\text{ K}\Omega$, repeat (1). [5%]
 - (4) If R_{3A} is $5.5\text{ K}\Omega$, repeat (1). [5%]



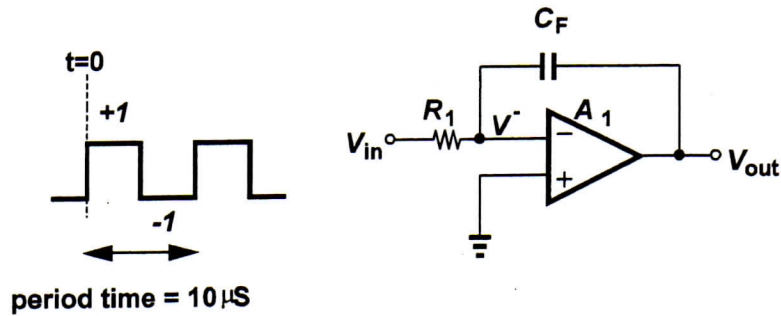2. An integrator is implemented as follows. Note that $R_1 = 1\text{ K}$ and $C_F = 1\text{ nF}$. The maximum/minimum output of the op amp are $12\text{ V}/-12\text{ V}$, respectively. Assume $V_{\text{out}}(t = 0) = 0$.
 - (1) With such input waveform, please draw the output V_{out} and V waveform. Please label all of the transition voltage levels. [6%]
 - (2) Now, the input voltage is scaled by a factor of 2 so that its high and low level are $2/-2\text{ V}$ respectively. Repeat part (1). [6%]
 - (3) For the rest of questions, let's assume the op amp has finite gain, A_1 . Please derive its transfer function. $V_{\text{out}}(s) / V_{\text{in}}(s)$. You can still assume the bandwidth of the op amp is infinite. [6%]
 - (4) If $A_1 = 10$, repeat part (1). [7%]




3. A p^+n junction is one in which the doping concentration in the p region is much greater than in the n region. In such a junction, the forward current is mostly due

to hole injection across the junction. Show that $I \sim I_p = Aq n_i^2 \frac{D_p}{L_p N_D} (e^{\frac{V}{V_T}} - 1)$. For the specific case in which $N_D = 10^{16}/\text{cm}^3$, $D_p = 10 \text{ cm}^2/\text{s}$, $L_p = 10 \mu\text{m}$, and $A = 10^4 \mu\text{m}^2$, find I_s and the voltage V obtained when $I = 0.5 \text{ mA}$. Assume operation at 300K where $n_i = 1.5 \times 10^{10}/\text{cm}^3$. [10%]

4. In Figure shown below, the Zener diode is specified to have $V_Z = 8\text{V}$ at $I_Z = 10 \text{ mA}$, $r_Z = 10 \Omega$, and $I_{ZK} = 0.1 \text{ mA}$. The supply voltage (V_S) is 12 V , but can vary by $\pm 1 \text{ V}$. $R_S = 200 \Omega$.

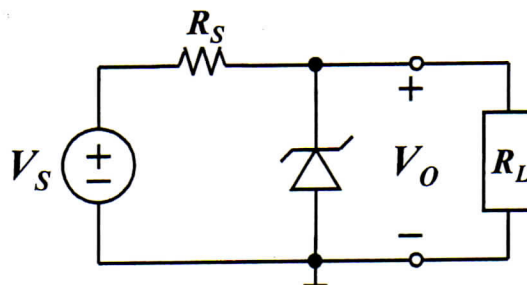- (1) If no load ($R_L = \text{infinite}$) and V_S is at the nominal value (12 V), find V_O . [4%]
- (2) Find the line regulation of this circuit. [4%]
- (3) Find the load regulation of this circuit. [4%]
- (4) If $R_L = 4 \text{ K}\Omega$ and $V_S = 12 \text{ V}$, find V_O . [4%]
- (5) What is the requirement on the value of R_L , for the circuit to operate properly across the possible range of V_S ? [4%]



5. The rectifier is one of the most important applications for diode circuits. Using the constant-voltage-drop (V_D) diode model, please answer the following questions:

- (1) Please draw the bridge rectifier circuit. [2%]
- (2) If the input waveform (after transformer) is shown as Fig. 1, please draw the output waveform. [2%]
- (3) Please find the peak-inverse-voltage and find the peak diode current of diodes in the bridge rectifier. [4%]
- (4) Assume $V_D \approx 0.7\text{ V}$, and the load resistance $R = 100\Omega$. If the input sinusoid with $V_P = 12\text{ V}$, please calculate the quantities of (3). [4%]
- (5) If the input waveform fluctuates by as much as 10%, please find the required PIV of the diodes (Consider the safety factor 50%). [2%]

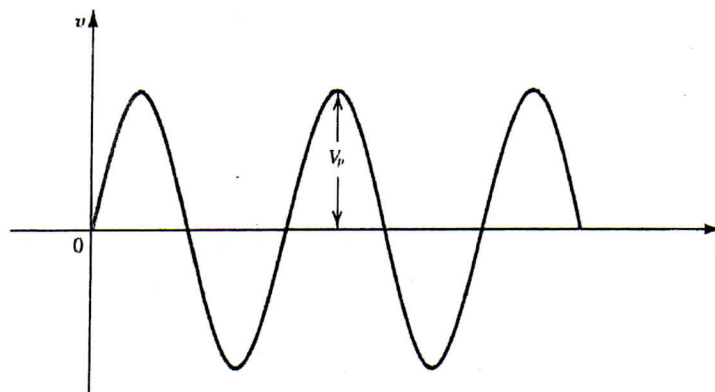


Figure 1

6. The Fig. 2 shows a diode rectifier circuit. Assume the constant-voltage-drop diode model and the input waveform is the same as Fig. 1. Please draw the output voltage waveform of C1 and C2. [6%]

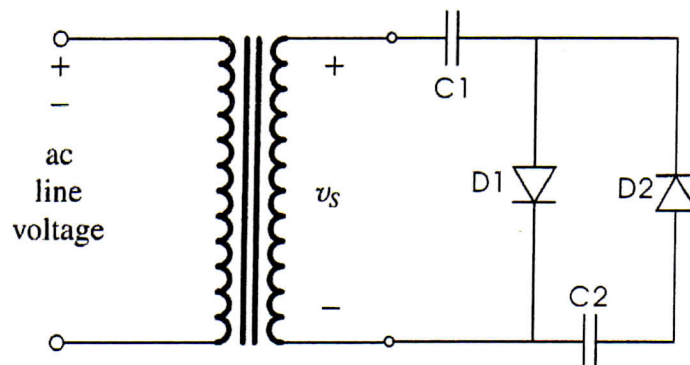


Figure 2