

Electromagnetics II Midterm Exam (10:10am-11:50am) 11/14/2005

註: 每題 20 分, 只計得分較高之 5 題, 合計滿分 100 分。

1. **Finding fields and power flow for a parallel-plate line for specified voltage along the line.** A parallel-plate transmission line is made up of perfect conductors of width $w = 0.1\text{ m}$ and lying in the planes $x = 0$ and $x = 0.01\text{ m}$. The medium between the conductors is a nonmagnetic ($\mu = \mu_0$), perfect dielectric. For a uniform plane wave propagating along the line, the voltage along the line is given by

$$V(z, t) = 10 \cos(3\pi \times 10^8 t - 2\pi z) \text{ V}$$

Neglecting fringing of fields, find: (a) the electric field intensity $E_x(z, t)$ of the wave; (b) the magnetic field intensity $H_y(z, t)$ of the wave; (c) the current $I(z, t)$ along the line; and (d) the power flow $P(z, t)$ down the line.

2. **Time-domain analysis of a transmission-line system using the bounce-diagram technique.** In the system shown in Fig.P2, the switch S is closed at $t = 0$. Assume $V_g(t)$ to be a direct voltage of 90 V and draw the voltage and current bounce diagrams. From these bounce diagrams, sketch: (a) the line voltage and line current versus t (up to $t = 7.25\text{ }\mu\text{s}$) at $z = 0$, $z = l$, and $z = l/2$; and (b) the line voltage and line current versus z for $t = 1.2\text{ }\mu\text{s}$ and $t = 3.5\text{ }\mu\text{s}$.

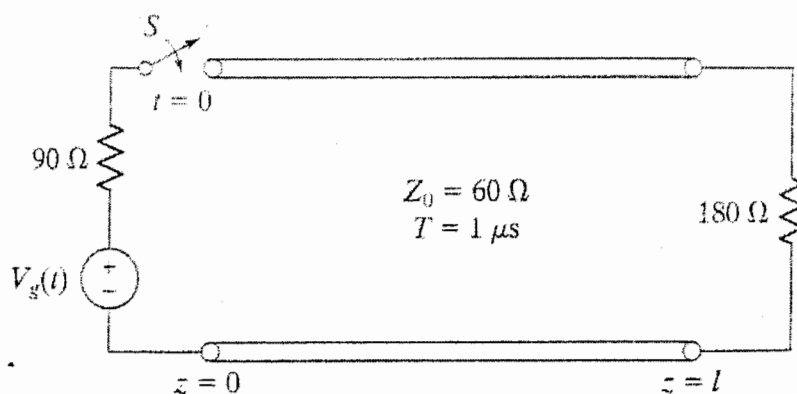


Figure P2

3. **A transmission-line system with inductive discontinuity.** In the system shown in Fig.P3, the switch S is closed at $t = 0$, with the lines uncharged and with zero current in the inductor. Obtain the solution for the line voltage versus time at $z = l+$.

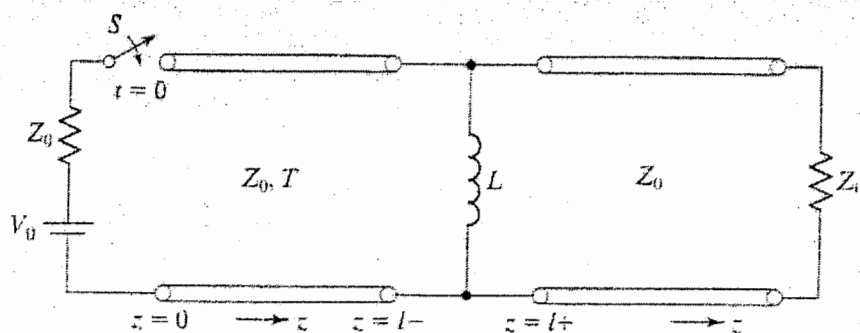


Figure P3

4. Fig. P4 shows a transmission line system driven by a switching gate. Transmission line 3 (Tx3) is a short stub between transmission line 1 (Tx1) and transmission line 2 (Tx2). A capacitive load C_L is terminated at the end of Tx2, and the end of Tx3 is open circuit. The per-unit-length coupling inductance and capacitance between Tx1 (or Tx2) and transmission line 4 (Tx4) are L_m and C_m , respectively. As shown in Fig. P4, the characteristic impedances of Tx1, Tx2 and Tx4 are all Z_0 . The characteristic impedance of Tx3 is Z_1 . The delay of Tx1, Tx2, Tx3, and Tx4 are $T/2$, $T/2$, $T/4$, and T , respectively. The propagation velocity of all transmission lines is V_p .
- Assume the initial voltage and current on the transmission line system is both zero, and switch S_1 and S_2 are opened. At $t = 0$, S_1 is closed. Please derive and sketch the voltage waveform $V_c(t)$ on the load C_L (point A) for $0 \leq t \leq 1.75T$. (The mutual coupling with Tx4 can be ignored here.)
 - The timing requirement for the voltage waveform $V_c(t)$ is $V_c(t) \geq V_{th}$ at $t \geq T + C_L Z_0$. Please design the minimum characteristic impedance of the short stub Z_1 to satisfy this timing requirement. It is assumed $C_L Z_0 \ll T/4$.

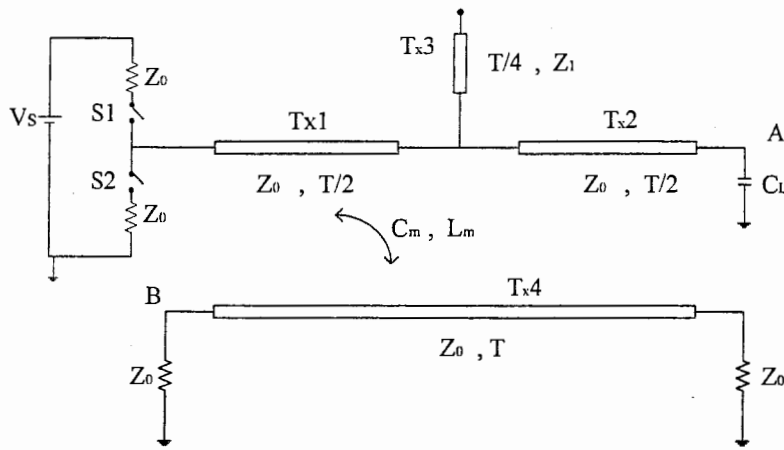


Figure P4

- In the system shown in Fig.P4, after the transmission lines system enters the steady state, the switch S_1 is opened and S_2 is closed simultaneously at time T_s . Please derive and sketch the coupling waveform at the near end of Tx4 (point B) for $T_s \leq t \leq T_s + T$. It is assumed that the system is weakly coupling.
- In the system shown in Fig. P6, steady-state conditions are established with the switch S closed. At the switch S is opened.
 - Find the energy stored in the system at $t = 0^-$.
 - Obtain the solutions for the voltages across R_{L1} and R_{L2} for $t > 0$.
 - Show that the total energy dissipated in R_{L1} and R_{L2} for $t > 0$ is equal to the energy stored in the system at $t = 0^-$.

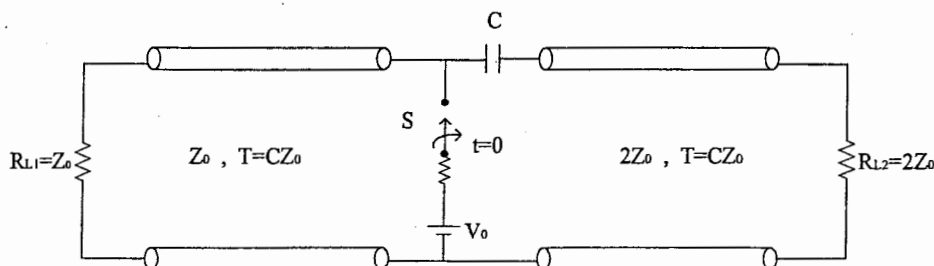


Figure P6

$$1. V(z, t) = 10 \cos(3\pi \times 10^8 t - 2\pi z) \text{ V}$$

$$W = 0.1 \text{ m}$$

$$d = 0.01 \text{ m}$$

$$(a) E_x = \frac{V}{d} = 1000 \cos(3\pi \times 10^8 t - 2\pi z) \text{ V/m}$$

$$(b) H_y = \frac{E_x}{\eta}$$

$$\sqrt{\mu} = \frac{3\pi \times 10^8}{2\pi} = 1.5 \times 10^8 \text{ m/s} = \frac{c}{2} = \frac{1}{\sqrt{\mu_0 \cdot 4\epsilon_0}}$$

$$\therefore \epsilon_r = 4$$

$$\eta = \sqrt{\frac{\mu}{\epsilon}} = \sqrt{\frac{\mu_0}{4\epsilon_0}} = \frac{120\pi}{2} = 60\pi$$

$$\therefore H_y = \frac{50}{3\pi} \cos(3\pi \times 10^8 t - 2\pi z) \text{ A/m}$$

$$(c) I = H_y W$$

$$= \frac{5}{3\pi} \cos(3\pi \times 10^8 t - 2\pi z) \text{ A}$$

$$(d) P = VI$$

$$= \frac{50}{3\pi} \cos^2(3\pi \times 10^8 t - 2\pi z) \text{ W}$$


2.

$$V^+ = 90 \times \frac{60}{90+60} = 36 \text{ V}$$











$$I^+ = \frac{60}{60} = 1 \text{ A}$$

$$\Gamma_R = \frac{180-60}{180+60} = \frac{1}{2}$$

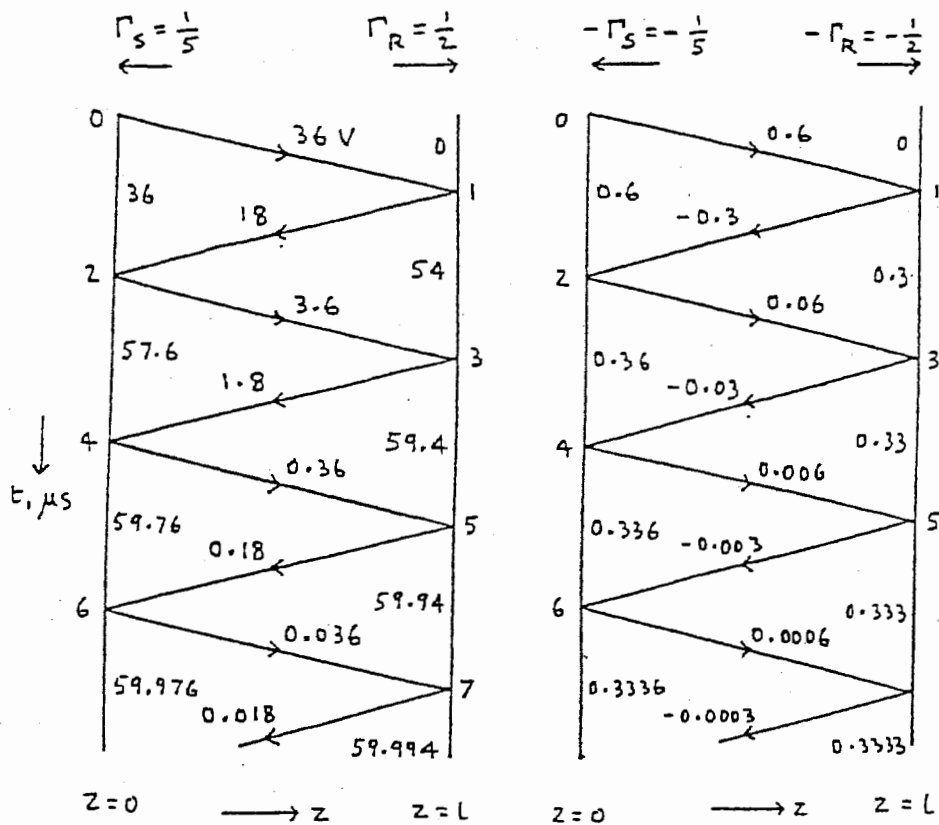
$$P_S = \frac{90-60}{90+60} = \frac{1}{5}$$



2 (continued)

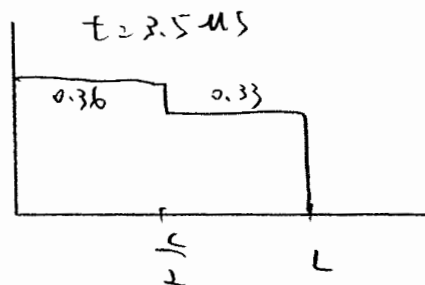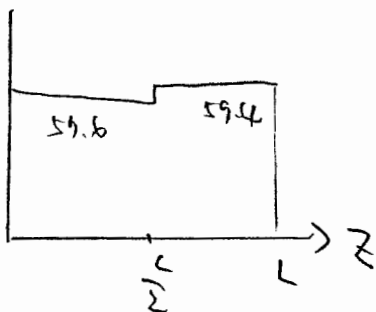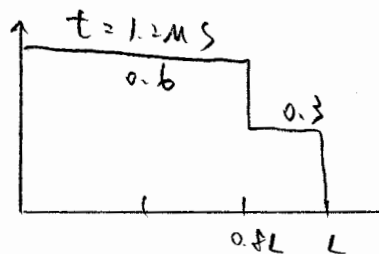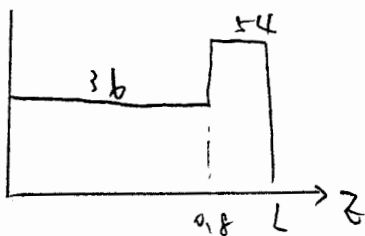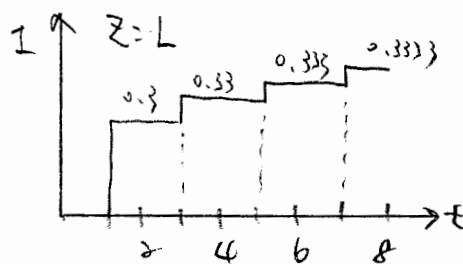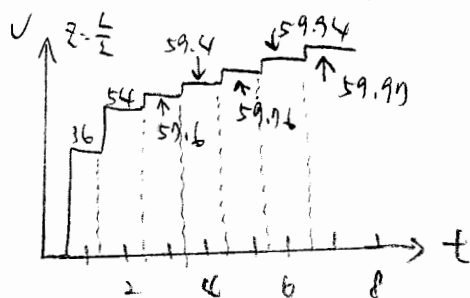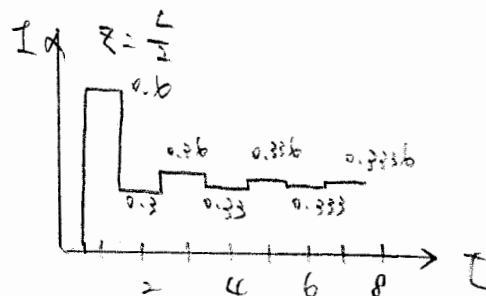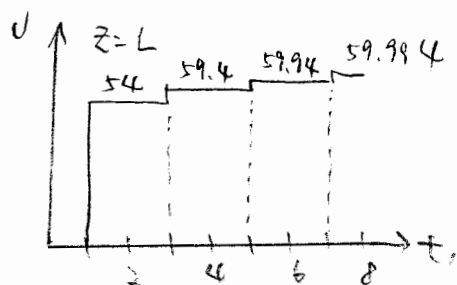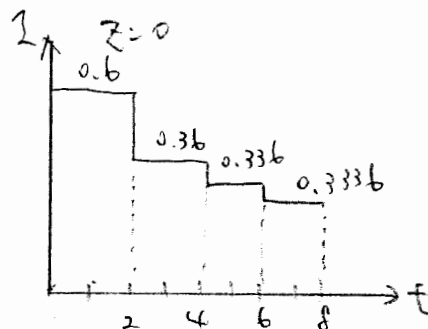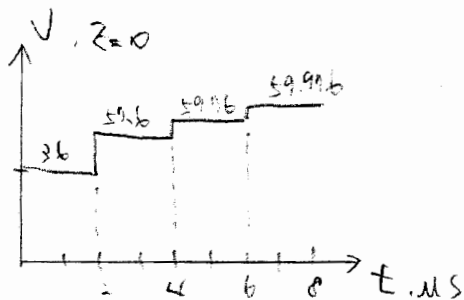

3

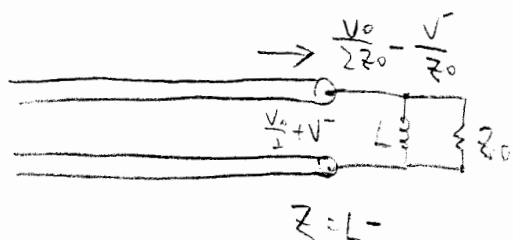

$$\frac{V_0}{2Z_0} - \frac{V^-}{Z_0} = \frac{1}{L} \int \left(\frac{V_0}{2} + V^- \right) dt + \frac{1}{Z_0} \left(\frac{V_0}{2} + V^- \right)$$

$$-\frac{1}{Z_0} \frac{dV^-}{dt} = \frac{1}{L} \left(\frac{V_0}{2} + V^- \right) + \frac{1}{Z_0} \frac{dV^-}{dt}$$

$$\frac{2L}{Z_0} \frac{dV^-}{dt} + V^- = -\frac{V_0}{2}$$

$$V^- = -\frac{V_0}{2} + A e^{-(\frac{Z_0}{2L})t}$$

At $t = T^+$, current through L is zero,

$$\therefore \left[\frac{V_0}{2Z_0} - \frac{V^-}{Z_0} \right]_{t=T^+} = \frac{1}{Z_0} \left[\frac{V_0}{2} + V^- \right]_{t=T^+}$$

$$[V^-]_{t=T^+} = 0$$

$$0 = -\frac{V_0}{2} + A e^{-(\frac{Z_0}{2L})T}$$

$$A = \frac{V_0}{2} e^{(\frac{Z_0}{2L})T}$$

$$V^-(t) = -\frac{V_0}{2} + \frac{V_0}{2} e^{-(\frac{Z_0}{2L})(t-T)}$$

$$[V]_{z=L^+} = [V]_{z=L^-} = \frac{V_0}{2} + V^-$$

$$= \frac{V_0}{2} e^{-(\frac{Z_0}{2L})(t-T)} \quad \text{for } t \geq T$$

#

4.

(a) a, $V_{in} = \frac{Z_0}{Z_0 + Z_0} V_s = \frac{1}{2} V_s$

b, $\Gamma_{stub} = \frac{(Z_1/Z_0) - Z_0}{(Z_1/Z_0) + Z_0} = -\frac{Z_0}{2Z_1 + Z_0}$

$\tau_{stub} = 1 + \Gamma = \frac{2Z_1}{2Z_1 + Z_0}$

c, $V_3^+ = \tau_{stub} V_{in} = V_2^+ = \frac{2Z_1}{2Z_1 + Z_0} \cdot \left(\frac{1}{2} V_s\right) = \frac{Z_1 V_s}{2Z_1 + Z_0}$

d, $V_3^{+-} = 2V_3^+ \text{ (open)} = \frac{2Z_1 V_s}{2Z_1 + Z_0}$

e, $\tau' = 1 + \frac{\frac{Z_0}{2} - Z_1}{\frac{Z_0}{2} + Z_1} = \frac{2Z_0}{2Z_1 + Z_0}$ (from stub (TX3) to (TX2))

$V_{3,2}^{+-} = \tau' V_3^{+-} = \frac{2Z_0 Z_1}{(2Z_1 + Z_0)^2} V_s$

f, V_2^+ arriving C_L at T


$V_{3,2}^{+-}$ arriving C_L at $T + \frac{T}{2}$

So, V_2^+ and $V_{3,2}^{+-}$ charging up C_L with time constant $C_L Z_0$,

$V_C(t) = 0, \quad 0 \leq t < T$

$V_C(t) = V_{C1}(t) = 2V_2^+ (1 - e^{-(t-T)/C_L Z_0}), \quad T \leq t < 1.5T$

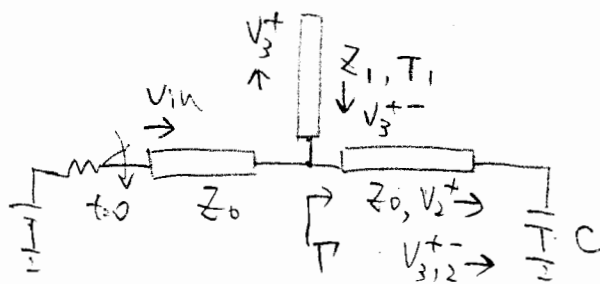$V_C(t) = V_{C1}(t) + V_{C2}(t) = V_{C1}(t) + 2V_{3,2}^{+-} (1 - e^{-(t-1.5T)/C_L Z_0}), \quad 1.5T \leq t \leq 1.75T$



4 (b)

$$V_{c1}(t) = 2V_s^+ (1 - e^{-(t-T)/C_L Z_0})$$

$$t = T + C_L Z_0$$

$$V_{c1} = 2V_s^+ (1 - e^{-1}) \geq V_{th}$$

$$\Rightarrow \frac{2Z_1 V_s}{2Z_1 + Z_0} (1 - e^{-1}) \geq V_{th}$$

$$\Rightarrow \frac{2Z_1}{2Z_1 + Z_0} \geq \frac{V_{th}}{V_s(1 - \frac{1}{e})}$$


$$\Rightarrow \underline{Z_1 \geq \frac{Z_0 V_{th}}{2V_s(1 - e^{-1}) - 2V_{th}}}$$

5.

a. At $t = T_s$

$$V^+ = -\frac{Z_0}{Z_0 + Z_0} V_s = -\frac{V_s}{2}$$

$$I^+ = -V_0 \frac{1}{R_L + Z_0}$$

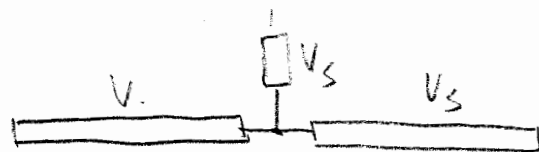


$$b. V^{+-} = \Gamma_{sub} \cdot V^+ = \frac{Z_0}{2Z_1 + Z_0} \cdot \frac{V_s}{2} = \frac{Z_0 V_s}{2(2Z_1 + Z_0)}$$


c. Coupling voltage at point B contributed from backward coupling from V^+ and forward coupling from V^{+-}

$$V_b(t) = K_b (V^+(t) - V^+(t-T)) = K_b \left(-\frac{V_s}{2} H(t) + \frac{V_s}{2} H(t-T) \right)$$

$$V_f(t) = \frac{V_p T}{2} K_f \delta(t-T) \times \frac{Z_0 V_s}{2(2Z_1 + Z_0)}$$
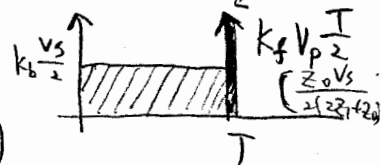
$$K_b = \frac{1}{4} V_p (C_m Z_0 + \frac{L_m}{Z_0}), \quad K_f = \frac{1}{2} (C_m Z_0 - \frac{L_m}{Z_0}),$$




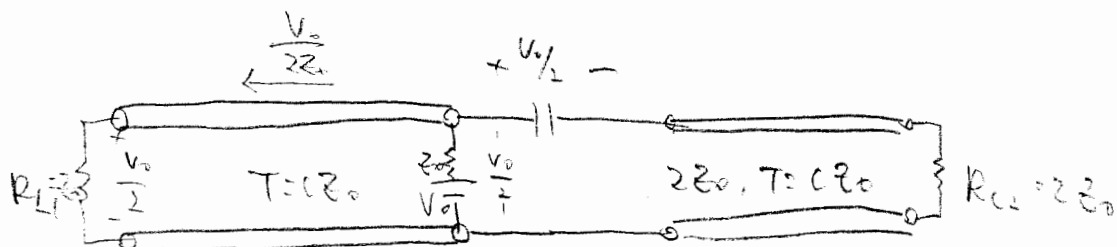

(a) Energy stored in the system

$$= \frac{1}{2} C \left(\frac{V_0}{2} \right)^2 + \frac{1}{2Z_0} \left(\frac{V_0}{2} \right)^2 (Z_0 + \frac{1}{2} \left(\frac{V_0}{2Z_0} \right)^2 Z_0 (lZ_0))$$

$$= \frac{3}{8} C V_0^2$$

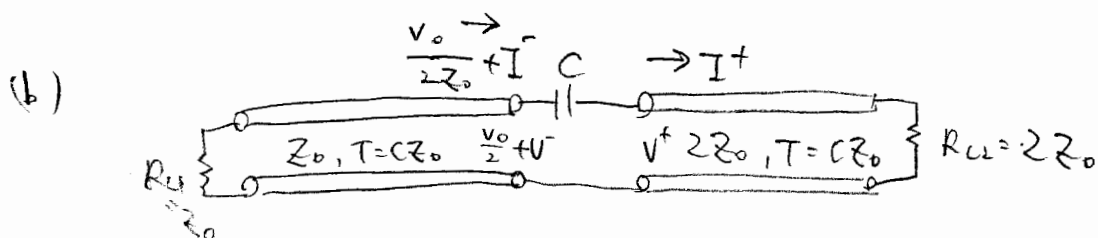

$$I^+ = \frac{V_0}{2Z_0} + I^-$$

$$\frac{V^+}{2Z_0} = \frac{V_0}{2Z_0} - \frac{V^-}{Z_0}$$

$$V^- = -\frac{V^+}{2} - \frac{V_0}{2}$$

$$C \frac{d}{dt} \left(\frac{V_0}{2} + V^- - V^+ \right) = I^+$$

$$C \frac{d}{dt} \left(\frac{V_0}{2} - \frac{V^+}{2} - \frac{V_0}{2} - V^+ \right) = -\frac{V^+}{2Z_0}$$

$$3CZ_0 \frac{dV^+}{dt} + V^+ = 0$$

$$V^+ = A e^{-\frac{1}{3CZ_0} t}$$

$$I, C. \left[\frac{V_0}{2} + V^- - V^+ \right]_{t=0} = \frac{V_0}{2}$$

b. (continued)

$$\left[-\frac{V^+}{2} - V^+ \right]_{t=0} = \frac{V_0}{2}$$

$$[V^+]_{t=0} = -\frac{1}{3}V_0$$

$$\therefore V^+ = -\frac{1}{3}V_0 e^{-\frac{1}{3c\epsilon_0}t}$$

$$V^- = -\frac{V_0}{2} + \frac{1}{6}V_0 e^{-\frac{1}{3c\epsilon_0}t}$$

$$V_{RL1} = \begin{cases} \frac{V_0}{2}, & t < T \\ \frac{1}{6}V_0 e^{-\frac{1}{3c\epsilon_0}(t-T)}, & t > T \end{cases}$$

$$V_{RL2} = \begin{cases} 0, & t < T \\ -\frac{1}{3}V_0 e^{-\frac{1}{3c\epsilon_0}(t-T)}, & t > T \end{cases}$$

(c) RL1:

$$E_1 = \left(\frac{V_0}{2} \right)^2 \frac{1}{2\epsilon_0} (c\epsilon_0) + \frac{1}{2\epsilon_0} \int_T^\infty \frac{V_0^2}{36} e^{-\frac{2}{3c\epsilon_0}(t-T)} dt$$

$$= \frac{1}{4} c V_0^2 + \frac{V_0^2}{36\epsilon_0} \left[\frac{e^{-\frac{2}{3c\epsilon_0}(t-T)}}{-\frac{2}{3c\epsilon_0}} \right]_{t=T}^\infty = \frac{7}{24} c V_0^2$$

RL2:

$$E_2 = \frac{1}{2\epsilon_0} \int_T^\infty \frac{V_0^2}{9} e^{-\frac{1}{3c\epsilon_0}(t-T)} dt = \frac{1}{12} c V_0^2$$

$$\text{Sum, } E_{\text{total}} = E_1 + E_2 = \left(\frac{7}{24} + \frac{1}{12} \right) c V_0^2 = \frac{3}{8} c V_0^2$$

#