
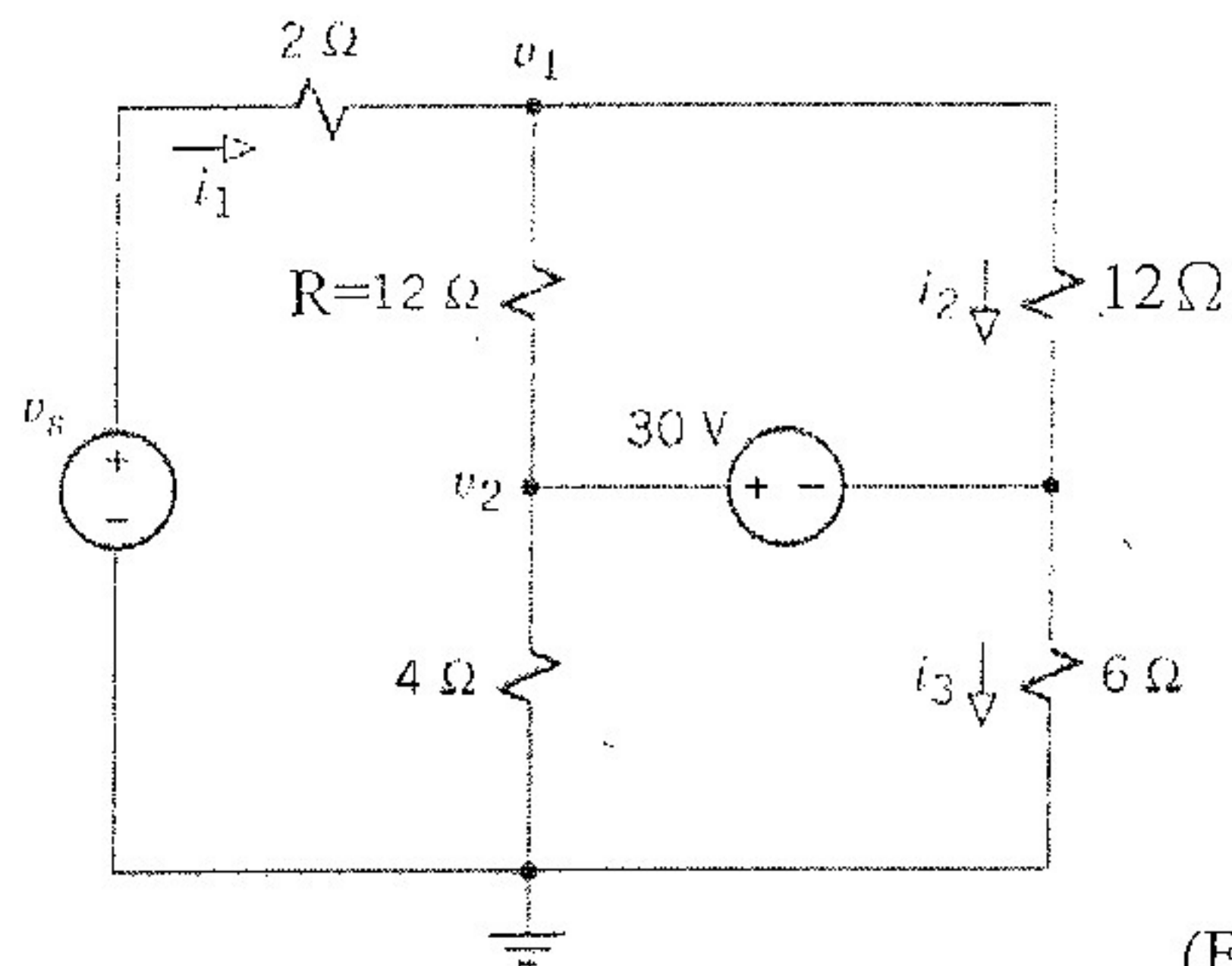


1. (30%) Let $v_s = 23\text{V}$ in Fig. 1. Use node or mesh analysis to calculate the power supplied by each source and power consumed by resistor R.

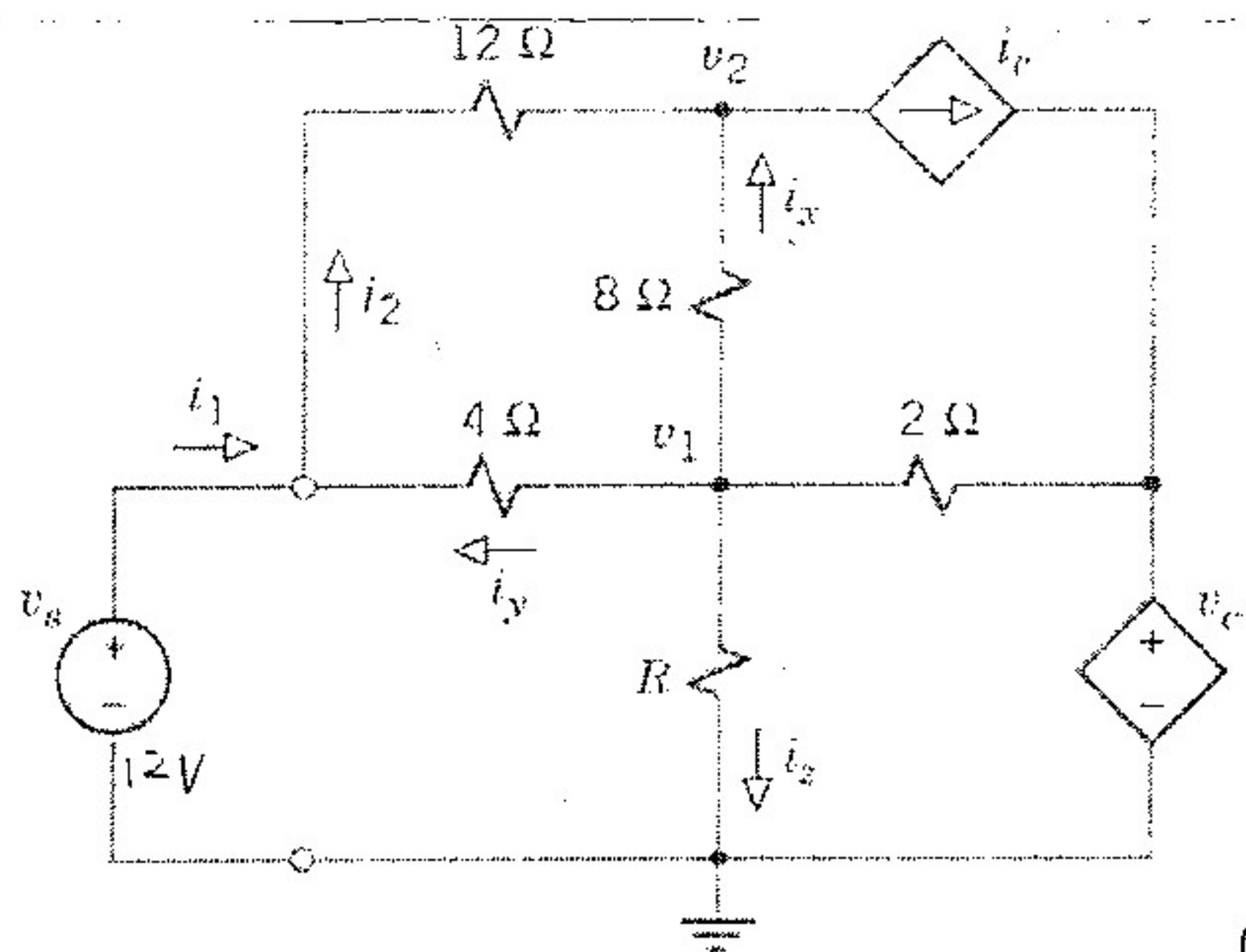


(Fig. 1)

2. (30%) Let the circuit in Fig. 2 have $v_s = 12\text{V}$, $i_c = 2 i_x$, $v_c = 6\Omega \times i_z$, and $R = 3\Omega$. Use node or mesh analysis to obtain v_1 , v_2 , i_1 , i_2 , and the equivalent input resistance $R_{eq} = v_s / i_1$.



(Fig. 2)

3. (10%) Derive the differential equation relating v_{out} to v_{in} for the ideal op-amp circuit in Fig. 3.

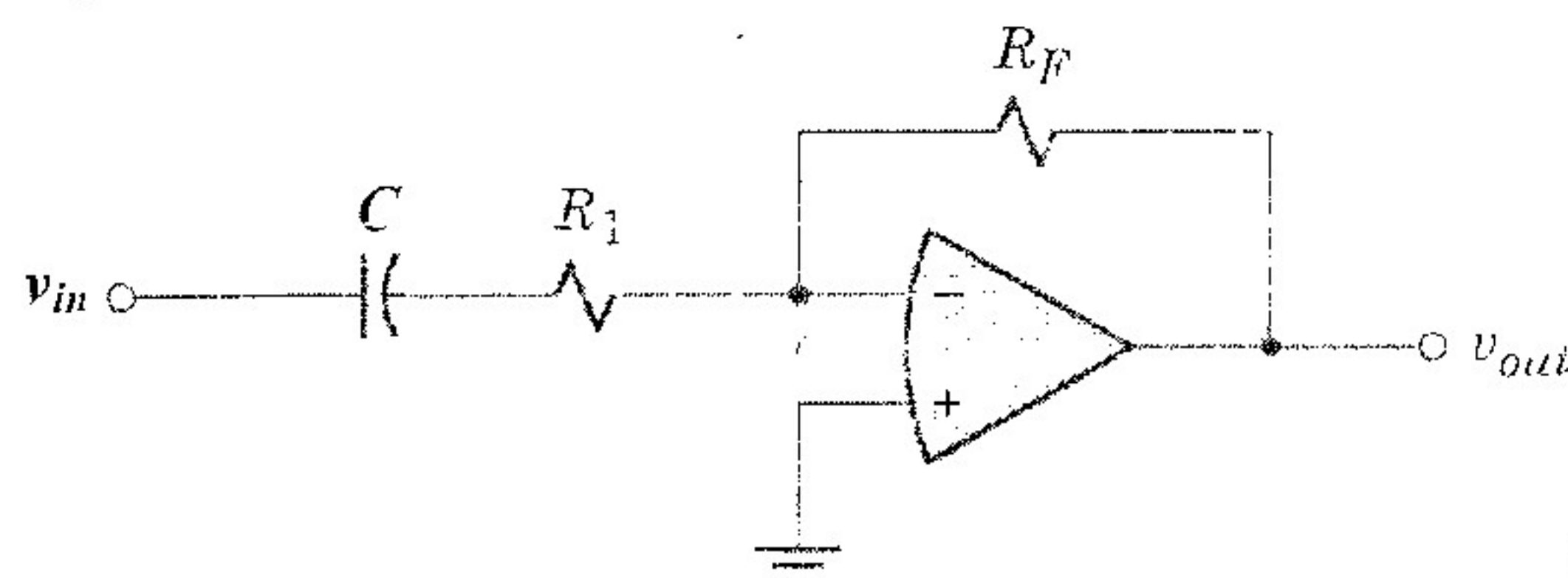

(Fig. 3)

4. (30%) Let $L = 1\text{H}$, $R = 120\Omega$, and $C = 500\mu\text{F}$ in Fig. 4.
- (a) Find the natural response $i_N(t)$. Is the circuit stable?
 - (b) Find the forced response $i_F(t)$ if $v = 520 \cos 100t$.
 - (c) If $i(0) = di(t)/dt|_{t=0} = 0$, find the complete solution $i(t)$.

