

1. (20%)

- (1) (8%) Find the transfer function $T(s) \equiv V_o/V_i$ of the circuit in Fig. 1.
- (2) (8%) Given that $Q = 10$, $R = 100 \text{ k}\Omega$ and $C = 1 \text{ nF}$, find the voltage gain of a sinusoidal signal at $\omega = 10000 \text{ rad}$.
- (3) (4%) Use the device parameters in (2) to find the output voltage V_o for a dc input of 1 V.

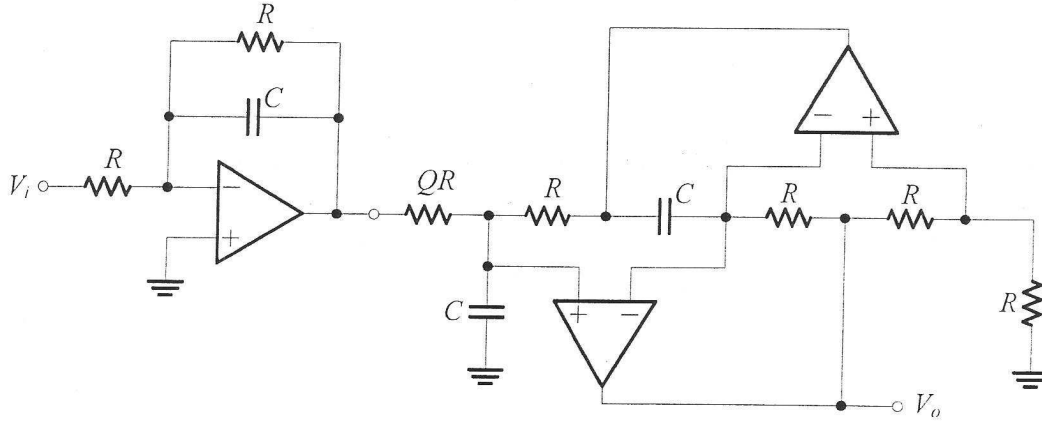


Fig. 1

2. (20%) Fig. 2 shows a Tow-Thomas biquad circuit.

- (1) (8%) Please derive the transfer functions V_A/V_{in} and V_B/V_{in} . If a low-pass response is designed, which node should be taken as the output node?
- (2) (8%) The circuit is designed as a low-pass filter (LPF) having a bandwidth $\omega_n = 2\pi \times 10 \text{ MHz}$ and a Q of 1. If $R_3 = 1 \text{ k}\Omega$, $R_2 = R_4$, and $C_1 = C_2$, determine the values of R_2 and C_1 .
- (3) (4%) In this LPF, what is the amount of gain peaking in the magnitude response (in terms of dB).

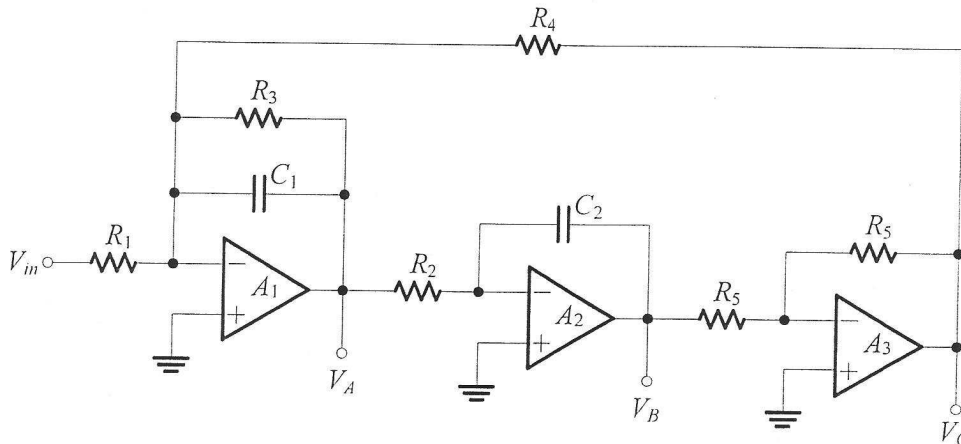


Fig. 2

3. (20%) In Fig. 3, we want to study quadrature oscillator design,
- (1) (5%) What R_f can make this oscillator start?
 - (2) (5%) Under such R_f , what is the oscillation frequency?
 - (3) (5%) Derive the peak-to-peak value of V_{out1} if $R_3 = 2R_4$ and diode turn-on voltage is V_D .
 - (4) (5%) What is the amplitude ratio between V_{out1} and V_{out2} ?

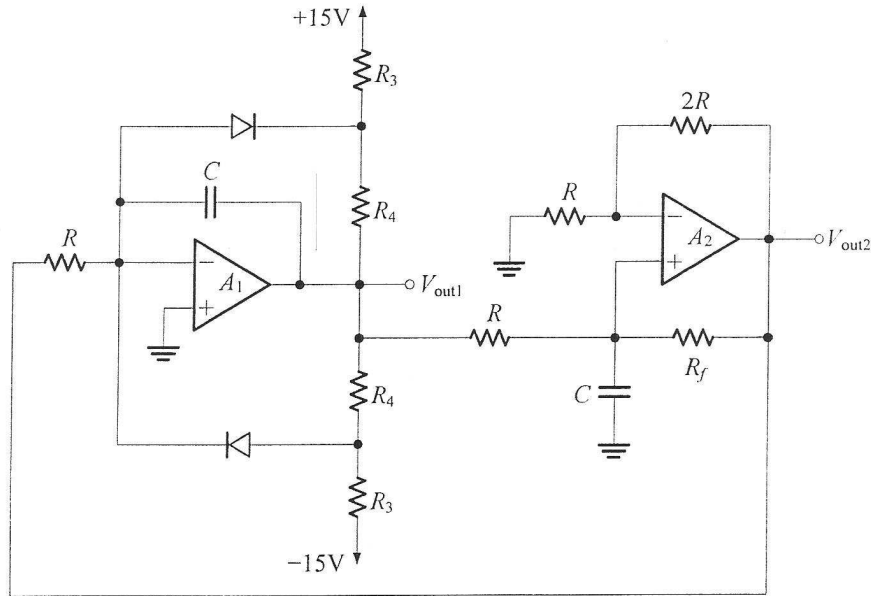


Fig. 3

4. (20%) Design a 100kHz, 50% duty-cycle oscillator. You have the following components to use: one 555 timer, resistors, capacitors, inductors, and diodes. (All passive devices are ideal.)
- (1) (14%) Explain your design with circuits and mathematical expressions, and
 - (2) (6%) determine the values of the passive devices.
5. (20%) For the circuit shown in Fig. 5,
- (1) (5%) Show that the output voltage of the circuit in Fig. 5(a) is given by

$$v_O = -nV_T \ln\left(\frac{v_I}{I_S R}\right), \quad v_I > 0$$

where I_S and n are the diode parameters and V_T is the thermal voltage.

- (2) (7%) Verify that the circuit in Fig. 5(b) implements the transfer characteristic $v_O = -v_1 v_2$ for $v_1, v_2 > 0$. Assume all diodes to be identical.
- (3) (8%) Check the circuit's performance (Fig. 5(b)) for $v_1 = 2V$ and $v_2 = 3V$. Assume all diodes to be identical, with 700-mV drop at 1mA current and $n = 2$.

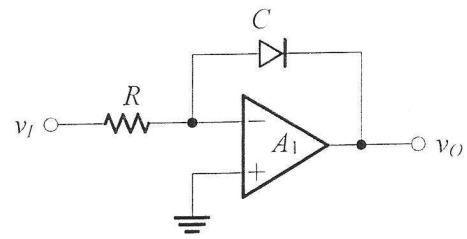


Fig. 5(a)

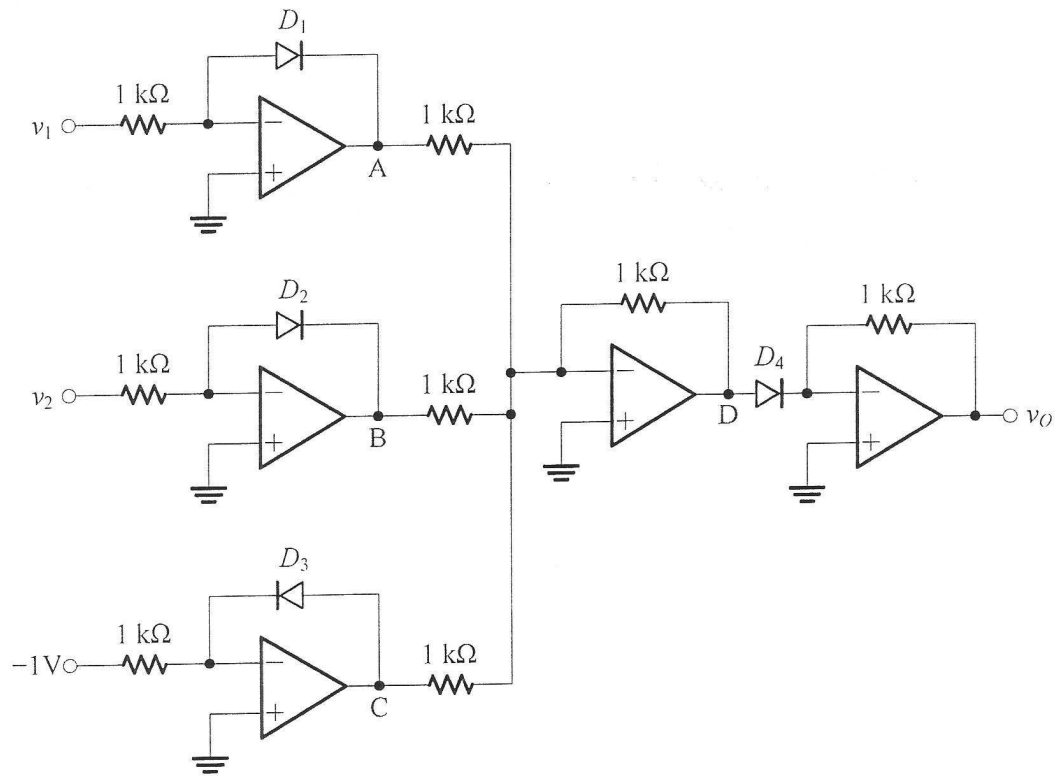


Fig. 5(b)