

Microelectronic Circuits I (Quiz 1)

date: 2008/10/17 (Fri)

time: 14:20~15:10

1. (50%) The circuit is in Fig.1.

- Find the resistances looking into node V_1 , R_1 ; node V_2 , R_2 ; node V_3 , R_3 ; and node V_4 , R_4 .
- Find the currents I_1 , I_2 , I_3 , and I_4 in terms of the input current I .
- Find the voltages V_1 , V_2 , V_3 , and V_4 in terms of (IR) .


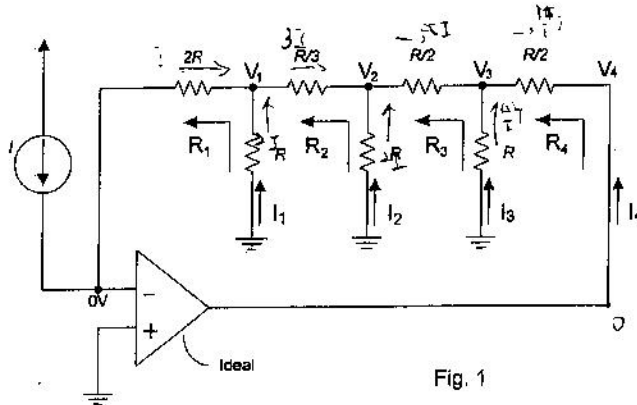


Fig. 1

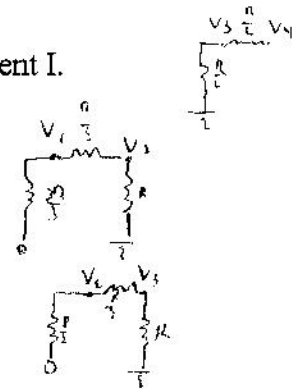

2. (50%) Derive the transfer function of the circuit in Fig.2 (for an ideal op amp)

- show that it can be written in the form

$$\frac{V_o}{V_i} = \frac{-\frac{R_2}{R_1}}{\left[1 + \frac{\omega_1}{j\omega}\right] \times \left[1 + j\frac{\omega}{\omega_2}\right]}$$

$$\text{Where } \omega_1 = \frac{1}{C_1 R_1} \text{ and } \omega_2 = \frac{1}{C_2 R_2}.$$

Assuming that the circuit is designed such that $\omega_2 \gg \omega_1$, find approximate expressions for the transfer function in the following frequency regions:

- $\omega \ll \omega_1$
- $\omega_1 \ll \omega \ll \omega_2$
- $\omega \gg \omega_2$
- If $\omega_1 \gg \omega_2$, find an approximate expression for the transfer function in the frequency range of $\omega_2 \ll \omega \ll \omega_1$. (50%)

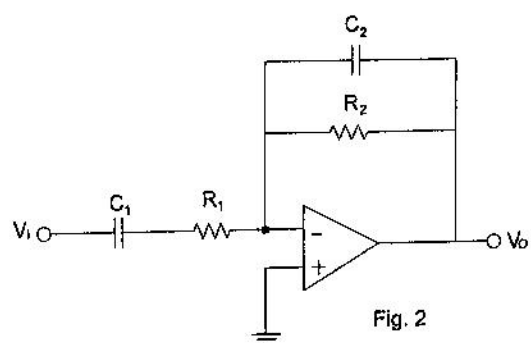


Fig. 2