

Electric Circuits Final Exam 01/21/2000

1. (a). Find all possible dc operating points of the circuit shown in Fig. 1. (10%)
 (b). For each operating point draw the small-signal equivalent circuit. (5%)
2. Find the current-controlled, hybrid 1, and transmission 1 representations of the two-port shown in Fig. 2. (The independent variables for the three representations are: current-controlled: i_1, i_2 , hybrid 1: i_1, v_2 and transmission 1: v_2, i_2 .) (15%)

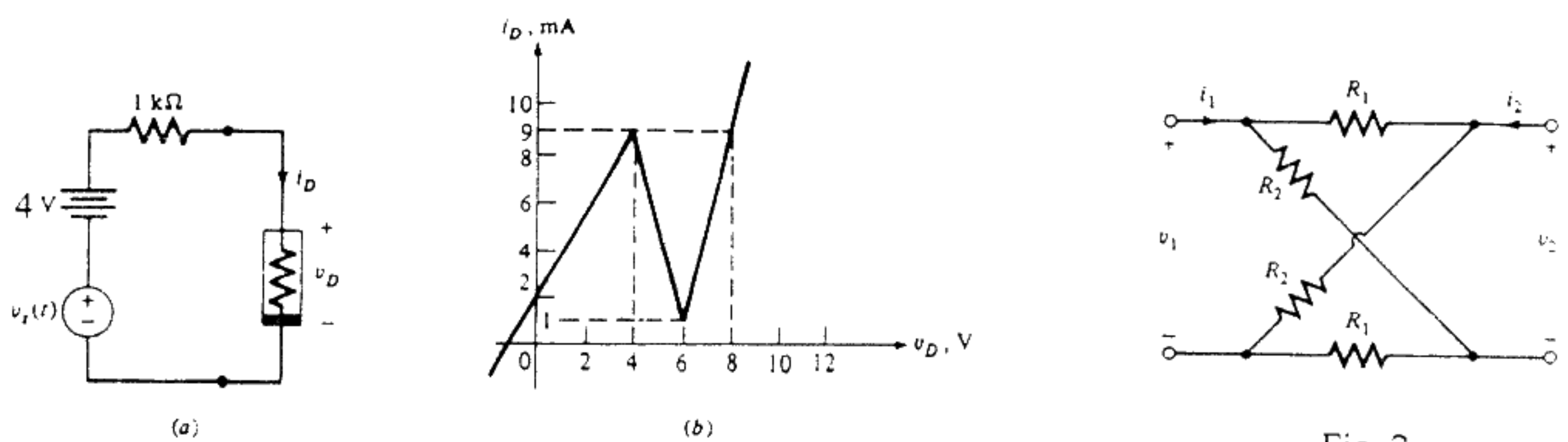


Fig. 1

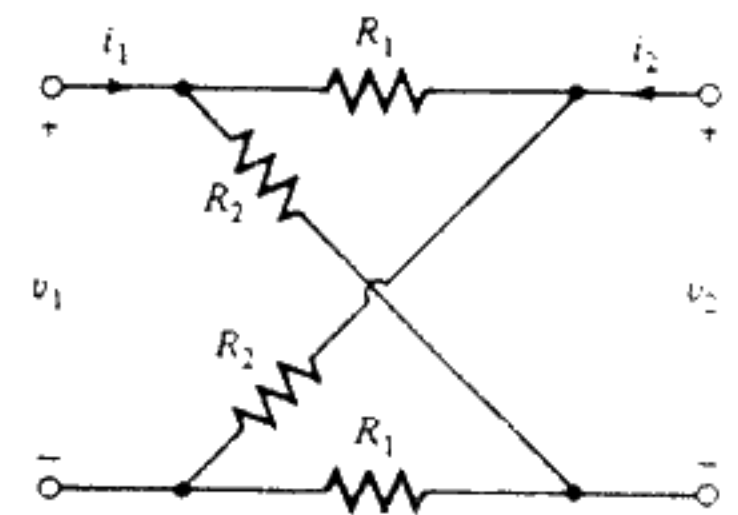


Fig. 2

3. Plot the equivalent circuits for three operating regions of the practical operational amplifiers with saturated voltages $\pm E_{\text{sat}}$. (15%)
4. Describe the four theorems in the Chapter 5. (15%)


5.(10%)

- (a) What is a relaxation point of a charge-controlled capacitor $\hat{V}(q)$?
- (b) Show that if a nonlinear capacitor has more than one relaxation pint, then each point will give the same stored energy $\varepsilon_c(Q)$

6.(30%)

Assume an ideal op-amp model in linear region for the circuit in Fig 3. , and assume that the switch S is closed for all time for part (a),(b),(c),(d). Let $V_o(t)$ be the response

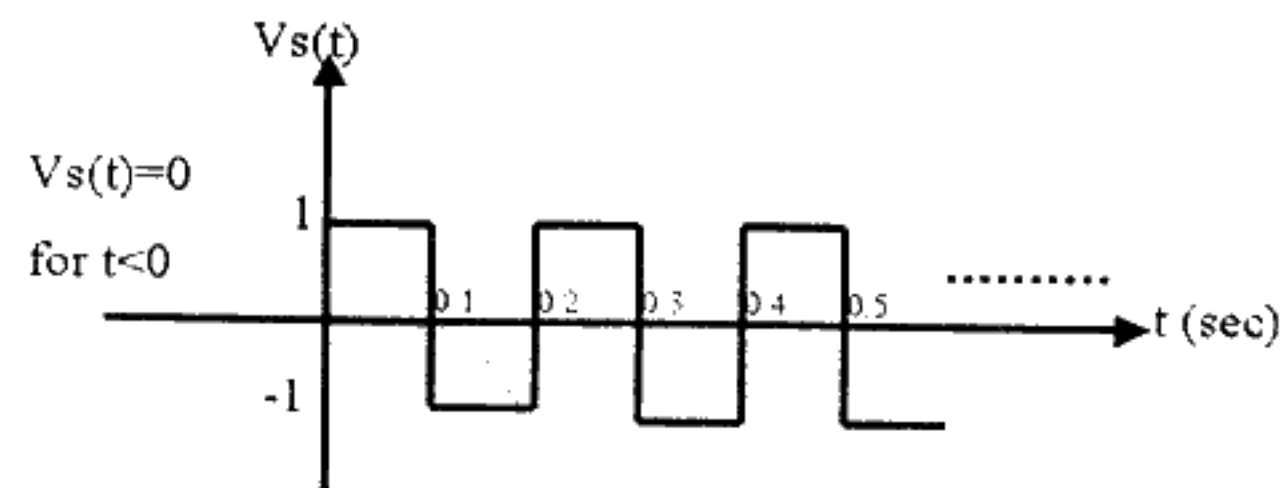- (a) Find the response when $V_s(t)$ is the unit step, $u(t)$
- (b) Find the response when $V_s(t)$ is the unit impulse, $\delta(t)$
- (c) Find the response when $V_s(t)$ is as follows :



- (d) Find $i(t)$ when $V_s(t)$ is as part(c)
- (e) Let $V_s(t) = 1$ V. Find $V_o(t)$ when the switch S is open and closed as follows:

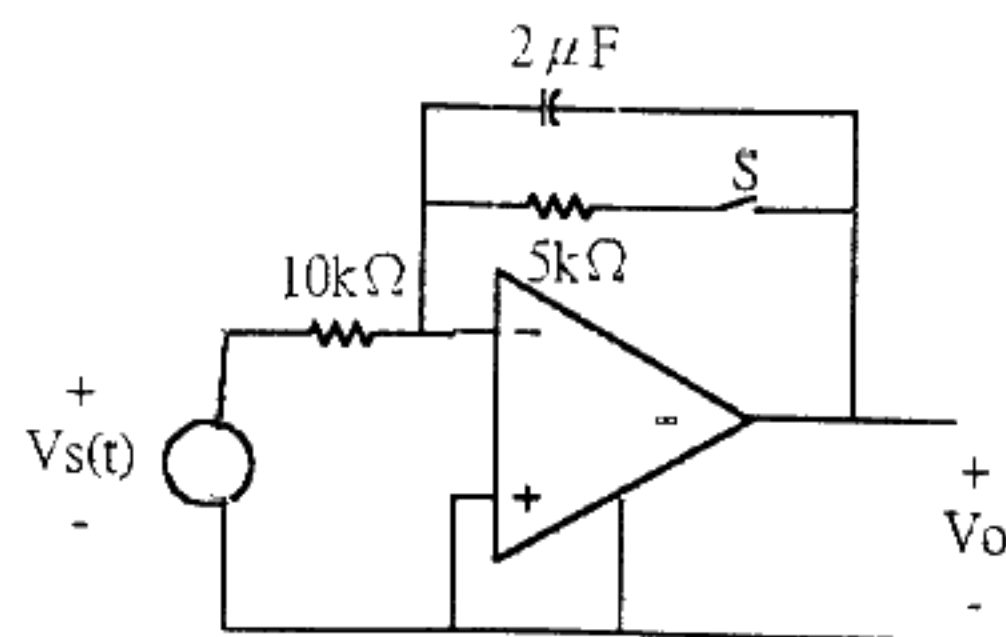
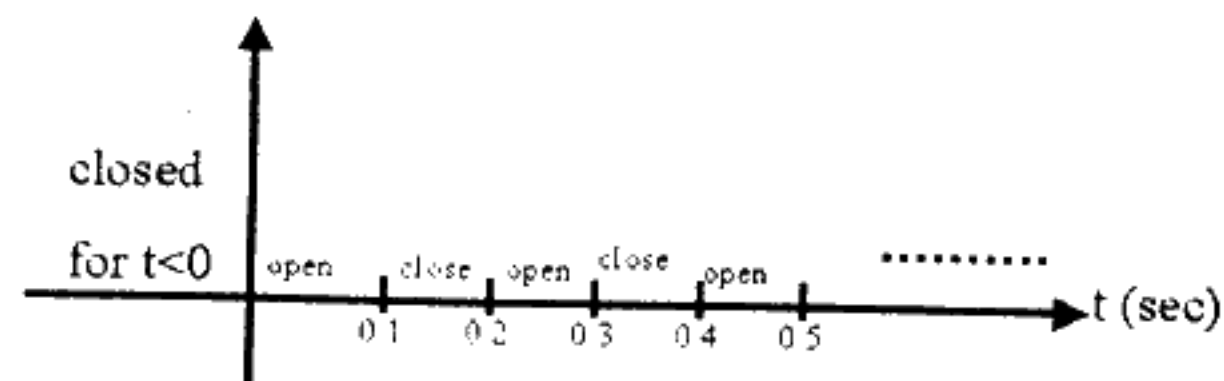


Fig. 3