

Switching Circuits & Logic Design, Fall 2013
Quiz # 2 (2013-12-12, from 2:20pm ~ 3:20pm)

Problem 1: (30 points)

Please design an even-odd counter which counts in sequence $(ABC) = 000, 010, 100, 110, 111, 101, 011, 001, 000 \dots$, using 3 J-K Flip Flops and minimum logic gates. Given the state table of J-K Flip Flops below, please finish the K-map of $J_A, K_A, J_B, K_B, J_C, K_C$, and show the SOP of them.

Q	Q ⁺	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Figure p1.1 State table of J-K Flip Flop

$$Q^+ = JQ' + KQ$$

$$0 = JQ'$$


$$1 = J$$

BC \ A	0	1
00		
01		
11		
10		

Figure p1.2 K-map

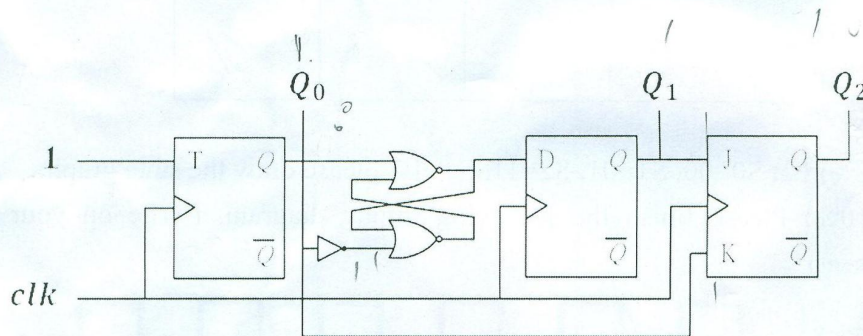Problem 2: (30 points)

Derive the state graph of circuit below. Assume the circuit with initial value $(Q_2Q_1Q_0) = (000)$



$$Q_2^+ =$$

$$J=1$$

$$K=1$$

$$Q_2=1$$

$$J = K = 1$$

$$JQ' + KQ$$

$$K' \times 1$$

$$Q_2 = JQ' + KQ$$

$$JQ' + KQ$$


$$K=1$$

$$JQ'$$

$$J$$

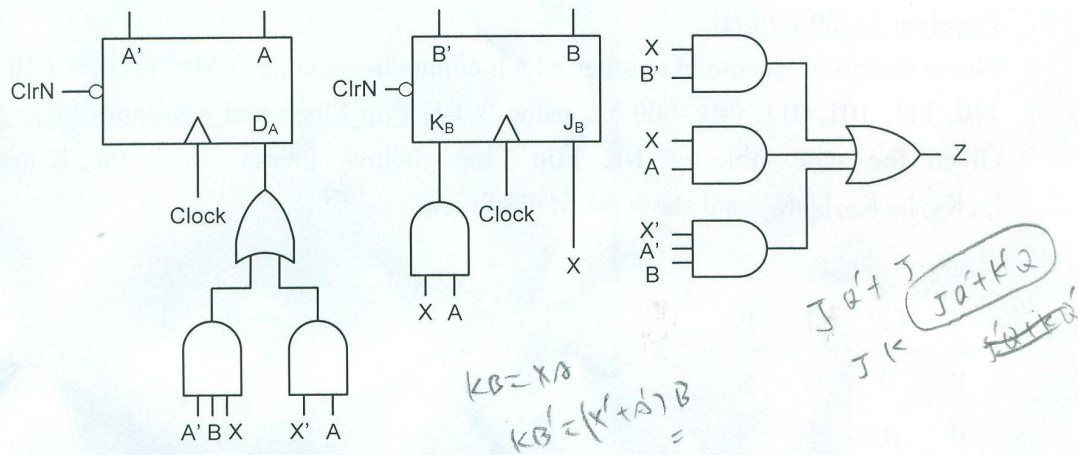Problem 3: (40 points)

For the following sequential circuit, where X is the input pin and Z is the output pin, please answer the followings questions:



- (a) (5%) Is it a Moore machine or a mealy machine? *Mealy machine*
- (b) (9%) Please derive the next state and output equations. That is, $A^+ = f_A(A, B, X)$, $B^+ = f_B(A, B, X)$, $Z = f_Z(A, B, X)$
- (c) (8%) Please derive the state transition table. (write on your answer sheet)

AB	A+B+		Z	
	X=0	1	X=0	1
00				
01				
11				
10				

- (d) (8%) Let $S_0=00$, $S_1=01$, $S_2=11$, $S_3=10$, please draw the state graph.
- (e) (10%) Please finish the following timing diagram. (write on your answer sheet)

