

Switching Circuits and Logic Design

Final Examination

15:30 ~ 17:20, January 16, 2009

1. [12 points] Design a positive-triggered D flip-flop with only the basic logic gates (NOT, AND, OR, NAND, NOR, XOR, and XNOR).
2. Solve the following problems.
 - (a) [15 points] Design a 3-bit counter which counts in the sequences $CBA = 001, 011, 010, 110, 111, 101, 100$, (repeat) $001 \dots$ with only positive-triggered T flip-flops and NAND gates.
 - (b) [5 points] Following (a), what will happen if the counter is started in state 000?
3. The state transition table of the sequential circuit with one input X and one output Z is as follows.

ABC	$A^+B^+C^+$		Z	
	$X=0$	$X=1$	$X=0$	$X=1$
000	011	010	0	1
001	000	010	1	0
010	100	100	0	1
011	010	000	1	0
100	100	000	0	1

- (a) [3 points] Is this a Mealy machine or Moore machine? Draw the state graph.
- (b) [6 points] Please provide the next-state maps for the flip-flops.
- (c) [4 points] If D flip-flops are used, please provide the input maps and input equations for the flip-flops, and the output map and output equation for Z .
- (d) [4 points] Following (c), please draw the circuit to implement this design.
- (e) [5 points] Assume that the initial state of the flip-flops is 000. For an input sequence of $X = 01101$, give a timing diagram for the clock, X , A , B , C , and Z . State changes occur on the rising clock edge, and X changes between rising and falling edges.
- (f) [4 points] What is the correct output sequence for Z ? Please indicate all false outputs on the diagram, if they exist.


NOTE: There are problems in the back.

4. A sequential circuit has one input (X) and one output (Z). Input sequence ending in 111 or 000 will produce an output $Z = 1$ coincident with the last bit of input sequence. The circuit resets after every four inputs.

A typical sequence of inputs and outputs is:

$$\begin{array}{ccccccccc} X = & 1101 & | & 1110 & | & 0000 & | & 0101 & | & 1111 \\ Z = & 0000 & | & 0010 & | & 0011 & | & 0000 & | & 0011 \end{array}$$

 - (a) [10 points] Construct a state table with minimum number of states. (Hint: total 10 states.)
- (b) [8 points] Draw the Mealy state graph.
5. An iterative circuit has a form in the following figure. The output Z is 1 if the total number of ones in input X is odd and the ^{total number} total number of ones in input Y is even, and otherwise Z is 0, where $X = x_1x_2x_3\dots x_i\dots x_n$, and $Y = y_1y_2y_3\dots y_i\dots y_n$.



- (a) [6 points] Find the Moore state table for the iterative circuit. (Hint: State i may contain more than 1-bit)
- (b) [8 points] Find the minimum SOP forms of a typical cell and the output network.
- (c) [4 points] Describe the initial state and simplify the first cell.
- (d) [6 points] By feeding x_i and y_i serially instead of parallelly, the iterative circuit can be converted to the sequential circuit. Plot the sequence circuit and output network.
6. [Bonus 5 points] The following verilog code describes some certain flip-flop we discussed in class. What is it? Show your inference by drawing the circuit and labeling each gate corresponding to the gate name in the code.

```
module mysteryFF ( clock, inport, outport );
    input clock;
    input [1:0] inport;
    output [1:0] outport;
    wire clock_n;
    wire [5:0] midport;

    not not0 (clock_n, clock);
    and and0 (midport[0], inport[0], clock_n, outport[1]);
    and and1 (midport[1], inport[1], clock_n, outport[0]);
    and and2 (midport[4], clock, midport[2]);
    and and3 (midport[5], clock, midport[3]);
    nor nor0 (midport[2], midport[1], midport[3]);
    nor nor1 (midport[3], midport[0], midport[2]);
    nor nor2 (outport[0], midport[5], outport[1]);
    nor nor3 (outport[1], midport[4], outport[0]);
endmodule
```