

電路學期末考

- For the circuit shown in Fig. 1, find v_x as a function of v_s . (10%)
- For the circuit shown in Fig. 2, find v_1 , v_2 and i_a . (15%)
- The switch in Fig. 3 is closed at $t = t_0$, when there is no stored energy.
 - Find the value of the stored energy and v_1 at $t \gg t_0$, when the circuit is in the dc steady state. (16%)
 - Assume that the dc voltage source is replaced by an ac voltage source $50 \cos 100t$, $t \geq t_0$, find $i_1(t)$ in the ac steady state. (9%) (*Note: Exact numerical results are not required. Use symbols such as $\sqrt{\quad}$ and \tan^{-1} when appropriate.*)
- Assume a value for V_2 in Fig. 4 to calculate $\frac{I_2}{I}$ and $\frac{V_1}{I}$ in polar form when $R = 5\Omega$ and $V_x = 2V_2$. (14%)
- An ac motor having impedance $Z_M = 3.6 + j4.8 \Omega$ is supplied from a 240V(rms), 60Hz source.
 - Calculate power factor, I , P, Q. (16%)
 - The power factor will be corrected to unity by connecting a capacitor in parallel with the motor. Find C and the power P and current I supplied by the source. (15%)
 - Calculate the voltage V_M across the motor. (5%)

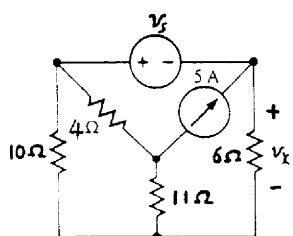


Fig. 1

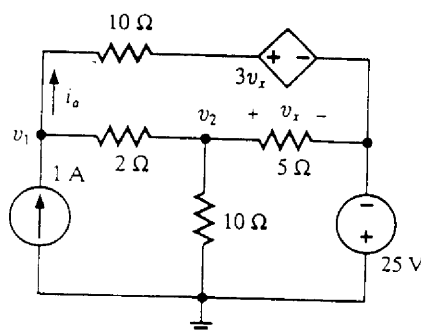


Fig. 2

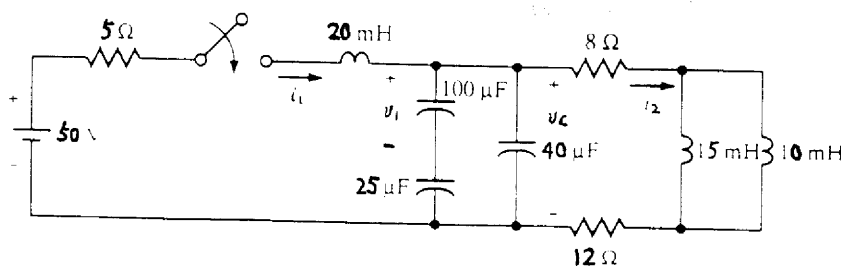


Fig. 3

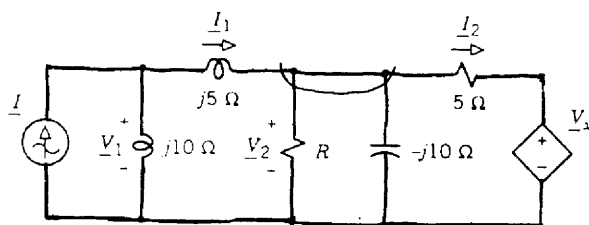


Fig. 4