

2006.5.24

陳秋慶
Ch7 小考

1. Try to derive the following items for the active-loaded MOS pair shown in the following figure. You may name all the parameters you need.

- (a) Transconductance G_m (30%)
- (b) Output resistance R_o (30%)
- (c) Differential gain (20%)
- (d) Common-mode gain (20%)

