

1. Assume a value for \underline{I}_1 in Fig.1 to calculate $\frac{V_1}{V}$ (15%) and $\frac{V}{I}$ (15%) in polar form when $R=6\Omega$ and $\underline{I}_x = 2\underline{I}_1$.

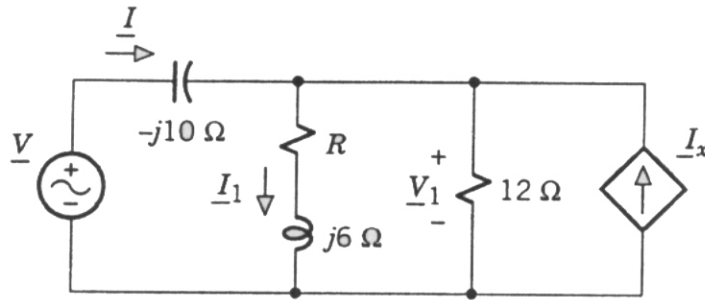


Fig. 1

2. For the circuit shown in Fig.2, find i_1 , i_2 and v_a using mesh analysis. (15%)

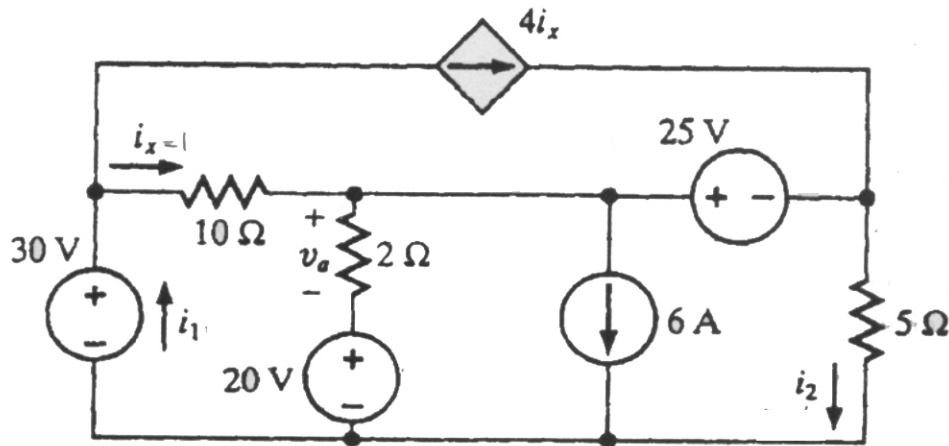


Fig. 2

3. The circuit shown in Fig.3 has two loads and a switch. (a). When the switch is open (i.e., not connected), $\underline{I} = 100A(rms)\angle 0^\circ$. Find the real power and power factor of load #1. (10%) (b). When the switch is closed, $\underline{I} = 125A(rms)\angle -30^\circ$. Find the reactive power of load #2. (5%)

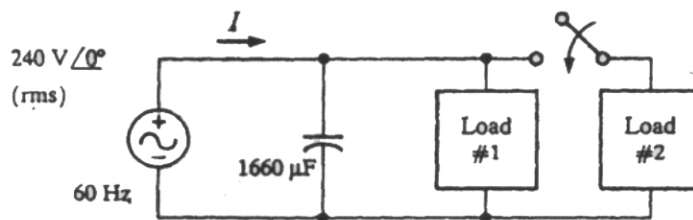


Fig. 3

4. For the circuit shown in Fig.4 and

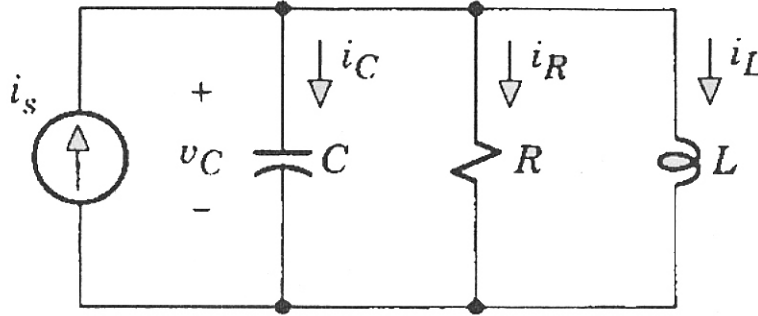


Fig. 4

- (a) Show that critical damping in a parallel RLC circuit corresponds to $Q_{par}=0.5$, where Q_{par} is the quality factor for parallel resonance. (6%)
- (b) Find expressions for the initial value and slope at $t=0^+$ for v_C , i_C and i_L in Fig.4 when

$$i_s = \begin{cases} I_1 & , t < 0 \\ I_2 & , t > 0 \end{cases} \quad (6\%)$$

- (c) Find the transient response of i_L when $R = 3\Omega$, $C = \frac{1}{24}F$, $L = 2H$, and

$$i_s = \begin{cases} 2A & , t < 0 \\ -1A & , t > 0 \end{cases} \quad (6\%)$$

- (d) Suppose that $C = \frac{1}{24}F$, $L = 2H$, determine the three different ranges of R ($R \geq 0$) in which overdamping, critical damping, and underdamping occur. (3%)
- (e) Explain why the natural responses of i_C and i_R satisfy the same second order differential equation as i_L . (3%)

5. For the circuit shown in Fig.5, find $i(t)$ for $t > 0$ given that $i_s(t) = 4\cos 10t$ A. (16%)

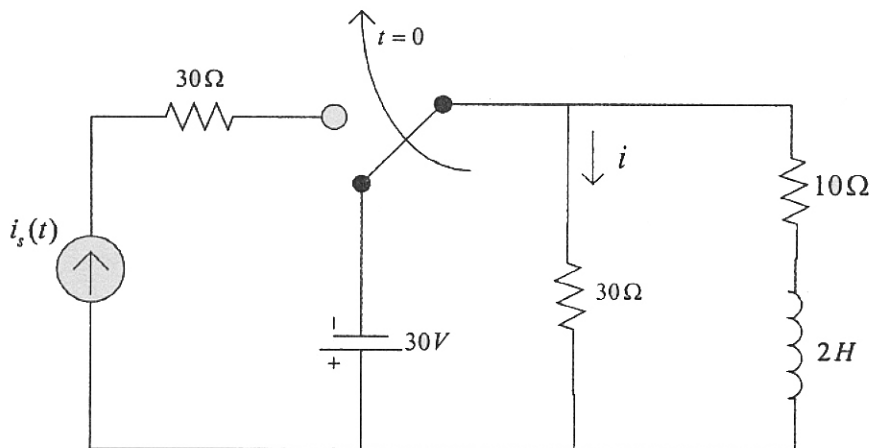


Fig. 5