

1. (25%) The circuit shown in Fig. 1(a) can be used to approximate an inductor; assuming the opamp is ideal.
- (1) For Fig. 1(a), derive an expression for the input impedance,  $Z_{in}$ . (10%)
- (2)  $Z_{in}$  can be modeled as that shown in Fig. 1(b). Please find expressions for  $L$ ,  $R_S$ , and  $R_P$ , in terms of  $C$ ,  $R_1$ , and  $R_2$ . (10%)
- (3) To realize a high- $Q$  inductor, how would you choose  $R_1$  and  $R_2$ . You must explain your reasons. (5%)

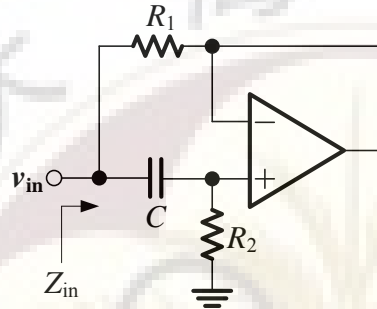


Fig. 1(a)


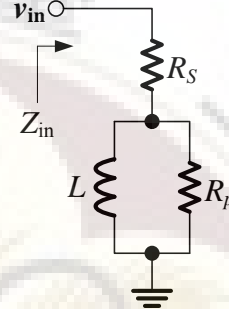


Fig. 1(b)

(Solution)

- (1) For Fig. 1(a), derive an expression for the input impedance,  $Z_{in}$ . (10%)

Answer:

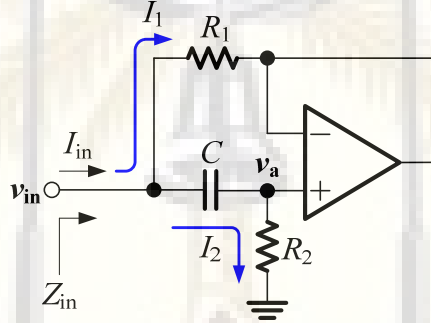


$$\begin{aligned}
 I_{in} &= I_1 + I_2 = (v_{in} - v_a) \frac{1}{R_1} + v_a \frac{1}{R_2} = v_{in} \left( 1 - \frac{sCR_2}{1 + sCR_2} \right) \frac{1}{R_1} + v_{in} \frac{sC}{1 + sCR_2} \\
 &= v_{in} \left[ \left( \frac{1 + sCR_2}{1 + sCR_2} - \frac{sCR_2}{1 + sCR_2} \right) \frac{1}{R_1} + \frac{sC}{1 + sCR_2} \right] = v_{in} \left[ \left( \frac{1}{1 + sCR_2} \right) \frac{1}{R_1} + \frac{sC}{1 + sCR_2} \right] \\
 &= v_{in} \left[ \frac{1}{(1 + sCR_2) R_1} + \frac{sC}{1 + sCR_2} \left( \frac{R_1}{R_1} \right) \right] = v_{in} \left[ \frac{1 + sCR_1}{(1 + sCR_2) R_1} \right] \\
 Z_{in} &= \frac{v_{in}}{I_{in}} = \frac{(1 + sCR_2) R_1}{1 + sCR_1}
 \end{aligned}$$

$$\text{where: } v_a = v_{in} \times \frac{R_2}{R_2 + \frac{1}{sC}} = v_{in} \times \frac{sCR_2}{1 + sCR_2}$$

(2)  $Z_{in}$  can be modeled as that shown in Fig. 1(b). Please find expressions for  $L$ ,  $R_s$ , and  $R_p$ , in terms of  $C$ ,  $R_1$ , and  $R_2$ . (10%)

Answer:

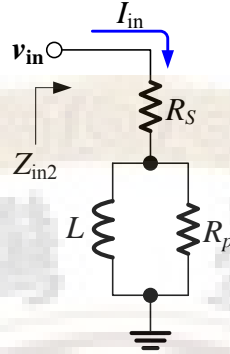

$$Z_{in2} = R_s + (sL \parallel R_p) = R_s + \frac{1}{\frac{1}{sL} + \frac{1}{R_p}} = R_s + \frac{(sL)R_p}{R_p + sL} = R_s + \frac{sL}{1 + s\frac{L}{R_p}} \dots (1)$$

where:

$$\begin{aligned} Z_{in} &= \frac{(1 + sCR_2)R_1}{1 + sCR_1} = \frac{R_1 + sCR_2R_1}{1 + sCR_1} = \frac{R_1 + sCR_1R_2 + sCR_1^2 - sCR_1^2}{1 + sCR_1} = \frac{R_1(1 + sCR_1) + sCR_1(R_2 - R_1)}{1 + sCR_1} \\ &= R_1 + \frac{sCR_1(R_2 - R_1)}{1 + sCR_1} \dots (2) \end{aligned}$$

Comparison (1) with (2)

$$\begin{cases} Z_{in2} = R_s + \frac{sL}{1 + s\frac{L}{R_p}} \\ Z_{in} = R_1 + \frac{sCR_1(R_2 - R_1)}{1 + s\frac{CR_1(R_2 - R_1)}{(R_2 - R_1)}} \end{cases} \rightarrow \begin{cases} R_s = R_1 \\ L = CR_1(R_2 - R_1) \\ R_p = R_2 - R_1 \end{cases}$$

(3) To realize a high- $Q$  inductor, how would you choose  $R_1$  and  $R_2$ . You must explain your reasons. (5%)

Answer:

For a high- $Q$  inductor,  $R_p$  should be larger, and  $R_s$  should be very small. According to the statement, we should choose large  $R_2$  and small  $R_1$ .

Note: The following derivations are only for reference. Those who take the exam do not need to provide them on their answer sheets.

$$P_{in2}(s) = \frac{1}{2} Z_{in2} |I|^2 = \frac{1}{2} |I|^2 \left( R_s + \frac{sL}{1 + s\frac{L}{R_p}} \right) = \frac{1}{2} |I|^2 R_s + \frac{1}{2} |I|^2 \left( \frac{sLR_p}{R_p + sL} \right)$$

$$\rightarrow P_{\text{in}2}(s) = \frac{1}{2}|I|^2 R_s + \frac{1}{2}|I|^2 \frac{sLR_p(R_p - sL)}{(R_p + sL)(R_p - sL)}$$

$$P_{\text{in}2}(j\omega) = \frac{1}{2}|I|^2 R_s + \frac{1}{2}|I|^2 \frac{j\omega LR_p(R_p - j\omega L)}{(R_p + j\omega L)(R_p - j\omega L)} = \frac{1}{2}|I|^2 R_s + \frac{1}{2}|I|^2 \frac{j\omega LR_p^2 + \omega^2 L^2 R_p}{R_p^2 + \omega^2 L^2}$$

$$= \frac{1}{2}|I|^2 \left( R_s + \frac{\omega^2 L^2 R_p}{R_p^2 + \omega^2 L^2} \right) + j\omega \frac{1}{2}|I|^2 \left( \frac{LR_p^2}{R_p^2 + \omega^2 L^2} \right) = P_{\text{loss}} + j\omega \cdot W$$

$$Q = \omega \frac{\text{average energy stored}}{\text{energy loss/second}} = \omega \frac{\frac{1}{2}|I|^2 \left( \frac{LR_p^2}{R_p^2 + \omega^2 L^2} \right)}{\frac{1}{2}|I|^2 \left( R_s + \frac{\omega^2 L^2 R_p}{R_p^2 + \omega^2 L^2} \right)} = \omega \frac{\left( \frac{LR_p^2}{R_p^2 + \omega^2 L^2} \right)}{\left( R_s + \frac{\omega^2 L^2 R_p}{R_p^2 + \omega^2 L^2} \right)}$$

$$= \omega \frac{LR_p^2}{R_s(R_p^2 + \omega^2 L^2) + \omega^2 L^2 R_p} \Big|_{R_s \ll 1} \approx \frac{\omega LR_p^2}{\omega^2 L^2 R_p} = \frac{R_p}{\omega L}, \text{ for } R_s \ll 1$$

2. (25%) Plot the transfer characteristic of the circuit in Fig. 2.


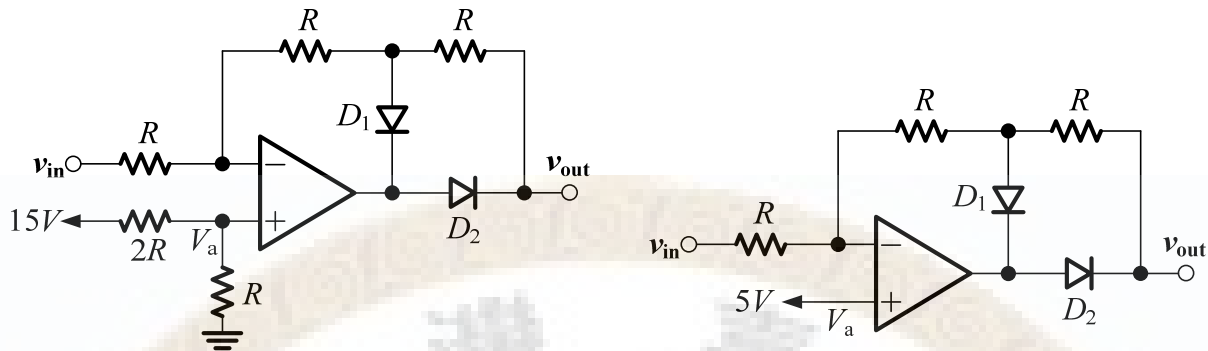


Fig. 2

Answer:  $V_a = 15V \times \frac{R}{2R + R} = 5V$

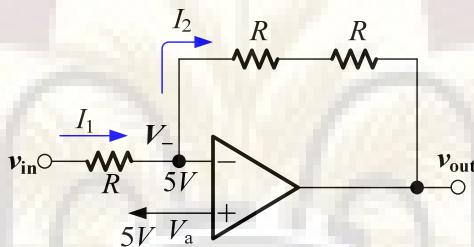
(1) If  $v_{in} < V_a = 5V$  (i.e.,  $V_+ > V_-$ ),  $v_{out} = L_+$  and  $D_1$  OFF,  $D_2$  ON.




$$\frac{v_{in} - V_-}{R} = \frac{V_- - v_{out}}{2R} \rightarrow \frac{2R}{R}(v_{in} - V_-) = V_- - v_{out} \rightarrow 2(v_{in} - V_-) = V_- - v_{out}$$

$$\rightarrow v_{out} = V_- - 2(v_{in} - V_-) = 5 - (2v_{in} - 10) = -2v_{in} + 15$$

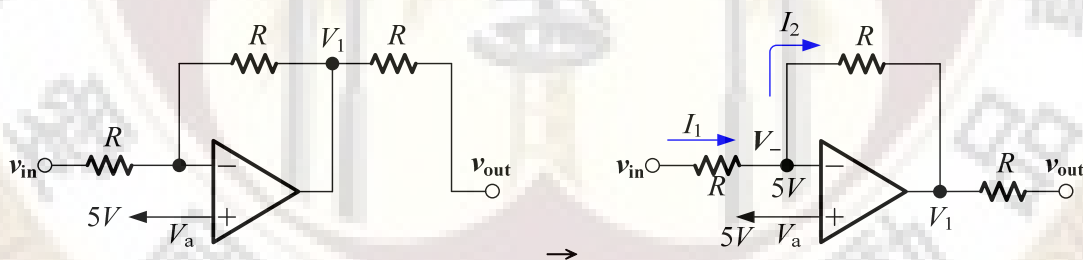(2) If  $v_{in} > V_a = 5V$  (i.e.,  $V_+ < V_-$ ),  $v_{out} = L_-$  and  $D_1$  ON,  $D_2$  OFF.


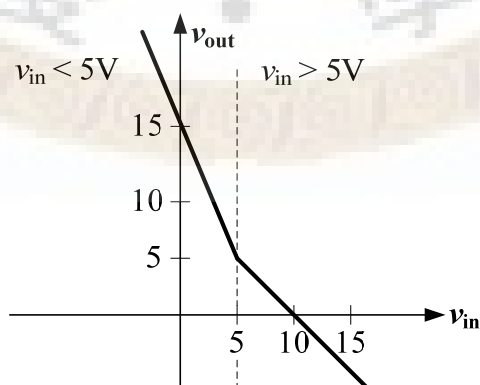
$$\frac{v_{in} - V_-}{R} = \frac{V_- - V_1}{R} \rightarrow v_{in} - V_- = V_- - V_1 \rightarrow V_1 = -v_{in} + 2V_- \rightarrow v_{out} = -v_{in} + 10$$



3. (25%)

(1) For the circuit in Fig. 3, find the transfer function  $T(s) = V_o/V_i$ . (10%)

(2) Choose  $C = 2$  nF. If the circuit is used to reject a frequency component at 10 kHz, find the value of  $R$ . (10%)

(3) For a 5-kHz input sine wave with amplitude of 2 V, find the voltage amplitude at the output. (5%)

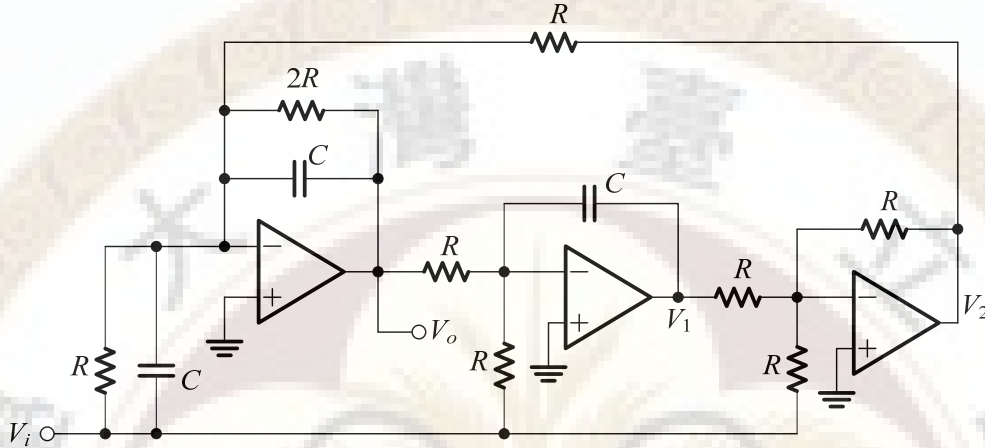


Fig. 3

(1) For the circuit in Fig. 3, find the transfer function  $T(s) = V_o/V_i$ . (10%)

$$\begin{aligned}
 V_o &= -\frac{2R \parallel \frac{1}{sC}}{R \parallel \frac{1}{sC}} V_i - \frac{2R \parallel \frac{1}{sC}}{R} V_2 = -\frac{\frac{1}{\frac{1}{2R} + sC}}{\frac{1}{\frac{1}{R} + sC}} V_i - \frac{\frac{1}{\frac{1}{2R} + sC}}{\frac{1}{R}} \left( \frac{1}{sCR} V_i - V_i + \frac{1}{sCR} V_o \right) \\
 &= -\frac{\frac{1}{\frac{1}{R} + sC}}{\frac{1}{\frac{1}{2R} + sC}} V_i - \frac{1}{\frac{1}{2} + sCR} \left( \frac{1}{sCR} V_i - V_i + \frac{1}{sCR} V_o \right) = -\frac{2 + s2RC}{1 + s2RC} V_i - \frac{2}{1 + s2RC} \left( \frac{1}{sCR} V_i - V_i + \frac{1}{sCR} V_o \right) \\
 &= -\frac{2 + s2RC}{1 + s2RC} V_i - \frac{1}{sCR} \frac{2}{1 + s2RC} V_i + \frac{2}{1 + s2RC} V_i - \frac{1}{sCR} \frac{2}{1 + s2RC} V_o \\
 \rightarrow V_o \left( 1 + \frac{2}{sCR} \frac{1}{1 + s2RC} \right) &= \left( \frac{2}{1 + s2RC} - \frac{2 + s2RC}{1 + s2RC} - \frac{1}{sCR} \frac{2}{1 + s2RC} \right) V_i \\
 \rightarrow V_o \left( 1 + s2RC + \frac{2}{sCR} \right) &= \left[ 2 - (2 + s2RC) - \frac{2}{sCR} \right] V_i = \left[ -s2RC - \frac{2}{sCR} \right] V_i \\
 \frac{V_o}{V_i} &= \frac{-s2RC - \frac{2}{sCR}}{1 + s2RC + \frac{2}{sCR}} = \frac{-s2RC(sCR) - 2}{(sCR) + s2RC(sCR) + 2} = \frac{-s^2 2R^2 C^2 - 2}{s^2 2R^2 C^2 + sRC + 2} = -\frac{s^2 + \left( \frac{1}{RC} \right)^2}{s^2 + s \frac{1}{2RC} + \left( \frac{1}{RC} \right)^2}
 \end{aligned}$$

$$\text{where: } V_1 = -\frac{1}{sCR} (V_i + V_o) = \frac{-1}{sCR} (V_i + V_o),$$

$$V_2 = \frac{-R}{R} (V_i + V_1) = -V_i - V_1 = -V_i - \frac{-1}{sCR} (V_i + V_o) = -V_i + \frac{1}{sCR} (V_i + V_o) = \frac{1}{sCR} V_i - V_i + \frac{1}{sCR} V_o$$

(2) Choose  $C = 2 \text{ nF}$ . If the circuit is used to reject a frequency component at  $10 \text{ kHz}$ , find the value of  $R$ . (10%)

Answer:

$$\frac{V_o}{V_i} = -\frac{s^2 + \left(\frac{1}{RC}\right)^2}{s^2 + s\frac{1}{2RC} + \left(\frac{1}{RC}\right)^2} = -\frac{s^2 + \omega_0^2}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2},$$

$$f_0 = \frac{1}{2\pi \cdot RC} = 10\text{kHz}, \rightarrow R = \frac{1}{2\pi \cdot 10\text{kHz} \cdot C} = \frac{1}{2\pi \cdot 10 \times 10^3 \cdot 2 \times 10^{-9}} = \frac{1}{4\pi \times 10^{-5}} = 7.96\text{K}\Omega$$

(3) For a  $5\text{-kHz}$  input sine wave with amplitude of  $2 \text{ V}$ , find the voltage amplitude at the output. (5%)

Answer:

$$T(s) = \frac{V_o(s)}{V_i(s)} = -\frac{s^2 + \left(\frac{1}{RC}\right)^2}{s^2 + s\frac{1}{2RC} + \left(\frac{1}{RC}\right)^2}, \rightarrow T(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = -\frac{\left(\frac{1}{RC}\right)^2 - \omega^2}{\left[\left(\frac{1}{RC}\right)^2 - \omega^2\right] + j\omega\frac{1}{2RC}}$$

$$\frac{V_o(f)}{V_i(f)} = -\frac{\left(\frac{1}{RC}\right)^2 - (2\pi f)^2}{\left[\left(\frac{1}{RC}\right)^2 - (2\pi f)^2\right] + j(2\pi f)\frac{1}{2RC}} = -\frac{1 - (2\pi f \cdot RC)^2}{1 - (2\pi f \cdot RC)^2 + j(\pi f \cdot RC)}$$

$$\left.\frac{V_o(f)}{V_i(f)}\right|_{f=5\text{kHz}} = -\frac{1 - \left(\frac{1}{2}\right)^2}{1 - \left(\frac{1}{2}\right)^2 + j\left(\frac{1}{4}\right)} = -\frac{\frac{3}{4}}{\frac{3}{4} + j\left(\frac{1}{4}\right)} = -\frac{3}{3 + j} = -\frac{3}{\sqrt{3^2 + 1} \angle \tan^{-1}\left(\frac{1}{3}\right)} = -0.95 \angle -18.43^\circ$$

$$\left.\frac{V_o(f)}{V_i(f)}\right|_{f=5\text{kHz}} = -0.95, \rightarrow |V_o(f)|_{f=5\text{kHz}} = -0.95 \times |V_i(f)|_{f=5\text{kHz}} = -0.95 \times 2 = -1.9\text{V}$$

$$\text{where: } f_0 = \frac{1}{2\pi \cdot RC} = 10\text{kHz}, \rightarrow RC = \frac{1}{2\pi \cdot 10\text{kHz}}$$

$$(a) (2\pi f \cdot RC)|_{f=5\text{kHz}} = \frac{2\pi \cdot 5\text{kHz}}{2\pi \cdot 10\text{kHz}} = \frac{1}{2}, (b) (\pi f \cdot RC)|_{f=5\text{kHz}} = \frac{\pi \cdot 5\text{kHz}}{2\pi \cdot 10\text{kHz}} = \frac{1}{4}$$

4. (16%)

- (1) Symbolically derive the loop gain of the Wien-bridge oscillator (4%) shown in Fig. 4.
- (2) Determine the frequency of oscillation (4%) and the condition to start oscillation (4%).
- (3) Find the frequency of oscillation numerically in units of Hz when  $R = 10 \text{ k}\Omega$  and  $C = 16 \text{ nF}$  (4%).

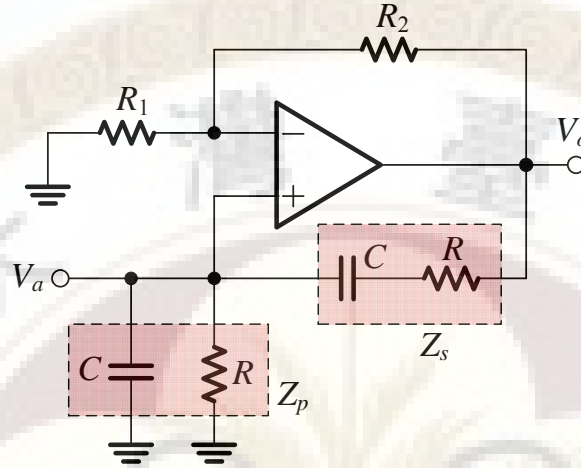


Fig. 4

(Solution)

- (1) Symbolically derive the loop gain of the Wien-bridge oscillator (4%) shown in Fig. 4.

Answer:

$$L(s) = \left[ 1 + \frac{R_2}{R_1} \right] \frac{Z_p}{Z_p + Z_s} = \frac{1 + \frac{R_2}{R_1}}{1 + Z_s Y_p}$$

$$L(j\omega) = \frac{1 + \frac{R_2}{R_1}}{1 + \left( R + \frac{1}{j\omega C} \right) \left( \frac{1}{R} + j\omega C \right)} = \frac{1 + \frac{R_2}{R_1}}{3 + \left( \frac{1}{j\omega RC} + j\omega CR \right)} = \frac{1 + \frac{R_2}{R_1}}{3 + j \left( \omega CR - \frac{1}{\omega RC} \right)}$$

where:  $Z_s = R + \frac{1}{j\omega C}$ ,  $Y_p = \left( \frac{1}{R} + j\omega C \right)$

- (2) Determine the frequency of oscillation (4%) and the condition to start oscillation (4%).

$$L(j\omega) = \frac{1 + \frac{R_2}{R_1}}{3 + j \left( \omega CR - \frac{1}{\omega RC} \right)}, \rightarrow \omega_0 = \frac{1}{RC} \rightarrow (+4\%)$$

$$\rightarrow L(j\omega_0) = \frac{1 + \frac{R_2}{R_1}}{3} = 1, \rightarrow \frac{R_2}{R_1} = 2 \text{ (Condition to start oscillation)} \rightarrow (+4\%)$$

- (3) Find the frequency of oscillation numerically in units of Hz when  $R = 10 \text{ k}\Omega$  and  $C = 16 \text{ nF}$  (4%).

$$\omega_0 = \frac{1}{RC} \rightarrow f_0 = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 10^4 \times 16 \times 10^{-9}} = 994.72 \text{ Hz} \rightarrow (+4\%)$$

5. (9%) Consider a modification of the circuit of Fig. 5 in which  $R_1$  is replaced by a pair of diodes connected in parallel in opposite directions. For  $L_+ = -L_- = 12\text{ V}$ ,  $R_2 = R = 10\text{ k}\Omega$ ,  $C = 0.1\text{ }\mu\text{F}$ , and the diode voltage as a constant denoted  $V_D$ , find an expression for frequency as a function of  $V_D$ .

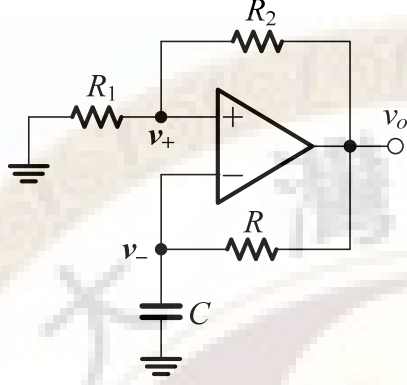


Fig. 5


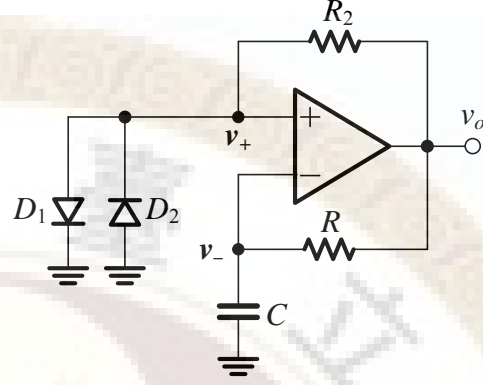


Fig. 5(a)

(Solution)

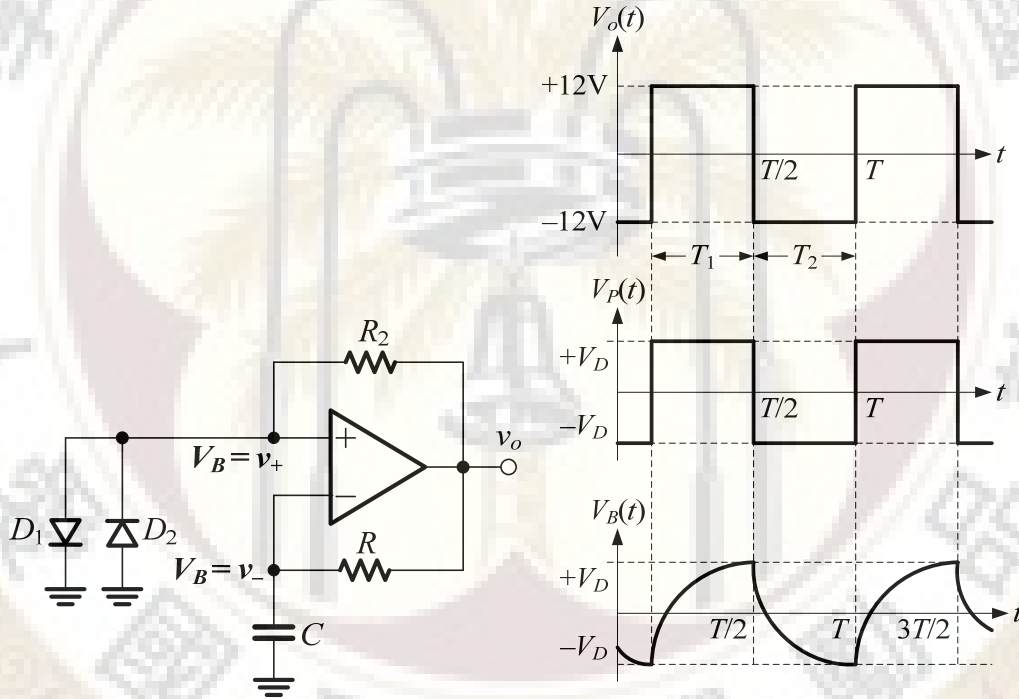

$$V_C(t) = V(\infty) + [V(0) - V(\infty)]e^{\frac{-1}{RC}t}, V_B(\infty) = 12\text{ V}, V_B(0) = -V_D, V_B(T_1) = V_D, T_1 = T_2 = \frac{T}{2},$$

$$\text{During } T_1: V_B(t) = 12 + (-V_D - 12)e^{\frac{-1}{RC}t}, \rightarrow V_B(T_1) = V_D = 12 - (V_D + 12)e^{\frac{-1}{RC}T_1}$$

$$\rightarrow T_1 = \frac{T}{2} = -RC \times \ln\left(\frac{12 - V_D}{12 + V_D}\right) = RC \times \ln\left(\frac{12 + V_D}{12 - V_D}\right) = 10 \times 10^3 \times 0.1 \times 10^{-6} \times \ln\left(\frac{12 + V_D}{12 - V_D}\right),$$

$$T = 2 \times 10^{-3} \times \ln\left(\frac{12 + V_D}{12 - V_D}\right), \rightarrow f = \frac{1}{T} = \frac{1}{2 \times 10^{-3} \times \ln\left(\frac{12 + V_D}{12 - V_D}\right)} = \frac{500}{\ln\left(\frac{12 + V_D}{12 - V_D}\right)}$$