

# 九十二學年度台灣大學電資學院電機系電子學(一)期末考

1. Design the circuit in Fig. 1 so that the transistor operates in saturation with  $V_{SD} = 1$  volt from the edge of the triode region, with  $I_D = 1$  mA and  $V_D = 3$  V, for each of the following devices (use a  $10\text{-}\mu\text{A}$  current in the voltage divider):

- (a) An enhancement MOSFET with  $|V_t| = 1$  V and  $k'_p W/L = 0.5\text{mA/V}^2$
- (b) A depletion MOSFET with  $|V_t| = 2$  V and  $k'_p W/L = 0.5\text{mA/V}^2$
- (c) A depletion MOSFET with  $|V_t| = 3$  V and  $k'_p W/L = 0.125\text{mA/V}^2$
- (d) A depletion MOSFET with  $|V_t| = 4$  V and  $k'_p W/L = 1.25\text{mA/V}^2$
- (e) An enhancement MOSFET with  $|V_t| = 2$  V and  $k'_p W/L = 1.25\text{mA/V}^2$

 


Fig. 1

 


Fig. 2

2. The MOSFETs in the circuit of Fig. 2 are matched, with  $k'_n \left( \frac{W}{L} \right)_1 = k'_p \left( \frac{W}{L} \right)_2 = 50\mu\text{A/V}^2$

and  $|V_t| = 2\text{V}$ . The resistance  $R_2 = 10\text{M}\Omega$ . For G and D open, what are the drain currents  $I_{D1}$  and

$I_{D2}$ ? For  $r_o = \infty$ , what is the voltage gain of the amplifier from G to D? For finite  $r_o$

( $r_o = |V_A|/I_D$ ,  $|V_A| = 180$  V), what is the voltage gain from G to D and the input resistance at G?

If G is driven (through a large coupling capacitor) from a source  $v_i$  having a resistance of  $1\text{M}\Omega$ , find the voltage gain  $v_d/v_i$ . For what range of output signals do  $Q_1$  and  $Q_2$  remain in the pinch-off region?

3. (a) If the common-emitter BJT circuit as shown in Fig. 3 is used as an amplifier, what is the limitation on choosing the value of  $R_C$  if the DC voltage at the input is 2.5V? (5%)
- (b) Determine the value of  $R_C$  for maximum output swing and find out the small signal voltage gain ( $v_o / v_i$ ). (10%)
- (c) If the same circuit is used as a logic inverter, what is the limitation on choosing the value of  $R_C$ ? (5%)
- (d) Determine the value of  $R_C$  in order to obtain a  $NM_H$  of 2V in this inverter. (9%)

 


Fig. 3

4. For the common-base amplifier (Fig. 4(a))
- (a) What is the function of  $C_C$ ? (2%)
- (b) In some cases,  $R_L$  is large so that  $r_o$  can't be neglected. Find the input resistance  $R_{in}$  seen by the signal source in terms of  $r_e$ ,  $r_o$ , and  $R_L$ . (6%)
- (c) Discuss the effects of  $R_L$  on  $R_{in}$ . (2%)
- (d) For the Thévenin equivalent circuit (small signal only) "seen" by  $R_L$  (Fig 4.(b)), Find  $G_{vo}$  and  $R_{out}$ . (8%)

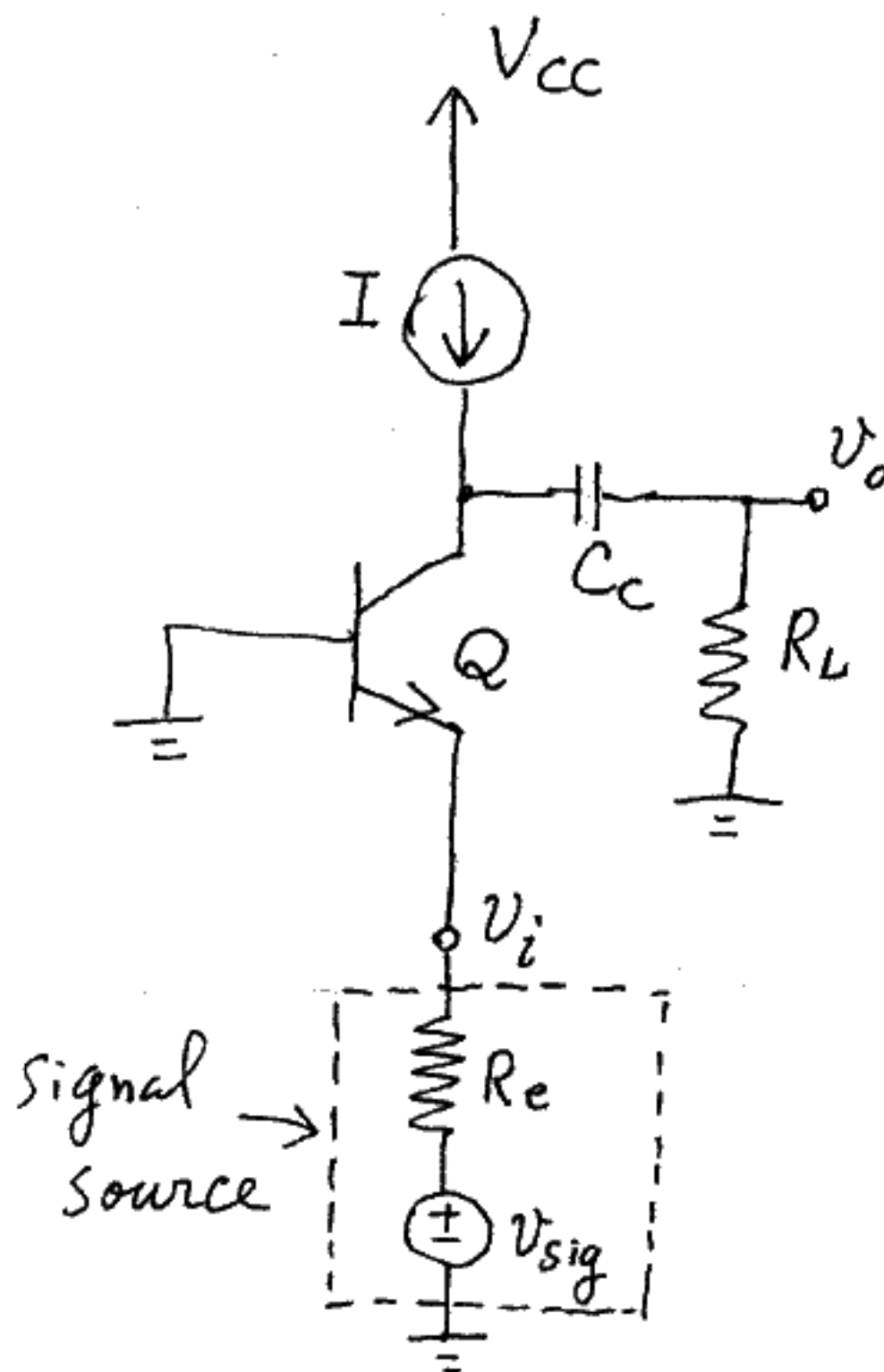


Fig. 4(a)

 


Fig. 4(b)

5. (a) With  $R_{B1} = \infty$ ,  $V_{cc}=3\text{ V}$ ,  $\beta=60$ , find  $R_c$  and  $R_{B2}$ , so that  $V_c \approx \frac{V_{cc}}{2}$ , and  $I_c=3\text{ mA}$ . (4%)
- (b) If  $\beta \rightarrow \infty$ , what then are  $I_c$  and  $V_c$ ? (3%)
- (c) To reduce the variations of dc current  $I_c$  voltage, we may connect an  $R_{B2}$  between the base and emitter of Q. Explain the beneficial effects of  $R_{B2}$ . (4%)

 


Fig. 5

6. Consider the CMOS common-source amplifier shown in Fig. xx. for the case:  $V_{DD} = 10\text{V}$ ,  $V_{tn} = |V_{tp}| = 1\text{V}$ ,  $\mu_n C_{ox} = 2\mu_p C_{ox} = 20\text{ }\mu\text{A/V}^2$ ,  $W = 100\text{ }\mu\text{m}$ ,  $L = 10\text{ }\mu\text{m}$ , and  $|V_A| = 100\text{V}$  for both the n and p devices, and  $I_{REF} = 100\text{ }\mu\text{A}$ . Find the small signal voltage gain  $v_o/v_i$  (using small signal analysis). (12%)

 


Fig. 6

7. In the CMOS inverter shown in Fig. 7(a),  $V_{DD} = 10\text{V}$ ,  $V_{tn} = |V_{tp}| = 1\text{V}$ ,  $\mu_n C_{ox} = 2\mu_p C_{ox} = 20\text{ }\mu\text{A/V}^2$ ,  $W = 100\text{ }\mu\text{m}$ ,  $L = 10\text{ }\mu\text{m}$ , and  $|V_A| = 100\text{V}$  for both the n and p devices.
- (a) The voltage transfer characteristic of the CMOS inverter is shown in Fig. 7(b). For point A, B, C, and D, give their  $v_i$  and  $v_o$ , respectively. (neglect the effect of  $|V_A|$ ) (8%)
- (b) Find the small signal voltage gain  $v_o/v_i$  (using small signal analysis). (10%)

 


Fig. 7(a)

 


Fig. 7(b)