

時間：2001/6/13 PM: 14:10~15:50

學號：_____

試題上請簽名並與答案卷一起繳回

姓名：_____

1. As shown in the Fig. 1 is the open-loop Bode plot of amplifier A. Curve 1 is uncompensated, while curve 2 is compensated by shunting a capacitor $C = 80$ pf between the input and output nodes of the mid-gain stage in amplifier A. This frequency compensation is called Miller compensation.

- (a) Compare the locations of the poles on curve 1 and 2. Explain what is pole splitting? And how the pole splitting benefits this compensation? (10%)
- (b) If the total capacitance seen at the input node of the mid-gain stage is 50 pf, find the voltage gain of the mid-gain stage. (10%)
- (c) If the closed-loop gain is fixed at 100 (40dB), locate the position of the lowest frequency pole in Hz (45° phase margin is needed). In this situation, find the capacitance should be placed across the mid-gain stage. (13%)

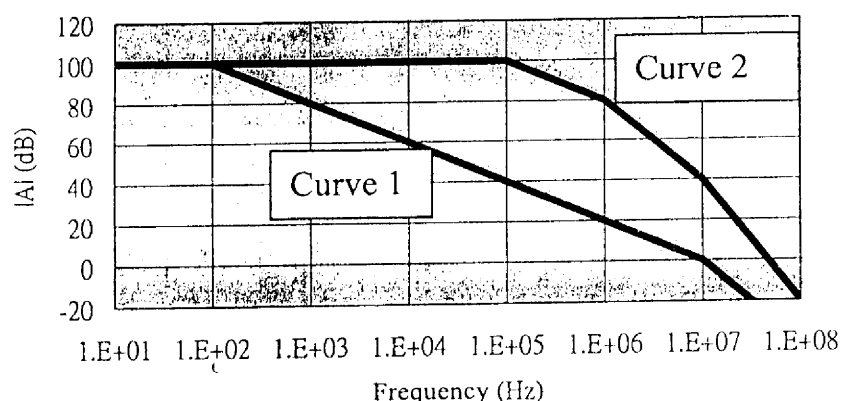


Fig. 1

2. For the class B output stage of Fig. 2, let $V_{CC}=6V$ and $R_L=4\Omega$. If the output is a sinusoid with 4.5-V peak amplitude, find (a) the output power; (b) the average power drawn from each supply; (c) the power efficiency obtained at this output voltage; (d) the peak current supplied by v_i , assuming that $\beta_N = \beta_P = 50$; (e) the maximum power that each transistor must be capable of dissipating safely. (25%).

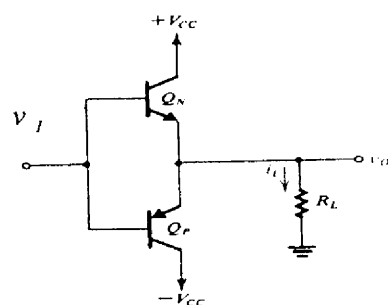


Fig. 2

3. It is required to use the LM380 to drive an $8-\Omega$ loudspeaker. Use the curves of Fig. 3 to determine the maximum power supply possible while limiting the maximum power dissipation to 2.9W. If for this application a 3% THD is allowed, find P_L and the peak-to-peak output voltage. (8%)

Shown in Fig. 4 is an operational amplifier. The differential inputs are at nodes 1 and 2. And the output is at node 9 with resistive load R_L .

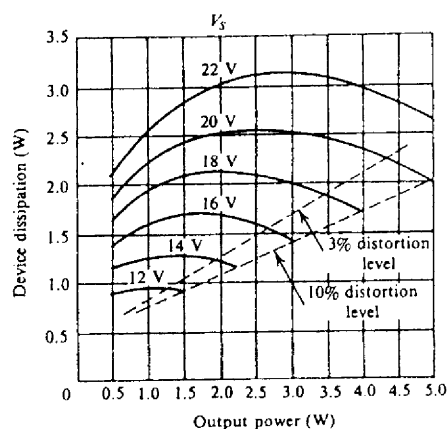


Fig. 3

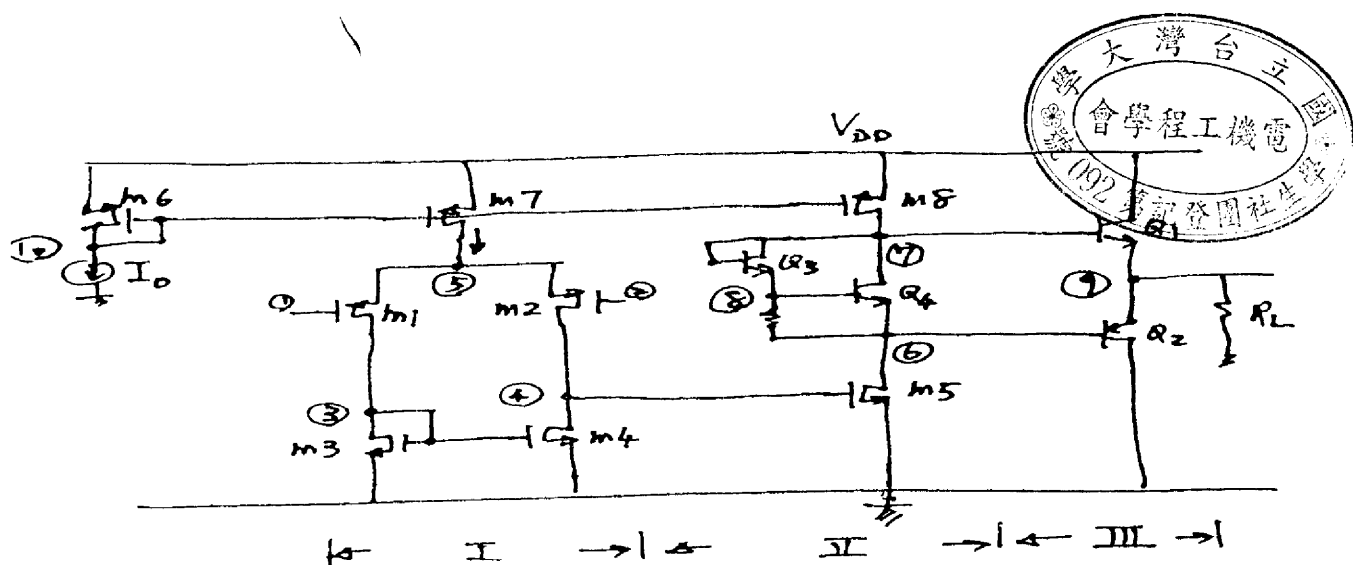


Fig. 4

4. A. Identify the transistors or the stages (I, II, and III) for the following configurations/functions: (a) DC biasing current, (b) differential to single conversion, (c) source coupled pair, (d) active load, (e) common source, (f) DC level shift. (3%)
 - Classify the stages (I, II, and III) in class A/B/AB/C. Justify your answers. (1%)
 - Which of the two input nodes 1 or 2 has the same polarity as the output node 9. (1%)
 - Give/Derive the (3%)
 - input maximum common mode voltage
 - input minimum common mode voltage
 - input common mode range (hint: subtraction of the above.)
 - output maximum voltage
 - output minimum voltage
 - input maximum swing (hint: subtraction of the above.)
5. A. Which stage major contributes the random offset? (1%)
 - Give/derive the random offset voltage in terms of threshold voltage V_T , device aspect ratio (W/L), and device over-drive ($V_{GS} - V_T$). (3%)
 - If the device aspect ratio (W/L) 7 of transistor m7 is twice that of device m6, what is the bias current in terms of I_0 in order to eliminate the systematic offset. (2%)
6. A. Give the CIRCUIT SCHEMATIC for small and AC signal analysis. (1 %)
 - Derive/Give the transconductance (G_m), output resistance (R_o) and voltage gain (a_v) of (a) stage I, (b) stage II, (c) stage III. (3%)
7. (a) Which nodes that give low frequency (dominant) poles before compensation? (1%)
 - Which nodes that yield high frequency (non-dominant) poles before compensation? (3%)
 - i. Give reasons why the op-amp requires a compensation. (3%)
 - which of the two nodes that compensation capacitor C_C can be connected. Justify your answer. (2%)
8. The parasitic capacitances should be considered for high frequency application.
 - Give the overall capacitances at nodes 4, 6 and 9. (1%)
 - In conjunction with the derived output resistances in III, give/derive expressions of
 - dominant pole, first non-dominant pole and zero after compensation. (2%)
 - op-amp transfer function given the derived a. (2%)
 - If one pole, which is the dominant pole, is assumed, give the transfer function of the op-amp. (2%)