

國立臺灣大學電機工程學系 89 年電子學（三）期中考試題

時間：2000/11/22 PM：6：30~8：30

學號：_____

試題上請簽名並與答案卷一起繳回

姓名：_____

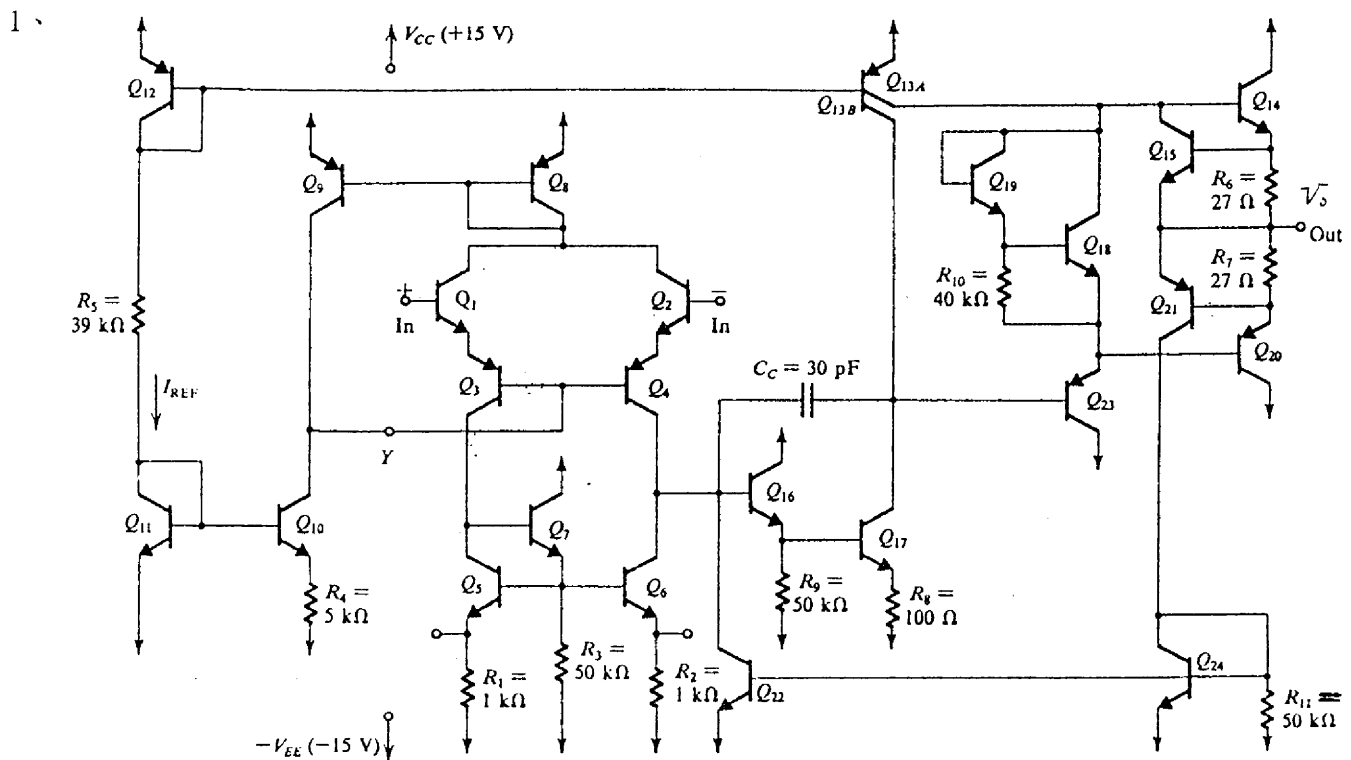


Fig. 1

(a). 簡答題 DC 操作時, Q_{15} , Q_{21} 的 I_c 偏壓電流為何? (2 pt)

假設有一大電流由 V_o 倒灌進來,

(b). 簡答題: 哪些電晶體與電阻會參與短路保護? (3 pt)

(c). 計算題: 寫出上述元件所對應之節點電流與電壓方程式, 註明由 V_o 倒灌進來的最大電流與流過各保護電晶體之電流/電壓關係 (4 pt)

(d). 簡答題: Q_3 - Q_4 如何防止 EBJ 崩潰? (2 pt)

What differential input voltage would result in the breakdown of the input-stage transistors? Assume V_{EBJ} breakdown at 7V for npn and 50 V for pnp transistor. (4 pt).

(e). 計算題: Neglect the voltage drops across R_1 and R_2 , and assume $V_{CC} = V_{EE} = 15$ V, calculate the input mode common range of the OP 741

(assume $V_{BE} \sim 0.6$ V, $V_{CE,sat} \sim 0.2$ V). (4 pt)

(f). 簡答題: Q_5 - Q_6 - Q_7 如何提供小信號時的 single-ended gain?

若表成 $i_o = x i_e$, $x = ?$ (3 pt)

(g). 計算題: (5 pt)

What is the output resistance of the first stage in Fig. 1?

(assume $I_{C4} = I_{C6} = 9.5 \mu A$, and $V_A = 125$ V for npn and 50 V for pnp)

2、計算題

 


Fig. 2

If the slew rate of an OP amplifier can be written as: $SR = aV\omega_p$,

(h). What are the constants of (a, V) for the case of 741-BJT and two-stage CMOS OP? (6 pt)

(i). From your study of Ch.10, which OP from (h) has the faster slew rate?

(assume both of them have the same ω_p) (2 pt)

3、For the two-stage CMOS OP AMP described in Sec. 10.7 and shown in Fig. 3:

 


Fig. 3

(a). What is the cause of "system offset"? (5pt)

(b). Explain how the performance will degrade when (i) a low-resistance load or (ii) a large capacitive load need to be driven. (8pt)

(c). A resistance R should be connected in series with the Miller compensation capacitance. Why? (5pt)

. For the cascode or folded cascode one-stage OP AMP : (Fig. 4-a-1, 4-a-2)

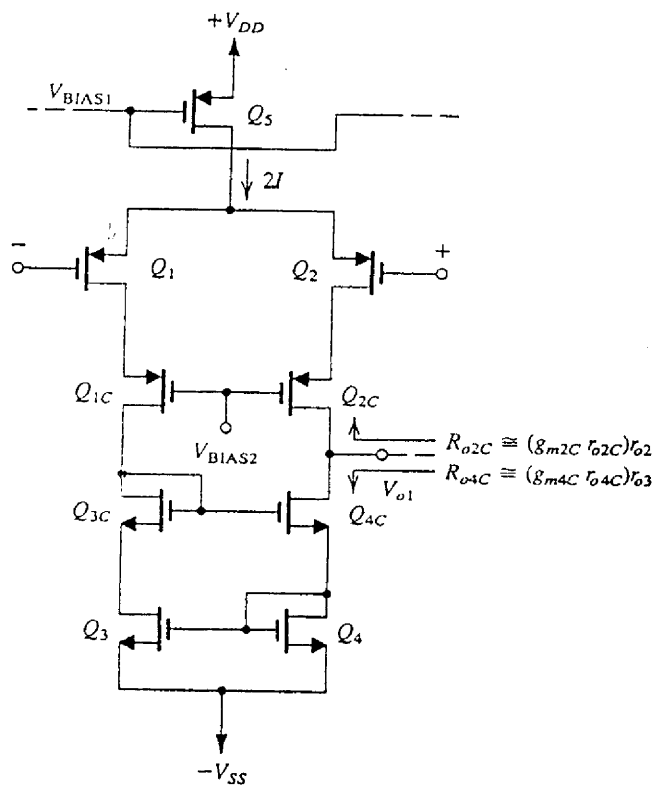


Fig. 4-a-1



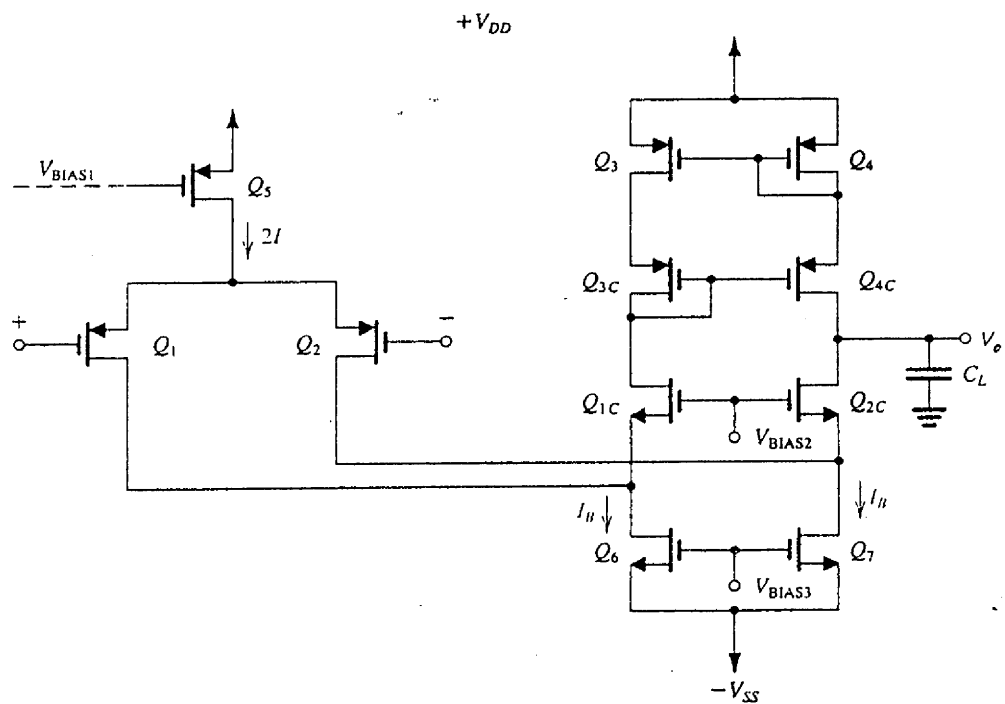


Fig. 4-a-2

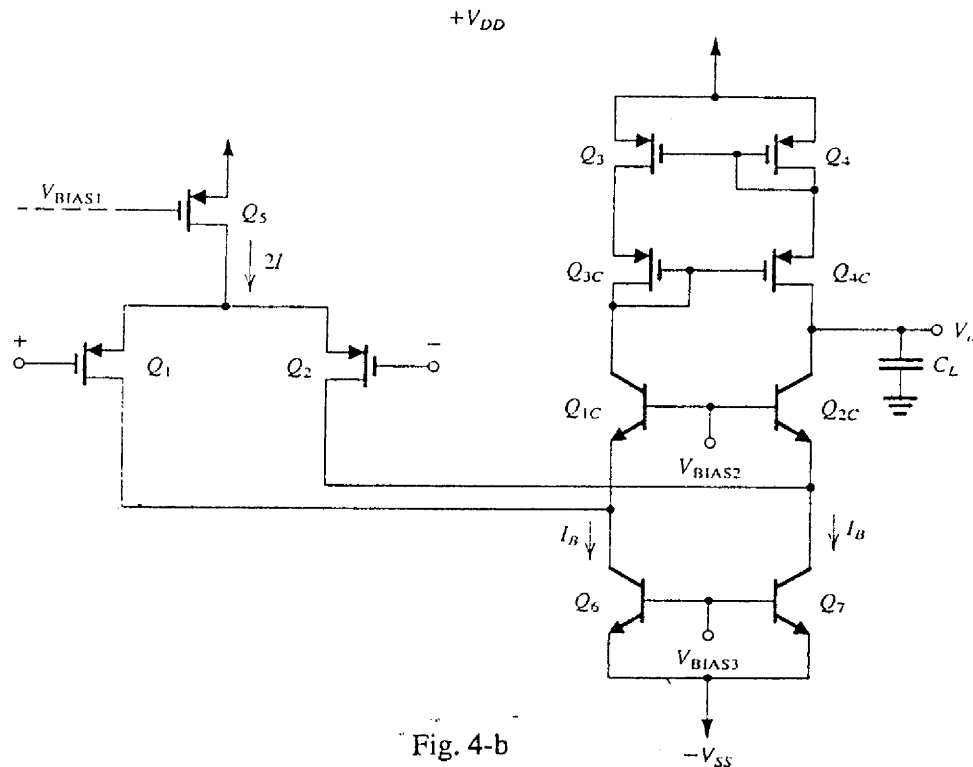- (a). What will happen to the amplifier characteristics when a large capacitive load is connected to the output? Make a comparison with the two stage design in Fig. 3. (6pt)



 (b). When BiCMOS process is available, it is advantageous to replace some of the MOSFETs with BJTs. Explain the reason. (Fig. 4-b)(6pt)



For the 4-bit DAC shown above, each of the current switches $S_0 \sim S_3$ is connected to the R_2R network or ground depending on whether a_i ($i=0 \sim 3$) is 1 or 0, respectively.

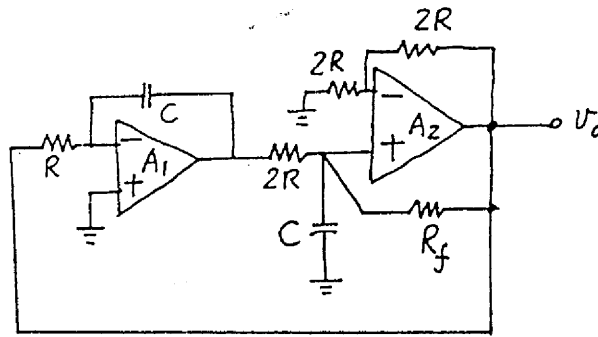


Fig. 6

For the quadrature oscillator shown above, assuming that A_1, A_2 are ideal OP AMPs.

- If $R_f = 2R/(1 + \epsilon)$, ϵ is a small positive number, show that the oscillation is sure to start. (5pt)
- Add some amplitude limiting circuit around A_1 so that the steady-state oscillation amplitude may be reached in a "softer" way. (5pt)

7.



 


Fig. 7

 Consider the circuit in Fig. 7 with $R_1 = 1\text{K}\Omega$ and $R_2 = 10\text{K}\Omega$. Find v_o and the voltage at the amplifier output for $v_i = +1\text{V}$, -10mV , and -1V . Assume the op amp to be ideal with saturation voltages of $\pm 12\text{V}$. The diodes have 0.7V voltage drops at 1mA , and the voltage drop changes by 0.1V per decade of current change. (10pt)



(a)

 

(b)

Fig. 8

The node in 555 timer at which the voltage is V_{TH} (that is, the inverting input terminal of comparator 1) is usually connected to an external terminal. This allows the use to change V_{TH} externally (that is, it no longer remains $2/3 V_{CC}$). Note, however, that whatever the value of V_{TH} becomes, V_{TL} always remains $1/2 V_{TH}$.

- For the astable circuit of Fig. 8, rederive the expressions for T_H and T_L , expressing them in terms of V_{TH} and V_{TL} . (5pt)
- For the case $C = 1 \text{ nF}$, $R_A = 7.2 \text{ K}\Omega$, $R_B = 3.6 \text{ K}\Omega$, and $V_{CC} = 5 \text{ V}$, find the frequency of oscillation and the duty cycle of the resulting square wave when no external voltage is applied to the terminal V_{TH} . (5pt)
- For the design in (b), let a Sine-wave signal of much lower frequency than that found in (b) and of 1-V peak amplitude be capacitively coupled to the circuit node V_{TH} . This signal will cause V_{TH} to change around its quiescent value of $2/3 V_{CC}$, and thus T_H will change correspondingly--a modulation process. Find T_H , find the frequency of oscillation and the duty cycle at the two extreme values of V_{TH} . (5pt)