

九十一年度台灣大學電資學院電機系電子學(一)期中考題

本試題共有三張，請同學檢查確認

1. Consider the circuit shown in fig. 1 for the case $R=10\text{ k}\Omega$. The power supply V^+ has a dc value of 10 V on which is superimposed a 60-Hz sinusoid of 1-V peak amplitude. (this "signal" component of the power supply voltage is an imperfection in the power-supply design. It is known as the **power-supply ripple**) Calculate both the dc voltage of the diode and the amplitude of the sine-wave signal appearing across it. Assume the diode to have a 0.7-V drop at 1-mA current and $n=2$. (6%)
2. A shunt regulator utilizes a zener diode whose voltage is 5.1 V at a current of 50mA and whose incremental resistance is 7Ω . The diode is fed from a supply of 15-V nominal voltage through a $200\text{-}\Omega$ resistor. What is the output voltage at no load ? Find the line regulation and the load regulation. (7%)
3. voltage doubler :

Consider the transition response of the voltage doubler shown in Fig.2(a). The input voltage $V_i(t)=V_p\sin(\omega t)$ is shown in Fig.2(b). Assuming no charge in C_1 and C_2 when $t=0$.

- (a) When $0 < t < T/4$, D1 is on or off ? D2 is on or off ? (2%)
- (b) What are the voltages across C_1 and C_2 when $t=T/4$? (1%)
- (c) When $T/4 < t < 5T/12$, D1 is on or off ? D2 is on or off ? (2%)
- (d) When $5T/12 < t < 3T/4$, D1 is on or off ? D2 is on or off ? (2%)
- (e) What are the voltages across C_1 and C_2 when $t=3T/4$? (1%)
- (f) When $3T/4 < t < 11T/12$, D1 is on or off ? D2 is on or off ? (2%)
- (g) When $11T/12 < t < 5T/4$, D1 is on or off ? D2 is on or off ? (2%)
- (h) What is the voltage across C_2 when $t=5T/4$? (3%)
- (i) What is the voltage across C_2 when $t=9T/4$? (3%)
- (j) What is the voltage across C_2 when $t \rightarrow \infty$? (2%)

 


Fig. 1

 


Fig. 2(a)

 


Fig. 2(b)

4. An OPAMP circuit is shown in Fig. 3 , the OPAMP is an ideal OPAMP. Find v_o and I_2 . (18%)

 


Fig. 3

5. For an OPAMP inverting amplifier, the slew rate is SR and the maximum amplitude of the output voltage is V_{OMAX} . Find the full-power bandwidth. (8%)
6. The circuit shown in Fig. 4 uses four diodes. $V_T = 25\text{mV}$. These diodes have identical junction ideality factors, $n = 2$. Their saturation currents have the following relation. $I_{S1} : I_{S2} : I_{S3} : I_{S4} = 1 : 2 : 4 : 8$. Find V. (7%)

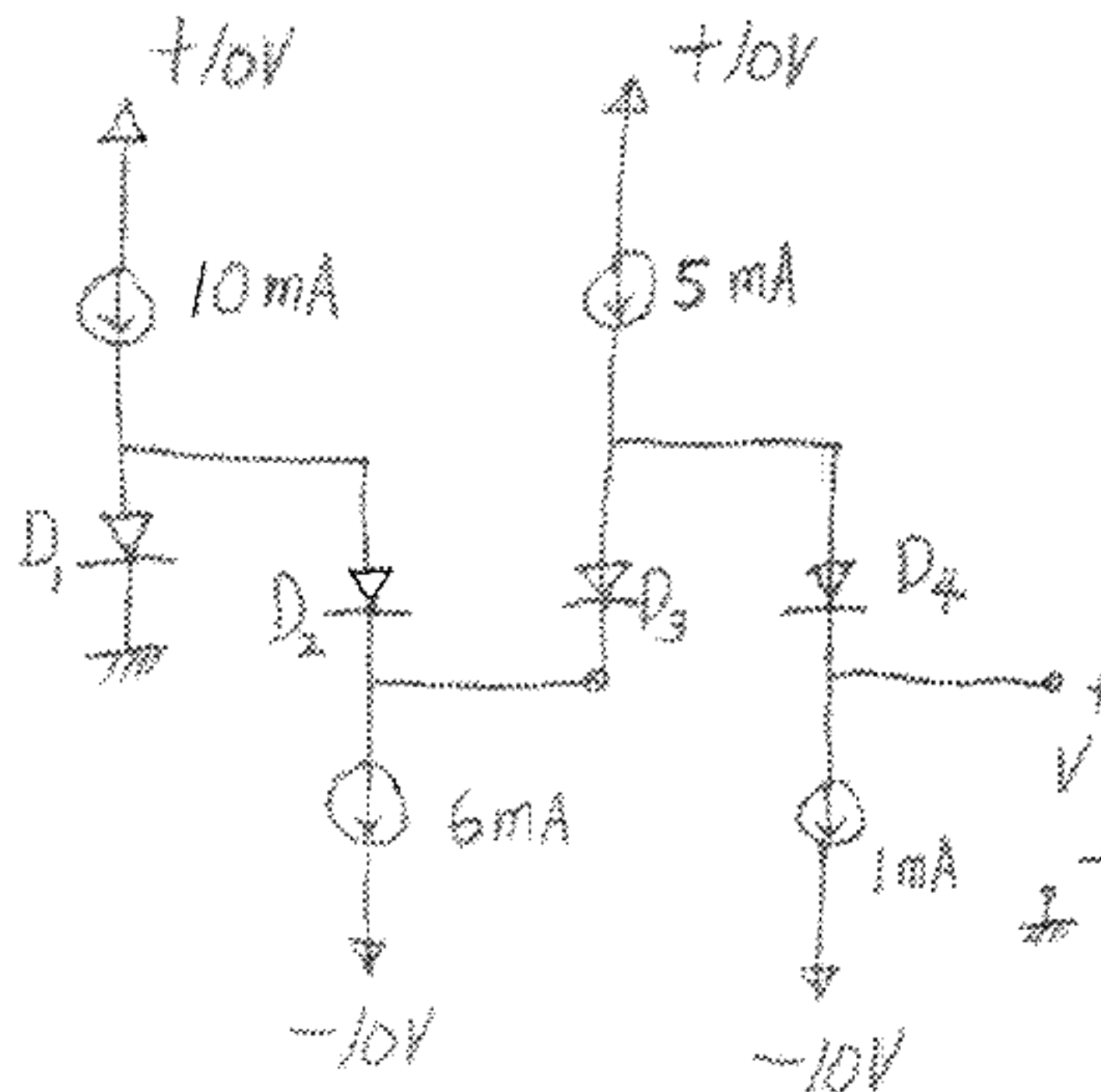


Fig. 4

7. Assuming that the op amp is ideal and the diode current can be expressed as $I_D = I_S e^{V_D/V_T}$,

analyze the following circuits:

- (1) Derive the expression for the output voltage v_O in Fig. 5(a) for a positive v_I . (5 %)
- (2) Derive the expression for the output voltage v_O in Fig. 5(b) for a negative v_I . (5 %)
- (3) With the expressions derived above, what is the output voltage v_O in Fig. 5(c) for positive v_1 and v_2 ? (10 %)

 


Fig. 5(a)

 


Fig. 5(b)

 


Fig. 5(c)

8. Consider the circuit in Fig. 6 for $R_1=10\text{K}\Omega$, $R_2=10\text{K}\Omega$, $R_3=1\text{K}\Omega$, $I_{EE}=11\text{mA}$, $\beta(\text{nnp})=50$ and $\beta(\text{pnp})=10$. Assuming the transistors are in forward active region and the forward bias at emitter-base junction is 0.7V for both *nnp* and *pnp*, find the voltage V_A (4 %), V_B (3 %), V_C (3 %) and V_D (4 %).

(Hint: collector current of *nnp* =
base current of *pnp* + current of R_1)

 


Fig. 6