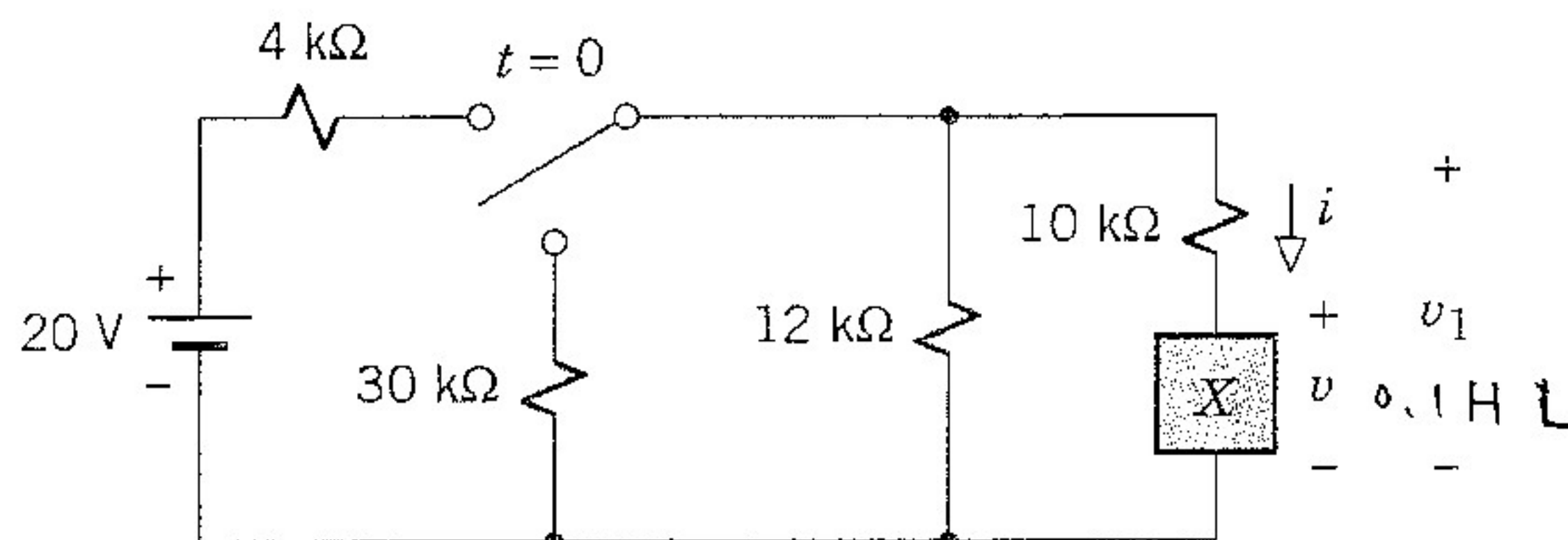
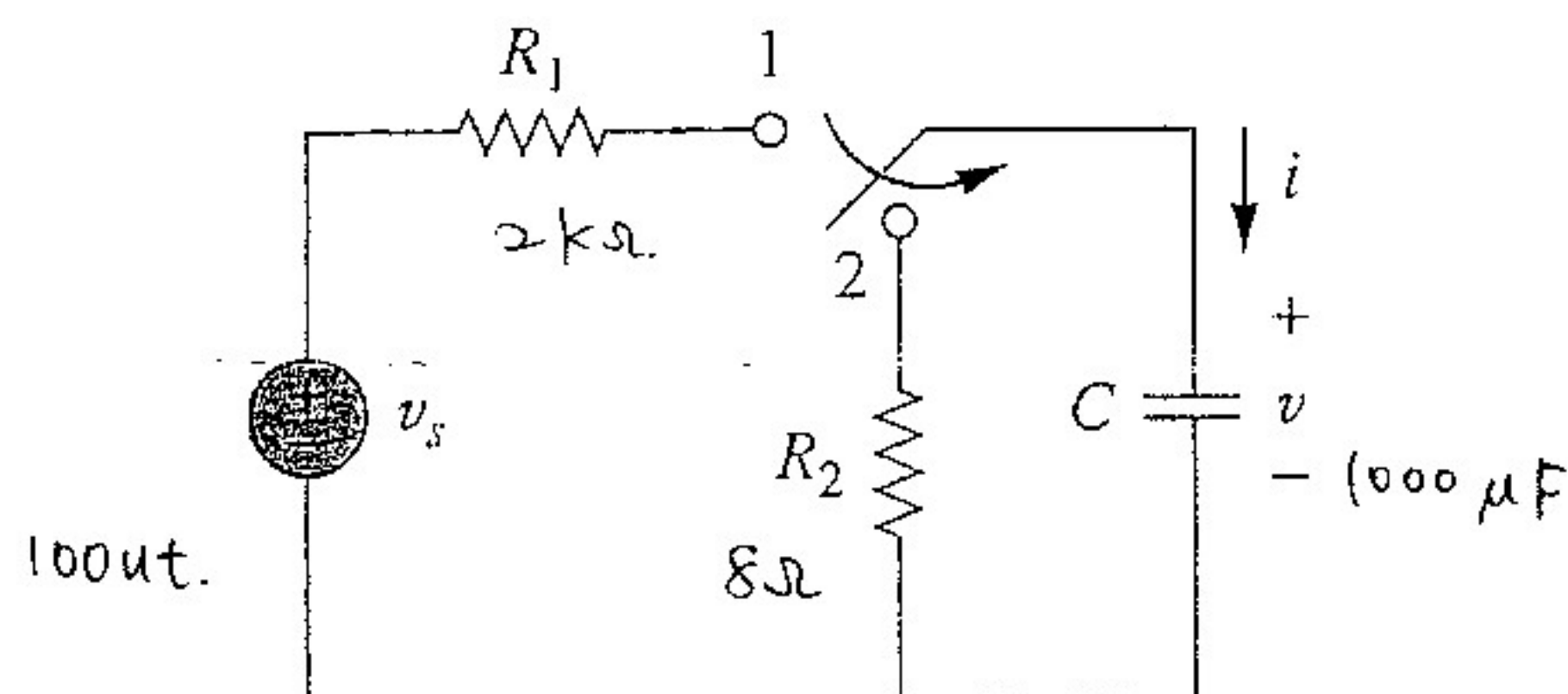


1. In the circuit below, the switch has been in the lower position a long time before $t = 0$. At $t = 0$, it is switched to the upper position. Find $i(t)$ and $v_1(t)$ for $t > 0$, if element X is a 0.1-H inductor. (30%)



2. The following circuit is used for a flash lamp with $R_1 = 2\text{ k}\Omega$, $C = 1000\text{ }\mu\text{F}$, $v_s = 100u(t)\text{ V}$, and the lamp resistance $R_2 = 8\text{ }\Omega$. If the circuit is switched to position 2 at $t = 20\text{ s}$ to discharge, plot the capacitor voltage $v(t)$ versus time and calculate the peak charging and discharging currents i , respectively. (30%)



3. For the following circuit,
- (1) derive the differential equation for i , and (10%)
 - (2) find its complete response for $t > 0$. (20%)
 - (3) What value should the 0.5 kΩ resistor become in order to achieve critical damping condition? (10%)

