

# 九十一學年度台灣大學電機系電子學(一)期末考題

\*本試題共有四張，請同學檢查確認\*

1. Consider the CMOS common-source amplifier in Fig. 1 for the case:  $V_{DD} = 10\text{ V}$ ,

$|V_{tn}| = |V_{tp}| = 1\text{ V}$ ,  $\mu_n C_{ox} = 2\mu_p C_{ox} = 20\mu\text{A}/\text{V}^2$ ,  $W = 100\mu\text{m}$ ,  $L = 10\mu\text{m}$  and

$|V_A| = 100\text{ V}$  for both the n and p devices, and  $I_{REF} = 100\mu\text{A}$ .

- Find the ac small signal voltage gain by small signal analysis. (5%)
- Sketch the transfer characteristics ( $v_O$  vs.  $v_I$ ) of this amplifier. (5%)
- Find the coordinates of the extremities of the amplifier region of the transfer characteristics. (8%)

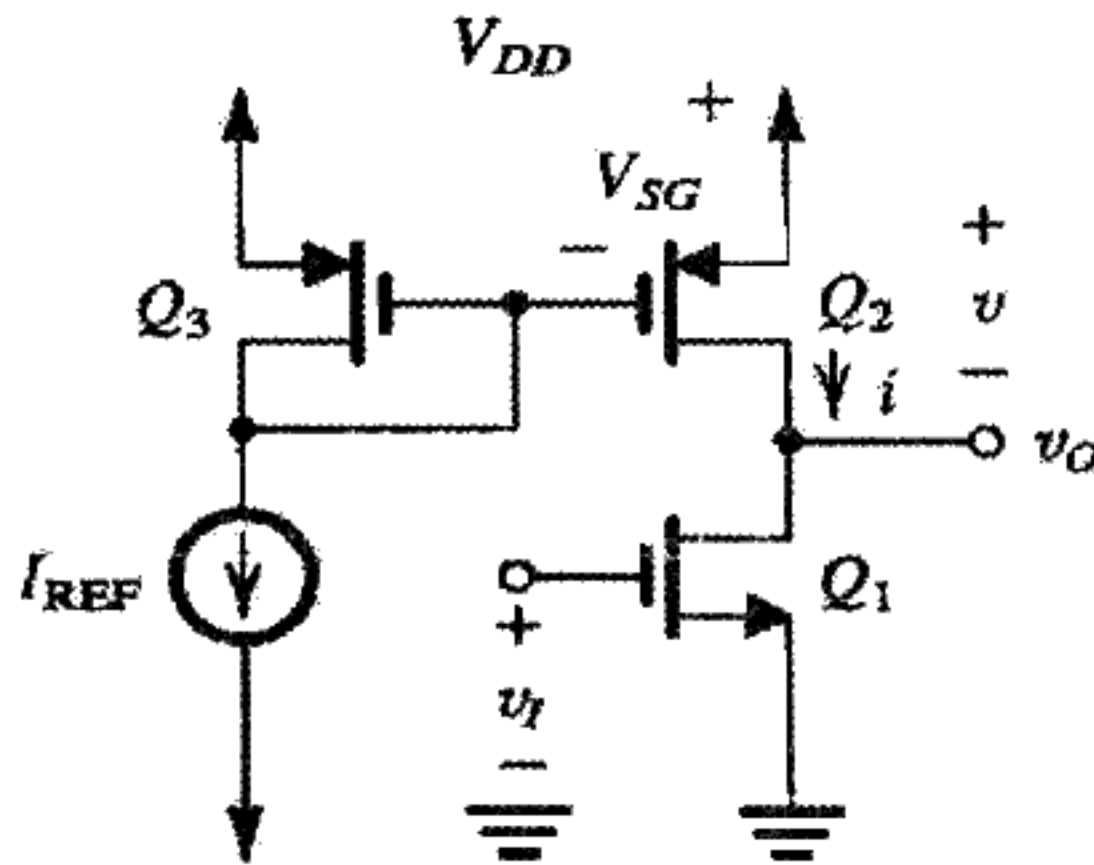


Fig. 1

- For the source follower in Fig.2(a), find the open-circuit voltage gain  $v_{O1}/v_I$  and the output resistance  $R_{O1}$ , in terms of  $g_{m1}$  and  $X$ . Neglect the effect of  $r_{o1}$  and that of the output resistance of the bias current source. (5%)
- For the common-gate amplifier in Fig.2(b), find the voltage gain  $v_O/v_{I2}$  and the input resistance  $R_i$ , in terms of  $g_{m1}$ ,  $X$ , and  $R$ . Neglect the effect of  $r_{o2}$  and that of the output resistance of the bias current source. (5%)
- If the output terminal of the source follower in (a) is connected to the input terminal of the common-gate amplifier in (b), find the overall voltage gain  $v_O/v_I$  of the cascaded amplifier. (5%)

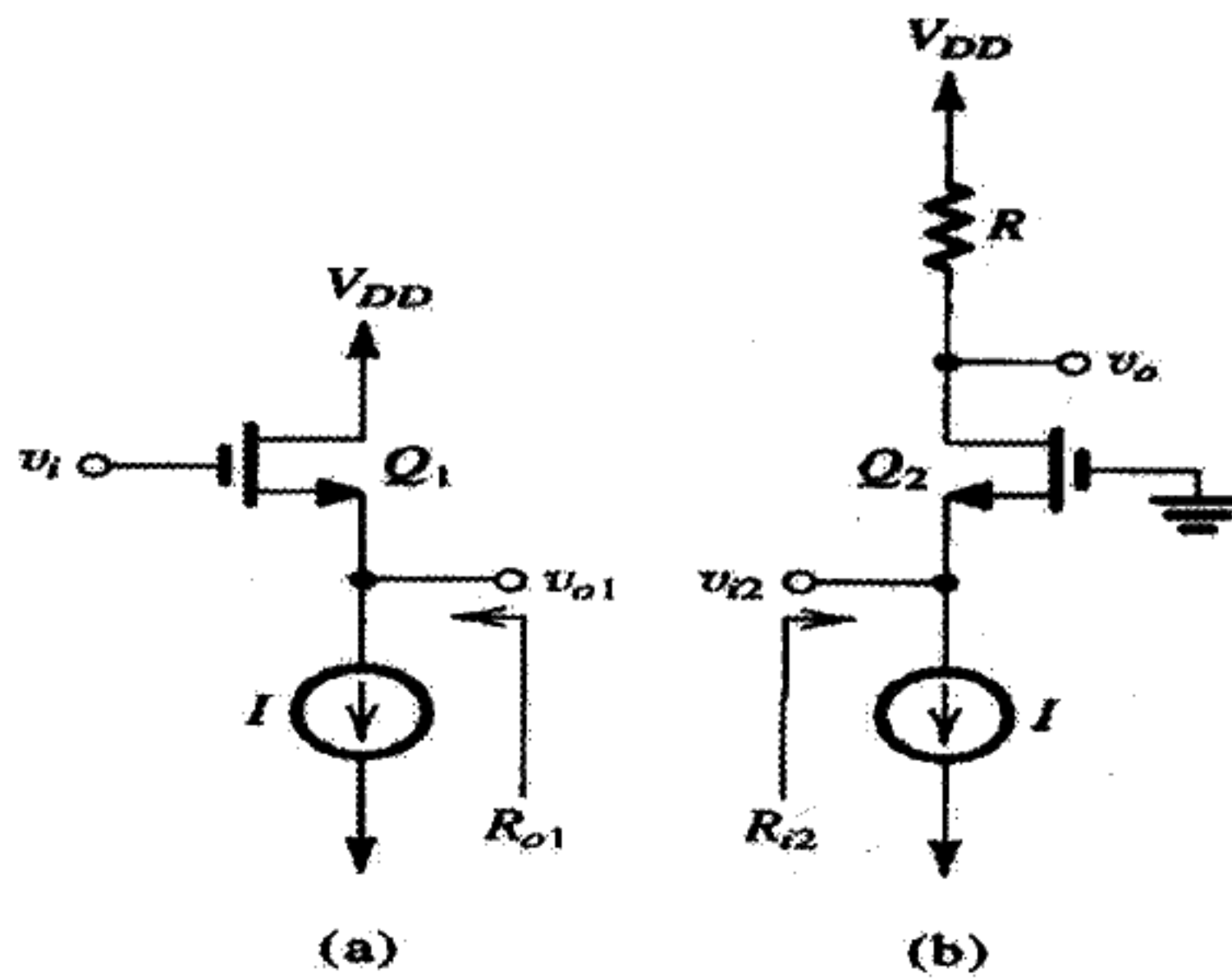


Fig.2

3. For the circuit shown in Fig.3, find the values of the labeled node voltages for:

(a)  $\beta = \infty$  (7%)

(b)  $\beta = 100$  (7%)

(For pnp BJT  $V_{EB}=0.7V$ ; and for npn BJT  $V_{BE}=0.7V$ )

 


Fig.3

4. The BJT in the circuit of Fig.4 has  $\beta = 100$ ,  $V_{BE}=0.7V$ , and  $V_T=25mV$ .

(a) Find the dc collector current and the dc voltage at the collector. (8%)

(b) Replacing the transistor by its T model, draw the small-signal equivalent circuit of the amplifier. Analyze the resulting circuit to determine the voltage gain  $v_o/v_i$

(12%)

 


Fig.4

5. Assuming that all the BJT transistors are identical with  $\beta=100$ ,  $V_{BE,on}=0.7\text{V}$ ,  $V_A=200\text{V}$  and  $V_T=25\text{mV}$ , solve the differential pair problems using the values in the following table.

$R_C$	$10\text{K}\Omega$	$R_L$	$10\text{K}\Omega$	$R_E$	$500\Omega$
$R_O$	$50\text{K}\Omega$	$I_{EE}$	$2\text{mA}$	$R$	$12.88\text{K}\Omega$

- (1) Find the DC bias ( $V_{C1}$ ,  $V_{E1}$ ,  $V_X$  and  $I_{C1}$ ) for the differential pair in Fig. 5(a). (4%)
- (2) Find differential-mode gain  $A_d = v_o/v_d$  (3%), common-mode gain  $A_{cm}$  (3%) and CMRR (in dB) (1%) using the differential pair in Fig. 5(a).
- (3) From above derivation, we can find that the  $A_d$  decreases as  $R_C$  increases. What is the maximum  $R_C$  value can be used to operate the differential pair as an amplifier? (2%) What is the CMRR in dB if the maximum  $R_C$  is used? (1%)
- (4) If the current source is replaced by a current mirror as shown in Fig. 5(b), find the CMRR (in dB). (5%) [Hint:  $V_A$  is large  $\rightarrow$  Early Effect can be neglected in calculating dc current.]
- (5) What is the maximum and minimum input common-mode voltage (DC voltage) allowed in the differential pair? (5%)

 


Fig. 5(a)

 


Fig. 5(b)

6. By applying the control voltage at the gate properly, the NMOS and PMOS can be used as a switch. Given that  $V_{tn}=1\text{V}$ ,  $V_{tp}=-2\text{V}$ ,  $V_C(\text{high})=5\text{V}$  and  $V_C(\text{low})=-5\text{V}$ , find:
- (1) the allowable range of the input voltage in Fig. 6(a). (3%)
  - (2) the allowable range of the input voltage in Fig. 6(b). (3%)
  - (3) the allowable range of the input voltage in Fig. 6(c). (3%)

 


Fig. 6(a)

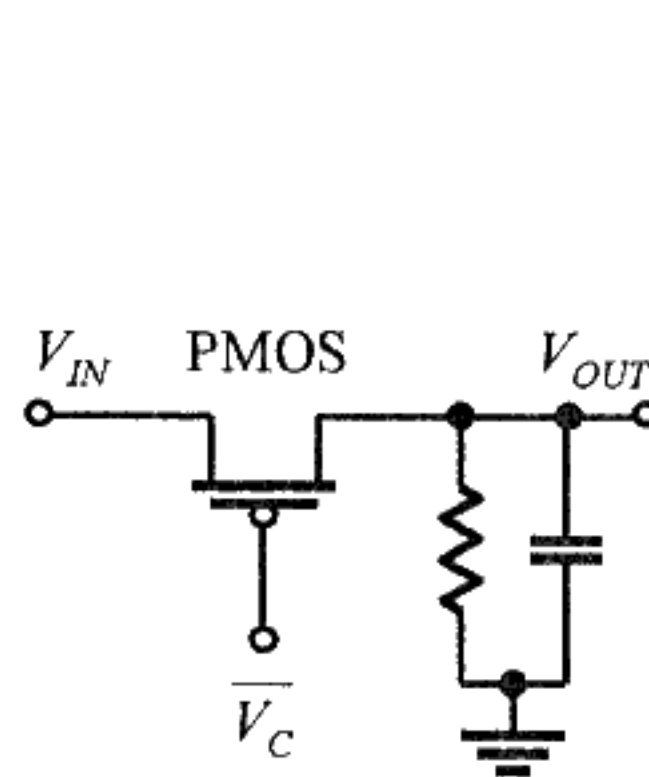


Fig. 6(b)

 


Fig. 6(c)