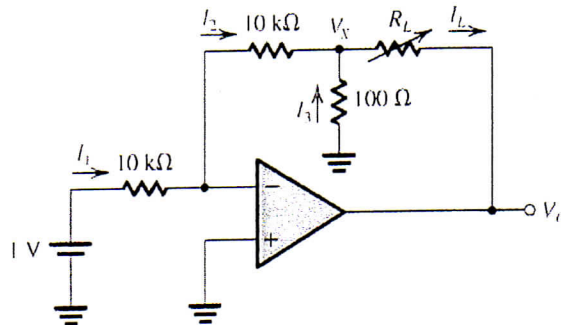


Microelectronic Circuits I (Quiz 1)

date: 2010/10/22 (Fri)

time: 14:20~15:10

1. (50%) The circuit shown below utilizes an ideal op amp.
 - (a) Find I_1 , I_2 , I_3 , and V_x .
 - (b) If V_O is not to be lower than -13V , find the maximum allowed value for R_L .
 - (c) If R_L is varied in the range 100Ω to $1\text{k}\Omega$, what is the corresponding change in I_L and in V_O ?



2. (50%) The circuit shown below is intended to supply a voltage to floating loads (those for which both terminals are ungrounded) while making greatest possible use of the available power supply.
 - (a) Assuming ideal op amps, sketch the voltage waveforms at nodes B and C for a 1-V peak-to-peak sine wave applied at A. Also sketch v_O .
 - (b) What is the voltage gain v_O/v_I ?
 - (c) Assuming that the op amps operate from $\pm 15\text{-V}$ power supplies and that their output saturates at $\pm 14\text{V}$, what is the largest sine-wave output that can be accommodated? Specify both its peak-to-peak and rms values.

