


Switching Circuits and Logic Design

Midterm Examination

15:30 ~ 17:20, November 13, 2009

1. (8%) Convert $(\frac{25}{3})_7$ to base 9. Truncate the final answer. Do all of the arithmetic in decimal with accuracy to 2 decimal places (just ignore the 3rd decimal place).

 2. (15%) In this problem, given the following circuit of input X, Y, and Z:



- (a) (7%) Find the minimum sum of product expression for output F .
- (b) (8%) Draw a circuit of input X, Y, Z to realize F by using two OR gates, two AND gates, and one inverter only. All of gates should have two inputs except the inverter. Note: There are three possible solutions. You just need to write ONE solution.

3. (15%) Simplify the Boolean expression using the consensus theorem and/or other theorems.

$$(a' + c' + d)(b + c' + d)(a + b + d)(a' + b + c)(a' + b + d)(a + b' + c + d')(a + b + c + d')$$

4. (22%) For the Boolean expression:

$$f(a, b, c, d) = \sum m(0, 2, 5, 8, 9, 12, 13) + \sum d(10, 11, 14)$$

(Assume that a is the most significant bit and d is the least significant bit. That means, $a'b'c'd = m_1$.)

- (a) (10%) Find the minimum sum-of-product expression with Karnaugh Map. Please also indicate which terms are essential prime implicants.
- (b) (12%) Derive the two-level minimum NAND-NAND, NOR-OR, OR-NAND circuits of $f(a, b, c, d)$.

5. (15%)

(a) (12%) Find a minimum two-level, multiple-output OR-AND circuit to realize

$$f_1(a,b,c,d) = \overline{b}d' + a'd + cd'$$


$$f_2(a,b,c,d) = b'c' + \overline{b'd} + \overline{a'b}$$

$$f_3(a,b,c,d) = \overline{a'b} + \overline{bd'} + \overline{b'd}$$

(b) (3%) Realize the same function with a minimum two-level NOR-NOR circuit.

 6. (15%)

For the circuit given below, assume all the gates have propagation delay 1 ns.



(a) (5%) Fill in the following chart with the 9 values corresponding to the $\{0,1,\times\}$ three-valued simulation of a 2-input NAND gate, where “ \times ” denotes an unknown value.

NAND	0	1	\times
0			
1		o	\times
\times		\times	\times

(b) (5%) Complete the following truth table of function Z in terms of input variables A , B , and C .


(Suggestion: Don't panic! Whenever you are not sure about the value of a wire, treat it as an unknown. Three-valued simulation may help you understand the circuit.)

ABC	Z
000	0
001	1
010	0
011	1
100	0
101	0
110	0
111	1

- (c) (2%) Can a static 1-hazard happen in Z ? If yes, under what condition (that is, fixing A, B, C to certain values for enough time and then switching one of the inputs to its opposite value) can it happen?

(Suggestion: K-map based analysis does not work here because it's a multi-level circuit. However, the mechanism for a static 1-hazard to happen here is similar to that in a two-level circuit.)

 - (d) (3%) Complete the following timing diagram (from 3ns to 7ns). (Assume $A = W = X = 1$ and $B = C = Y = Z = 0$ initially.)




7. (10%)

Let Boolean function $f(A,B,C,D) = A'D' + A'C + AB' + AC'D$, whose K-map is shown below for your reference.

AB \ CD	00	01	11	10
00	1	1		1
01			1	1
11	1	1		1
10	1	1		1

 - (a) (8%) Implement f using a 4-to-1 MUX and 2-input AND/OR gates.
 (Let variables A and B be the control variables of the MUX. Assume a variable and its complement are available as inputs.)
- (b) (2%) Suppose f is implemented with two function generators g and h connected as shown below. Determine the functions of $g(A,B,H)$ and $h(C,D)$.
 (There can be multiple solutions; however, showing one is enough.)



$(c+d')$
 $c'd$
 cd'