

姓名：_____
學號：_____

注意事項：1. 題目卷、答案卷，皆要填寫考生姓名與學號；

2. 考試完畢，請將題目卷、答案卷一併繳回，未繳回者，不予計分；

1. (22%) Fig. 1 is a MOS cascode amplifier. Assume that two transistors, Q_1 and Q_2 , have the same g_m and r_o .
- (1) Find A_{v1} , A_{v2} , R_{in2} and R_o , where $A_{v1} = v_{o1}/v_i$ and $A_{v2} = v_o/v_{o1}$. (12%)
- (2) If $R_L = 2r_o$, find A_{v1} and R_{in2} . (6%)
- (3) Explain how to select R_L so that A_{v1} can be comparable with the intrinsic gain of Q_1 (in the same order of magnitude). (4%)

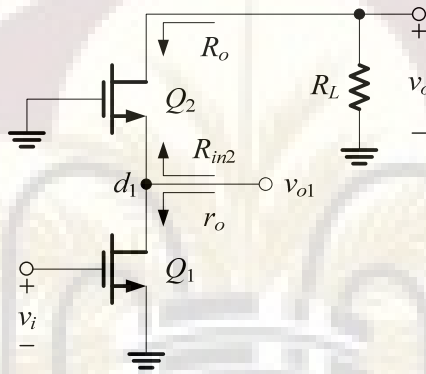


Fig. 1

(Solution)

- (1) Find A_{v1} , A_{v2} , R_{in2} and R_o , where $A_{v1} = v_{o1}/v_i$ and $A_{v2} = v_o/v_{o1}$. (12%)

Answer:

$$A_v = A_{v1}A_{v2} = -g_{m1}(g_{m2}r_{o2}r_{o1} // R_L) = -g_{m1}(g_{m2}r_{o2}r_o // R_L), \text{ where } r_o = r_{o1}$$

$$A_{v1} = \frac{v_{o1}}{v_i} = -g_{m1}(r_{o1} // R_{in2}) = -g_{m1}(r_o // R_{in2})$$

$$A_{v2} = \frac{A_v}{A_{v1}} = \frac{g_{m2}r_{o2}r_{o1} // R_L}{r_{o1} // R_{in2}} = \frac{g_{m2}r_{o2}r_{o1} // R_L}{r_{o1} // \left(\frac{R_L + r_{o2}}{1 + g_{m2}r_{o2}} \right)} = \frac{\frac{1}{r_{o1}} + \frac{1 + g_{m2}r_{o2}}{R_L + r_{o2}}}{\frac{1}{g_{m2}r_{o2}r_{o1}} + \frac{1}{R_L}} = \frac{(R_L + r_{o2}) + (1 + g_{m2}r_{o2})r_{o1}}{r_{o1}(R_L + r_{o2})} \cdot \frac{R_L + g_{m2}r_{o2}r_{o1}}{g_{m2}r_{o2}r_{o1}R_L}$$

$$\rightarrow A_{v2} = \frac{(R_L + r_{o2}) + (1 + g_{m2}r_{o2})r_{o1}}{r_{o1}(R_L + r_{o2})} \cdot \frac{g_{m2}r_{o2}r_{o1}R_L}{R_L + g_{m2}r_{o2}r_{o1}} = \frac{(R_L + r_{o2}) + (1 + g_{m2}r_{o2})r_{o1}}{R_L + r_{o2}} \cdot \frac{g_{m2}r_{o2}R_L}{R_L + g_{m2}r_{o2}r_{o1}} \quad \because g_{m2}r_{o2}r_{o1} \gg r_{o1}$$

$$\rightarrow A_{v2} \approx \frac{R_L + r_{o2} + g_{m2}r_{o2}r_{o1}}{R_L + r_{o2}} \cdot \frac{g_{m2}r_{o2}R_L}{R_L + g_{m2}r_{o2}r_{o1}} \bigg|_{g_{m2}r_{o2}r_{o1} \gg r_{o2}} \approx \frac{R_L + g_{m2}r_{o2}r_{o1}}{R_L + r_{o2}} \cdot \frac{g_{m2}r_{o2}R_L}{R_L + g_{m2}r_{o2}r_{o1}} = \frac{g_{m2}r_{o2}R_L}{R_L + r_{o2}}$$

$$\rightarrow A_{v2} = g_{m2}(r_{o2} // R_L)$$

$$R_{in2} = \frac{R_L + r_{o2}}{1 + g_{m2}r_{o2}}$$

$$R_o = r_{o2} + (1 + g_{m2}r_{o2})r_{o1} \approx g_{m2}r_{o2}r_{o1} = g_{m2}r_{o2}r_o$$

(2) If $R_L = 2r_o$, find A_{v1} and R_{in2} . (6%)

Answer:

$$A_{v1} = \frac{v_{o1}}{v_i} = -g_{m1}(r_o // R_{in2}) = -g_{m1} \frac{r_o R_{in2}}{r_o + R_{in2}} = -g_{m1} \frac{r_o \frac{3r_o}{1+g_{m2}r_o}}{r_o + \frac{3r_o}{1+g_{m2}r_o}} = -g_{m1} \frac{\frac{3r_o}{1+g_{m2}r_o}}{1 + \frac{3}{1+g_{m2}r_o}}$$

$$\rightarrow A_{v1} = -g_{m1} \left(\frac{3r_o}{4 + g_{m2}r_o} \right)$$

$$R_{in2} = \left. \frac{R_L + r_{o2}}{1 + g_{m2}r_{o2}} \right|_{R_L=2r_o} = \frac{3r_o}{1 + g_{m2}r_o}$$

(3) Explain how to select R_L so that A_{v1} can be comparable with the intrinsic gain of Q_1 (in the same order of magnitude). (4%)

Answer:

$$A_{v1} = \frac{v_{o1}}{v_i} = -g_{m1}(r_{o1} // R_{in2}) = -g_{m1}(r_o // R_{in2}) = -g_{m1} \left(r_o // \frac{R_L + r_{o2}}{1 + g_{m2}r_{o2}} \right) \dots (1)$$

Intrinsic gain of Q_1 ,

$$A_{v1}' = -g_{m1}(r_o // R_L) \dots (2)$$

Let (1) = (2),

$$r_o // \frac{R_L + r_{o2}}{1 + g_{m2}r_{o2}} = r_o // R_L \rightarrow \frac{1}{r_o} + \frac{1 + g_{m2}r_{o2}}{R_L + r_{o2}} = \frac{1}{r_o} + \frac{1}{R_L} \rightarrow \frac{1 + g_{m2}r_{o2}}{R_L + r_{o2}} = \frac{1}{R_L}$$

$$\rightarrow R_L(1 + g_{m2}r_{o2}) = R_L + r_{o2} \rightarrow g_{m2}r_{o2}R_L = r_{o2} \rightarrow R_L = \frac{1}{g_{m2}}$$

2. Fig. 2 shows a MOS Wilson current source. Assume the transistors have identical parameters.

(1) Find the output resistance in terms of g_m and r_o of the transistors. (10%)

(2) The V_{DS} of Q_2 is higher than that of Q_1 , which results in difference between I_{REF} and I_O . If

$V_{GS3} = V_{GS2} = V_{GS1}$ and $V_A = 20 V_{GS1}$, find I_O/I_{REF} . (8%)

(Hint: $I_D = (1/2)k_n'(W/L)(V_{GS}-V_t)^2(1+V_{DS}/V_A)$)

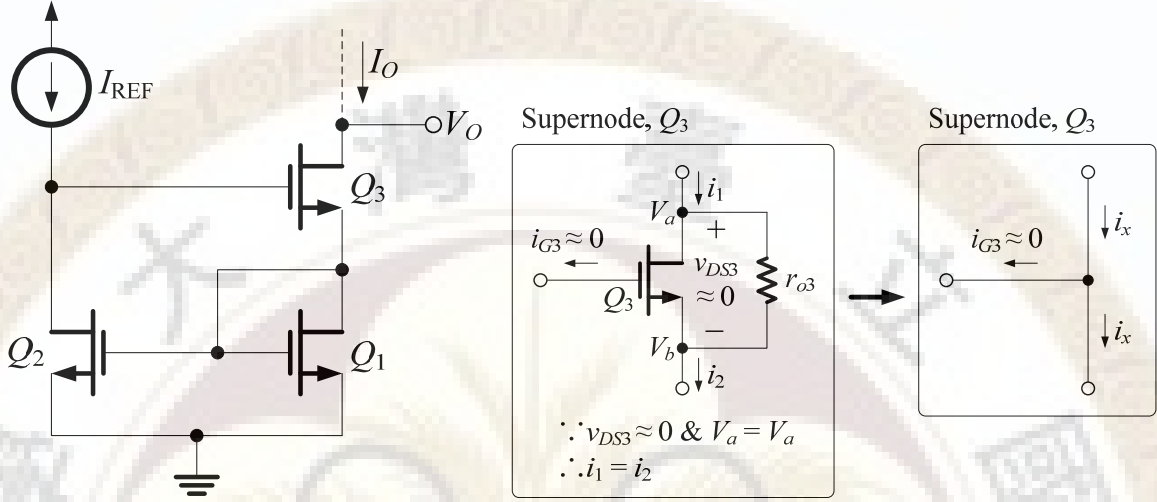


Fig. 2

(Solution)

(1) Find the output resistance in terms of g_m and r_o of the transistors. (10%)

Answer:

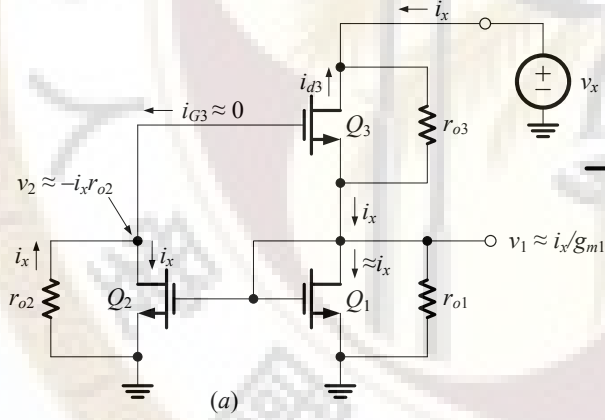


Fig. 2(1.1)

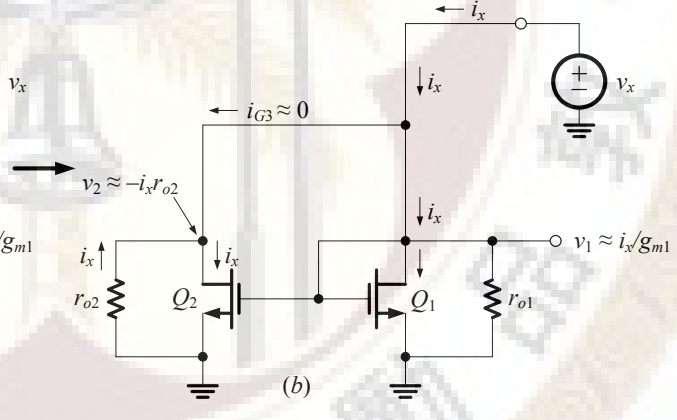


Fig. 2(1.2)

where: the small-signal equivalent circuit of Q_3 is shown in Fig. 2(1.2).

Note: The test takers do not need to plot the circuit shown in Fig. 2(1.1) and Fig. 2(1.2). They are illustrated to help understand the process of finding the answers.


$$i_{d3} = g_{m3}v_{gs3} = g_{m3}(v_{g3} - v_{s3}) = g_{m3}\left(-i_x r_{o2} - \frac{i_x}{g_{m1}}\right) = -i_x g_{m3}\left(r_{o2} + \frac{1}{g_{m1}}\right) \approx -(g_{m3}r_{o2})i_x$$

$$v_x = -i_{d3}r_{o3} + v_1 = g_{m3}r_{o2}r_{o3}i_x + \frac{i_x}{g_{m1}} = \left(g_{m3}r_{o2}r_{o3} + \frac{1}{g_{m1}}\right)i_x \approx g_{m3}r_{o2}r_{o3}i_x$$

$$R_o = \frac{v_x}{i_x} = (g_{m3}r_{o2})r_{o3}$$


直觀解法：因為 Q_1 為 diode connect 電路，因此，在求該電路之小訊號輸出阻抗為目的時， Q_1 並不會參與阻抗轉換之過程，亦即，從 drain 端看入之阻抗是 source 端看到阻抗之 $(1+g_m r_o)$ 倍。

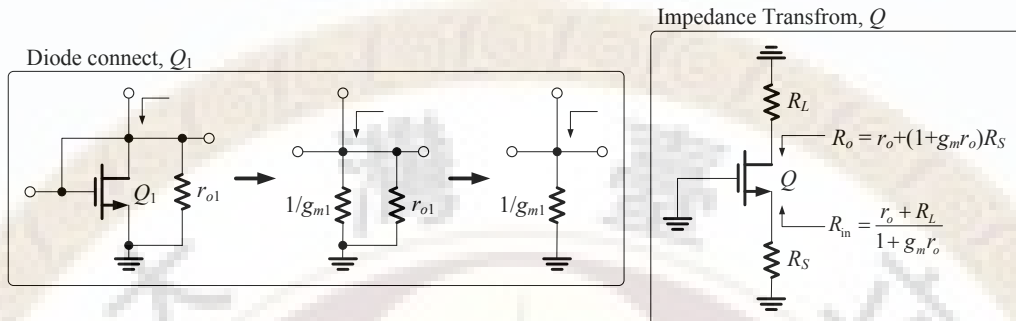原因是 Q_1 為 diode connect 電路，在此電路中不具電晶體放大之功能。而真是會參與這樣轉換的電晶體，即只剩 (Q_2, Q_3) 。



(2) The V_{DS} of Q_2 is higher than that of Q_1 , which results in difference between I_{REF} and I_O . If $V_{GS3} = V_{GS2} = V_{GS1}$ and $V_A = 20 V_{GS1}$, find I_O/I_{REF} . (8%) (Hint: $I_D = (1/2)k_n'(W/L)(V_{GS}-V_t)^2(1+V_{DS}/V_A)$)

Answer:

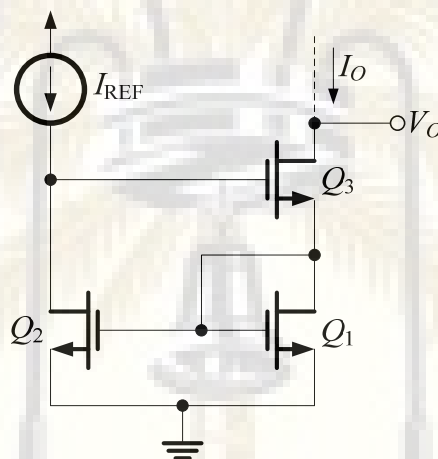

3. (27%) Fig. 3 shows a differential cascode amplifier with an active load formed by a Wilson current mirror. Assume all the transistors are identical.
- (1) Plot the small-signal model of the Wilson current mirror (3%)
 - (2) Find the output resistance of the Wilson current mirror (8%)
 - (3) Plot the small-signal model of the bipolar cascode composed of Q_2 and Q_4 (3%)
 - (4) Find the output resistance of the bipolar cascode composed of Q_2 and Q_4 (8%)
 - (5) Prove that the differential gain of this differential cascode amplifier is given approximately by $A_d = (\beta g_m r_o)/3$ (5%)

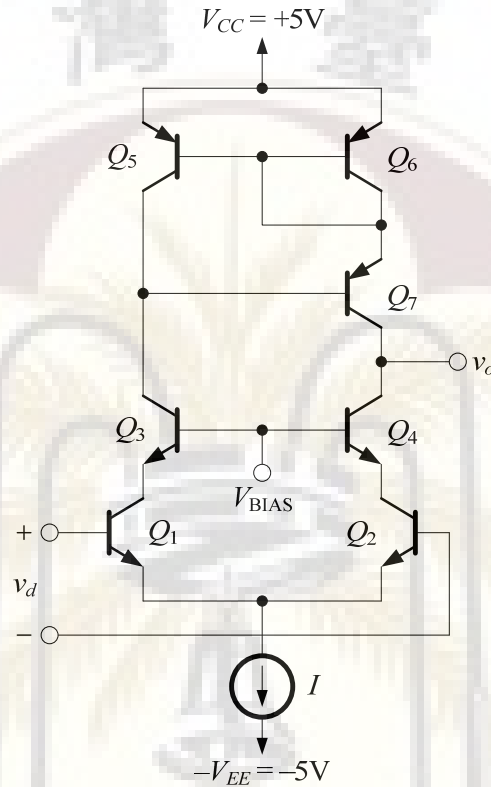



Fig. 3

(Solution)


- (1) Plot the small-signal model of the Wilson current mirror (3%)

Answer:

(Case 1) T model small-signal equivalent circuits.

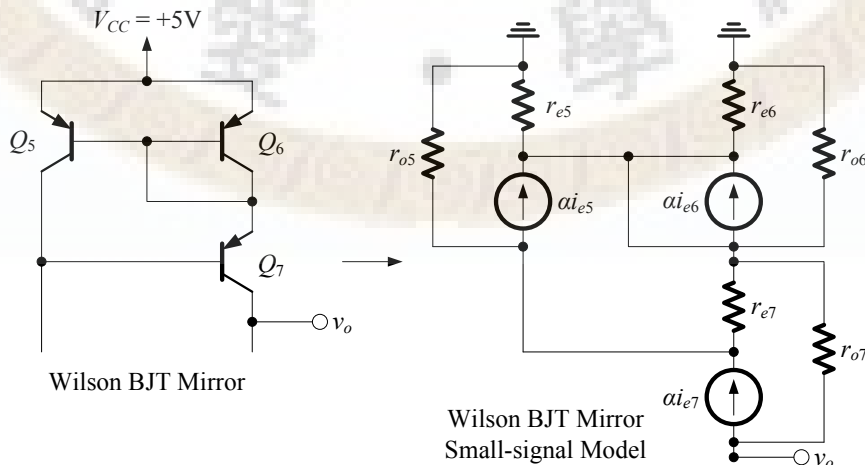


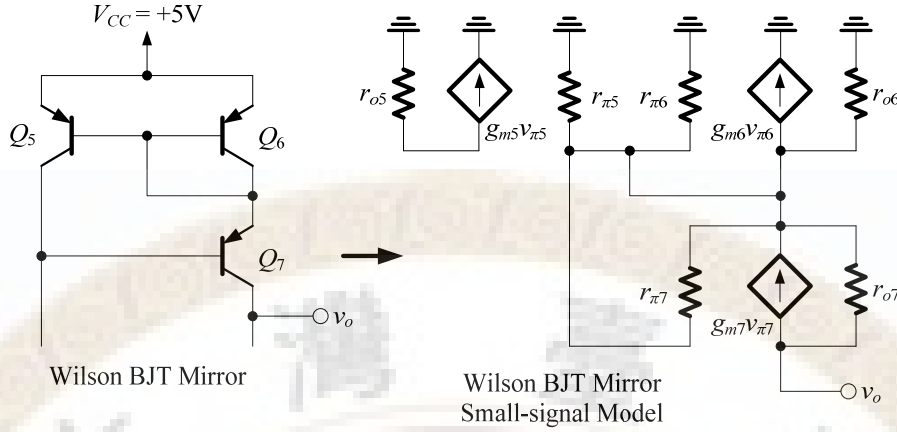(Case 2) π model small-signal equivalent circuits.



(2) Find the output resistance of the Wilson current mirror (8%)

Answer:

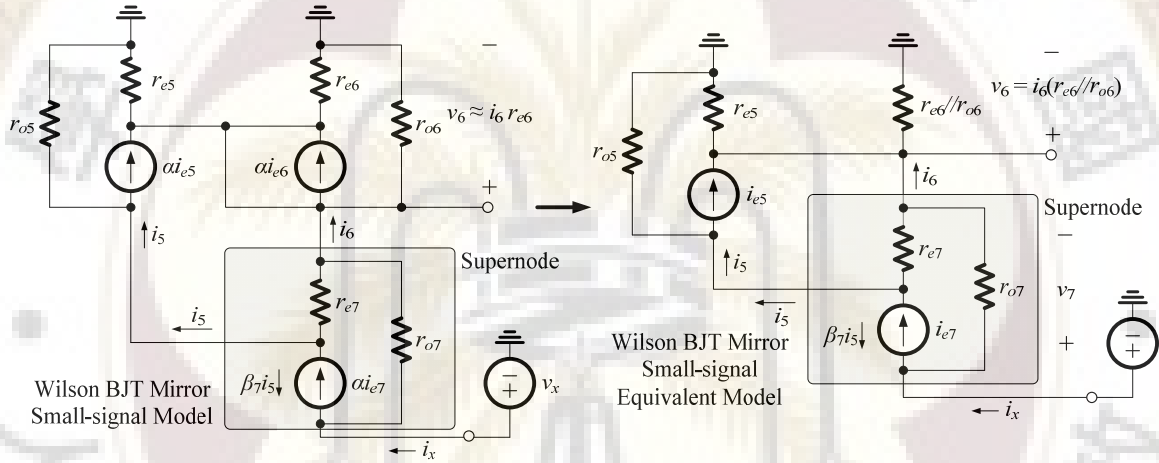


$$v_7 = (\beta_7 i_5 + i_x) r_{o7}, \quad v_6 = i_6 (r_{e6} // r_{o6}) \approx i_6 r_{e6}$$

$$v_x = v_6 + v_7 = i_6 r_{e6} + (\beta_7 i_5 + i_x) r_{o7} = \frac{i_x}{2} r_{e6} + \left(\beta_7 \frac{i_x}{2} + i_x \right) r_{o7} = i_x \left[\frac{r_{e6}}{2} + \left(\frac{\beta_7}{2} + 1 \right) r_{o7} \right] \approx i_x \frac{\beta_7}{2} r_{o7}$$

$$R_o = R_{o,upper} = \frac{v_x}{i_x} = \frac{\beta_7}{2} r_{o7}, \quad \text{where: } i_6 \approx i_5 = \frac{i_x}{2}$$


(3) Plot the small-signal model of the bipolar cascode composed of Q_2 and Q_4 (3%)

Answer:

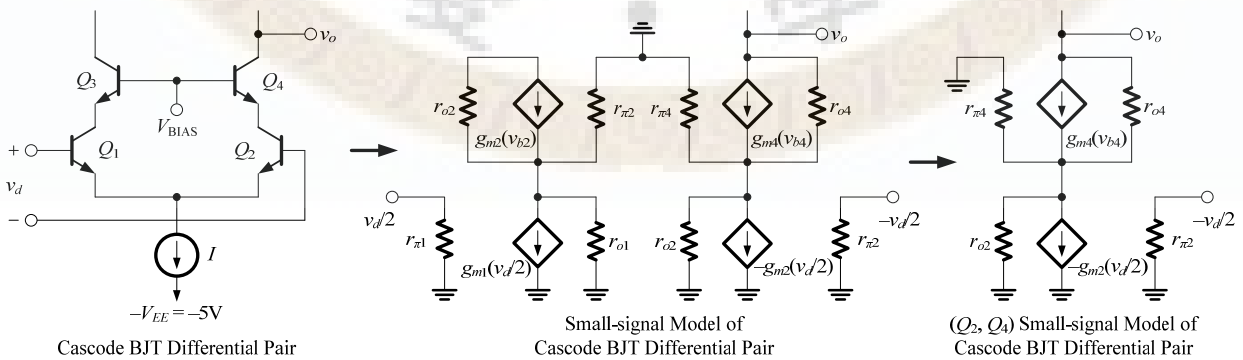

(4) Find the output resistance of the bipolar cascode composed of Q_2 and Q_4 (8%)

Answer:

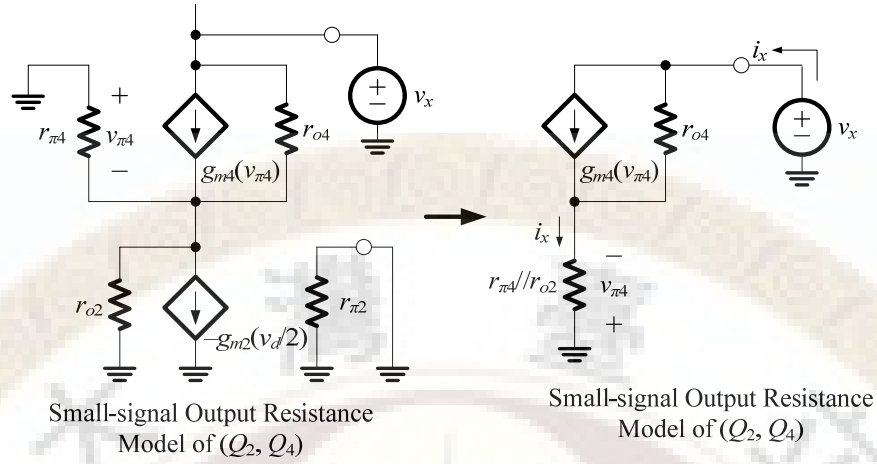

$$v_x = (i_x - g_{m4}v_{\pi4})r_{o4} + i_x(r_{\pi4} // r_{o2}) = i_x [1 + g_{m4}(r_{\pi4} // r_{o2})]r_{o4} + i_x(r_{\pi4} // r_{o2})$$


$$\text{where: } -v_{\pi4} = i_x(r_{\pi4} // r_{o2})$$

$$R_o = R_{o,lower} = \frac{v_x}{i_x} = [1 + g_{m4}(r_{\pi4} // r_{o2})]r_{o4} + (r_{\pi4} // r_{o2}) \approx g_{m4}(r_{\pi4} // r_{o2})r_{o4} \approx g_{m4}r_{\pi4}r_{o4} = \beta_4 r_{o4}$$

(5) Prove that the differential gain of this differential cascode amplifier is given approximately by

$$A_d = (\beta g_m r_o)/3 \quad (5\%)$$

Answer:

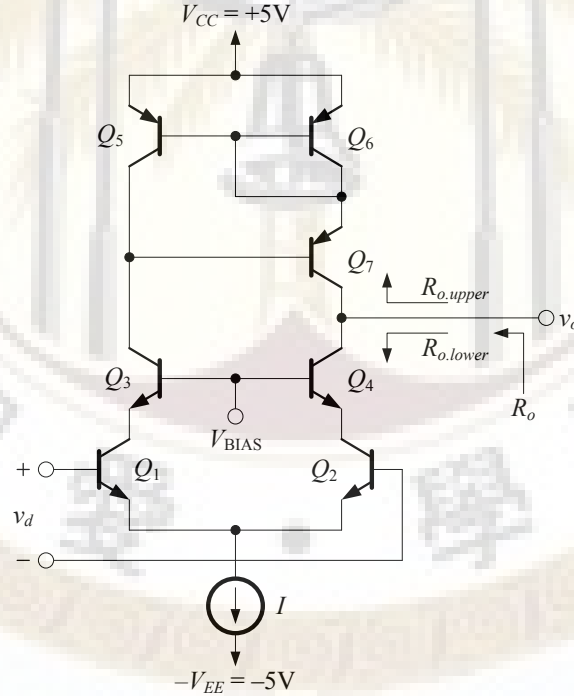

$$R_{o,upper} = \frac{\beta_7}{2} r_{o7}, R_{o,lower} = \beta_4 r_{o4} \rightarrow R_o = R_{o,upper} // R_{o,lower} = \left(\frac{1}{2} \beta r_o \right) // \beta r_o = \frac{1}{3} \beta r_o$$

$$A_d = G_m R_o = \frac{1}{3} (\beta g_m r_o)$$

4. (13%) Fig. 4 shows a MOS differential amplifier. Assume Q_1 and Q_2 are in saturation.

(1) Find the currents i_{D1} and i_{D2} in terms of $v_d \equiv v_{G1} - v_{G2}$ and other semiconductor parameters (8%)

(2) When the tail current I is steered entirely into Q_1 . Find v_d in this case. (5%)

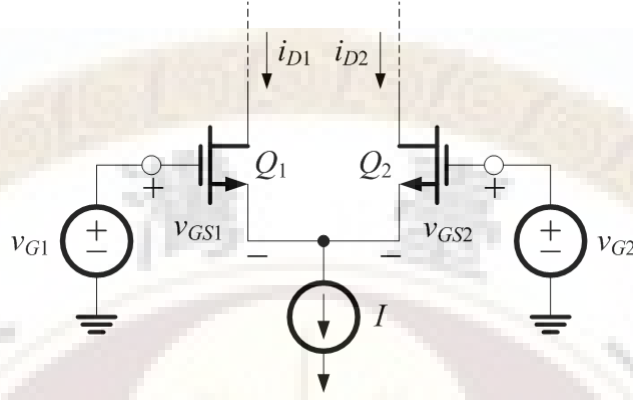


Fig. 4

(Solution)

(1) Find the currents i_{D1} and i_{D2} in terms of $v_d \equiv v_{G1} - v_{G2}$ and other semiconductor parameters (8%)

Answer:

$$(a) \begin{cases} i_{D1} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS1} - V_t)^2 \\ i_{D2} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS2} - V_t)^2 \end{cases} \rightarrow \begin{cases} \sqrt{i_{D1}} = \sqrt{\frac{1}{2} k'_n \frac{W}{L}} (v_{GS1} - V_t) \dots (1) \\ \sqrt{i_{D2}} = \sqrt{\frac{1}{2} k'_n \frac{W}{L}} (v_{GS2} - V_t) \dots (2) \end{cases}$$

$$v_d = v_{GS1} - v_{GS2} = v_{G1} - v_{G2}$$

$$(1) - (2), \rightarrow \sqrt{i_{D1}} - \sqrt{i_{D2}} = \sqrt{\frac{1}{2} k'_n \frac{W}{L}} v_d \dots (3)$$

$$(3)^2 \rightarrow (\sqrt{i_{D1}} - \sqrt{i_{D2}})^2 = \frac{1}{2} k'_n \frac{W}{L} v_d^2 \rightarrow i_{D1} + i_{D2} - 2\sqrt{i_{D1}i_{D2}} = \frac{1}{2} k'_n \frac{W}{L} v_d^2$$

$$\rightarrow 2\sqrt{i_{D1}i_{D2}} = I - \frac{1}{2} k'_n \frac{W}{L} v_d^2 \dots (4), \text{ where } i_{D1} + i_{D2} = I \dots (5)$$

$$(b) (\sqrt{i_{D1}} + \sqrt{i_{D2}})^2 = i_{D1} + i_{D2} + 2\sqrt{i_{D1}i_{D2}} = 2I - \frac{1}{2} k'_n \frac{W}{L} v_d^2 \rightarrow \sqrt{i_{D1}} + \sqrt{i_{D2}} = \sqrt{2I - \frac{1}{2} k'_n \frac{W}{L} v_d^2} \dots (6)$$

$$(c) (3) + (6) \rightarrow 2\sqrt{i_{D1}} = \sqrt{\frac{1}{2} k'_n \frac{W}{L}} v_d + \sqrt{2I - \frac{1}{2} k'_n \frac{W}{L} v_d^2} \rightarrow i_{D1} = \frac{1}{4} \left(\sqrt{\frac{1}{2} k'_n \frac{W}{L}} v_d + \sqrt{2I - \frac{1}{2} k'_n \frac{W}{L} v_d^2} \right)^2$$

$$\rightarrow i_{D1} = \frac{1}{4} \left(\frac{1}{2} k'_n \frac{W}{L} v_d^2 + 2I - \frac{1}{2} k'_n \frac{W}{L} v_d^2 + 2\sqrt{\frac{1}{2} k'_n \frac{W}{L}} v_d \sqrt{2I - \frac{1}{2} k'_n \frac{W}{L} v_d^2} \right)$$

$$= \frac{I}{2} + \sqrt{\frac{1}{2} k'_n \frac{W}{L}} \left(\frac{v_d}{2} \right) \sqrt{2I - \frac{1}{2} k'_n \frac{W}{L} v_d^2} = \frac{I}{2} + \sqrt{\frac{1}{2} k'_n \frac{W}{L}} \left(\frac{v_d}{2} \right) \sqrt{2I - \frac{1}{2} k'_n \frac{W}{L} v_d^2}$$

$$= \frac{I}{2} + \sqrt{k'_n \frac{W}{L}} I \left(\frac{v_d}{2} \right) \sqrt{1 - \frac{1}{I} k'_n \frac{W}{L} \left(\frac{v_d}{2} \right)^2} = \frac{I}{2} + \sqrt{k'_n \frac{W}{L}} I \left(\frac{v_d}{2} \right) \sqrt{1 - \frac{(v_d/2)^2}{I/(k'_n(W/L))}}$$

$$\rightarrow i_{D1} = \frac{I}{2} + \sqrt{k'_n \frac{W}{L}} I \left(\frac{v_d}{2} \right) \sqrt{1 - \frac{(v_d/2)^2}{I/(k'_n(W/L))}}$$

(d) $\because i_{D1} + i_{D2} = I$

$$\rightarrow i_{D2} = I - i_{D1} = \frac{I}{2} - \sqrt{k'_n \frac{W}{L}} I \left(\frac{v_d}{2} \right) \sqrt{1 - \frac{(v_d/2)^2}{I/(k'_n(W/L))}}$$

(e) At the bias point, $v_d = 0$, leading to

$$i_{D1} = i_{D2} = \frac{I}{2}, \quad v_{GS1} = v_{GS2} = V_{GS},$$

$$\rightarrow i_{D1} = i_{D2} = \frac{I}{2} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS1} - V_t)^2 = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2 = \frac{1}{2} k'_n \frac{W}{L} V_{OV}^2$$

$$\rightarrow I = k'_n \frac{W}{L} V_{OV}^2 \rightarrow V_{OV} = \sqrt{\frac{I}{k'_n(W/L)}} \rightarrow \sqrt{k'_n \frac{W}{L}} = \frac{\sqrt{I}}{V_{OV}}$$

$$(f) \quad i_{D1} = \frac{I}{2} + \sqrt{k'_n \frac{W}{L}} I \left(\frac{v_d}{2} \right) \sqrt{1 - \frac{(v_d/2)^2}{I/(k'_n(W/L))}} = \frac{I}{2} + \left(\frac{I}{V_{OV}} \right) \left(\frac{v_d}{2} \right) \sqrt{1 - \left(\frac{v_d/2}{V_{OV}} \right)^2}$$

$$i_{D2} = \frac{I}{2} - \left(\frac{I}{V_{OV}} \right) \left(\frac{v_d}{2} \right) \sqrt{1 - \left(\frac{v_d/2}{V_{OV}} \right)^2}$$

(2) When the tail current I is steered entirely into Q_1 . Find v_d in this case. (5%)

Answer:

$$\rightarrow i_{D1} = \frac{I}{2} + \left(\frac{I}{V_{OV}} \right) \left(\frac{v_d}{2} \right) \sqrt{1 - \left(\frac{v_d/2}{V_{OV}} \right)^2} = I$$

$$\rightarrow \left(\frac{I}{V_{OV}} \right) \left(\frac{v_d}{2} \right) \sqrt{1 - \left(\frac{v_d/2}{V_{OV}} \right)^2} = \frac{I}{2} \rightarrow \left(\frac{v_d}{V_{OV}} \right) \sqrt{1 - \left(\frac{v_d/2}{V_{OV}} \right)^2} = 1 \rightarrow \left(\frac{v_d}{V_{OV}} \right)^2 \left[1 - \left(\frac{v_d/2}{V_{OV}} \right)^2 \right] = 1$$

$$\rightarrow \left(\frac{v_d}{V_{OV}} \right)^2 \left[1 - \frac{1}{4} \left(\frac{v_d}{V_{OV}} \right)^2 \right] = 1 \rightarrow -\frac{1}{4} \left(\frac{v_d}{V_{OV}} \right)^4 + \left(\frac{v_d}{V_{OV}} \right)^2 - 1 = 0 \rightarrow \left(\frac{v_d}{V_{OV}} \right)^4 - 4 \left(\frac{v_d}{V_{OV}} \right)^2 + 4 = 0$$

$$\rightarrow \left[\left(\frac{v_d}{V_{OV}} \right)^2 - 2 \right]^2 = 0 \rightarrow \left(\frac{v_d}{V_{OV}} \right)^2 = 2 \rightarrow v_d = \sqrt{2} V_{OV} = \sqrt{\frac{2I}{k'_n(W/L)}}$$

5. (20%) The NMOS transistor in the discrete common-source amplifier of Fig. 5 is biased to have $g_m = 1 \text{ mA/V}$. Find

(1) A_M (4%),

(2) f_{p1} (4%), f_{p2} (4%),

(3) f_{p3} (4%) and f_L (4%)

in unit of Hz using the short circuit time-constant method (i.e., the low-frequency 3dB frequency is given by the summation of all poles). Do not forget the (2π) .

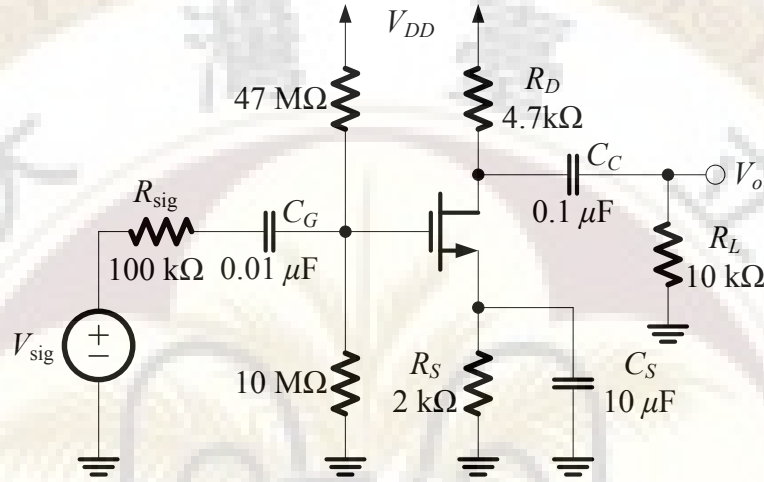


Fig. 5

(Solution)

(1) A_M (4%),

$$R_G = 47 \text{ M}\Omega // 10 \text{ M}\Omega = 8.25 \text{ M}\Omega \rightarrow (+1\%)$$

$$A_M = -\frac{R_G}{R_G + R_{\text{sig}}} g_m (R_D // R_L) \rightarrow (+2\%) = -\frac{8.25 \text{ M}\Omega}{8.25 \text{ M}\Omega + 0.1 \text{ M}\Omega} (1 \text{ mA/V}) (4.7 \text{ k}\Omega // 10 \text{ k}\Omega)$$

$$\rightarrow A_M = -3.16 (V/V) \rightarrow (+1\%)$$

(2) f_{p1} (4%), f_{p2} (4%),

$$f_{p1}|_{\text{@Gate Terminal}} = \frac{1}{2\pi C_G (R_G + R_{\text{sig}})} \rightarrow (+3\%) = \frac{1}{2\pi \times 0.01 \mu\text{F} \times (8.25 \text{ M}\Omega + 0.1 \text{ M}\Omega)} = 1.9 \text{ Hz} \rightarrow (+1\%)$$

$$f_{p2}|_{\text{@Source Terminal}} = \frac{1}{2\pi C_S \left(R_S // \frac{1}{g_m} \right)} \rightarrow (+3\%) = \frac{1}{2\pi \times 10 \mu\text{F} \times (2 \text{ k}\Omega // 1 \text{ k}\Omega)} = 23.87 \text{ Hz} \rightarrow (+1\%)$$

(3) f_{p3} (4%) and f_L (4%)

$$f_{p3}|_{\text{@Drain Terminal}} = \frac{1}{2\pi C_C (R_D + R_L)} \rightarrow (+3\%) = \frac{1}{2\pi \times 0.1 \mu\text{F} \times (4.7 \text{ k}\Omega + 10 \text{ k}\Omega)} = 108.27 \text{ Hz} \rightarrow (+1\%)$$

$$f_L \approx f_{p3} \rightarrow (+3\%) = 108.27 \text{ Hz} \rightarrow (+1\%)$$