

## Electromagnetics II midterm exam date: 2013/11/04

題目一共六題，每題 20 分，採計個人最高分五題。

- (20%) Figure 1 depicts the cross section of a parallel-plate waveguide. The two plates are perfect conductor ( $\sigma \rightarrow \infty$ ), separated by  $d$  (m), and each has a width of  $w$  (m). Two materials of  $(\epsilon_1 = 16\epsilon_0, \mu_1 = \mu_0)$  and  $(\epsilon_2 = 4\epsilon_0, \mu_2 = 4\mu_0)$ , respectively, are inserted between these two plates. Assume a TEM wave propagates in the  $\hat{z}$  direction, its electric field has only the  $\hat{x}$  component, and its magnetic field has only the  $\hat{y}$  component. The fields in the left-half of the cross section are  $(\bar{E}_1, \bar{H}_1)$ , and the fields in the right-half are  $(\bar{E}_2, \bar{H}_2)$ . The fringing effect is neglected.

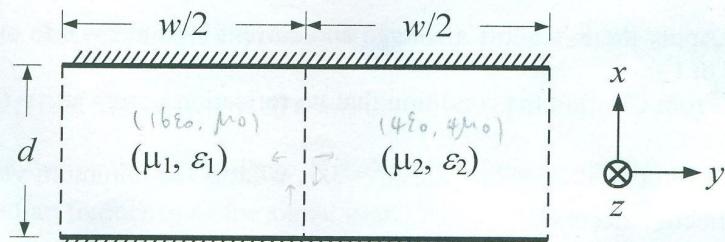


Figure 1

The following boundary conditions may be applicable:

- At the interface between two materials:

$$\hat{n} \times \bar{E}_1 = \hat{n} \times \bar{E}_2, \quad \hat{n} \times \bar{H}_1 = \hat{n} \times \bar{H}_2, \quad \hat{n} \cdot \bar{D}_1 = \hat{n} \cdot \bar{D}_2, \quad \hat{n} \cdot \bar{B}_1 = \hat{n} \cdot \bar{B}_2.$$

- At the interface between the material and the plate:

$$\hat{n} \times \bar{E}_1 = 0, \quad \hat{n} \times \bar{H}_1 = \bar{J}_s, \quad \hat{n} \cdot \bar{D}_1 = \rho_s, \quad \hat{n} \cdot \bar{B}_1 = 0.$$

- (2%) Specify the relation between  $\bar{E}_1$  and  $\bar{E}_2$ .
- (2%) Specify the relation between  $\bar{H}_1$  and  $\bar{H}_2$ .
- (3%) Derive the surface current density and the total surface current on the bottom plate, in terms of the fields.
- (3%) Derive the surface charge density and the total surface charge on the bottom plate, per meter in the  $\hat{z}$  direction, in terms of the fields
- (3%) What is the capacitance of the waveguide per meter in the  $\hat{z}$  direction?
- (3%) What is the inductance of the waveguide per meter in the  $\hat{z}$  direction?
- (4%) If  $\mu_1\epsilon_1 \neq \mu_2\epsilon_2$ , what will happen to the wave propagation in the  $\hat{z}$  direction?

- (20%) Figure 2 depicts a cascade of transmission line segments. Assume a voltage wave,  $V_{10}e^{-j\beta_1 z}$ , is incident from segment 1.

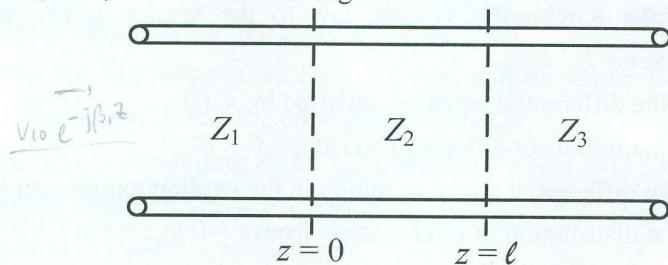


Figure 2

$$\beta = \frac{2\pi}{\lambda} = \frac{\omega}{V_p}$$

The voltage wave in each segment can be expressed as

$$V_1 = V_{10}e^{-j\beta_1 z} + \Gamma_{12}V_{10}e^{j\beta_1 z}$$

$$V_2 = V_{20}e^{-j\beta_2 z} + \Gamma_{23}V_{20}e^{j\beta_2 z}$$

$$V_3 = \tau_{23}V_{20}e^{-j\beta_3 z}$$

where  $\beta_1 = \omega\sqrt{L_1 C_1}$ ,  $\beta_2 = \omega\sqrt{L_2 C_2}$ , and  $\beta_3 = \omega\sqrt{L_3 C_3}$ .

(1) (5%) Derive the current waves,  $I_1$ ,  $I_2$  and  $I_3$ , using the Telegrapher's equation,

$$\frac{\partial V(z)}{\partial z} = -j\omega L I(z)$$

(2) (5%) Apply the Kirchhoff's voltage and current laws at  $z = \ell$  to solve  $\Gamma_{23}$  and  $\tau_{23}$ .

(3) (5%) Apply the Kirchhoff's voltage and current laws at  $z = 0$  to express  $\Gamma_{12}$  in terms of  $\Gamma_{23}$ .

(4) (3%) From (3), find the condition that no reflection occurs at  $z = 0$ , that is,  $\Gamma_{12} = 0$ .

(5) (2%) From (4), if  $Z_1 = Z_3 = Z_0$ ,  $Z_2 = 3Z_0$ , what is the minimum value of  $\ell$  that no reflection occurs?

3. (20%) Figure 3 shows a transmission line loaded with a capacitor. At  $t = 0 - \varepsilon$  ( $\varepsilon$  is an infinitesimal number), there is no residual charge in the capacitor,  $C$ .


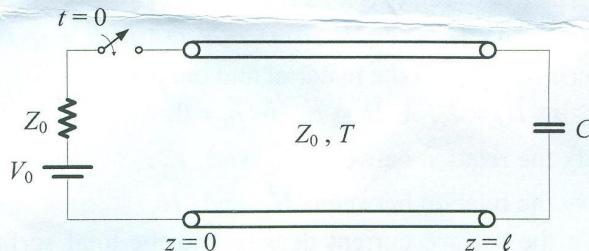


Figure 3

- (1) (2%) At  $t = 0 + \varepsilon$ , what is the ratio between the voltage  $V_+$  and the current  $I_+$  at  $z = 0 + \delta$  ( $\delta$  is an infinitesimal number)?
- (2) (3%) Apply the Kirchhoff's voltage law at  $z = 0$  to find  $V_+$ .
- (3) (2%) At  $t = T + \varepsilon$ , another voltage wave,  $V_-$ , is induced at the capacitor,  $C$ , and propagates in the  $-\hat{z}$  direction. Write down the total current wave and the total voltage wave at  $z = \ell$ .
- (4) (2%) Apply the Kirchhoff's voltage law to the results in (3), across the capacitor,  $C$ , at  $t > T$ .
- (5) (3%) Derive the differential equation satisfied by  $V_-(t)$ .
- (6) (2%) Derive the initial condition of  $V_-(t)$  at  $t = T$ .
- (7) (3%) Solve the differential equation to obtain the explicit expression of  $V_-(t)$ .
- (8) (3%) Draw the distribution of total voltage from  $z = 0$  to  $z = \ell$  at  $t = 2T$ .

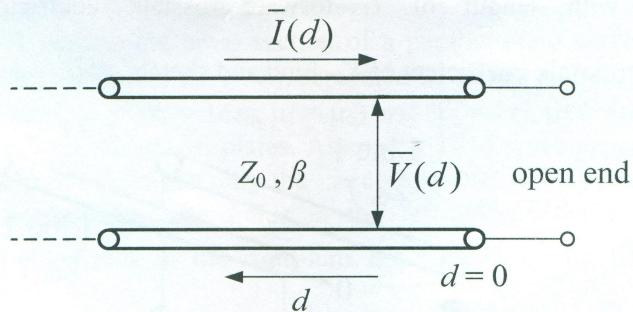4. (20%) Answer the following questions for the open-ended transmission line system.



- (1) Please derive complex voltage  $\bar{V}(d)$  and complex current  $\bar{I}(d)$  in phasor form. (Hint: The answer is in terms of  $\bar{V}^+$ ,  $Z_0$ ,  $\beta$  and  $d$ .)
- (2) Please derive the real voltage  $V(d, t)$  and real current  $I(d, t)$  in time domain if the radian frequency of the signal is  $\omega$ .
- (3) Following (2), will the wave propagate? If yes, what's the velocity? If no, please explain why.
- (4) Calculate the time average power flow  $\langle P \rangle$  on the transmission line.
- (5) If the length of this line is  $\ell$ , what's the input impedance of this line?

5. A quarter-wave transformer matching is used in a transmission line of characteristic impedance  $Z_0$  with the load impedance  $Z_\ell$  as shown in Figure 5. Please answer following questions if  $Z_\ell = 30 \Omega$ :

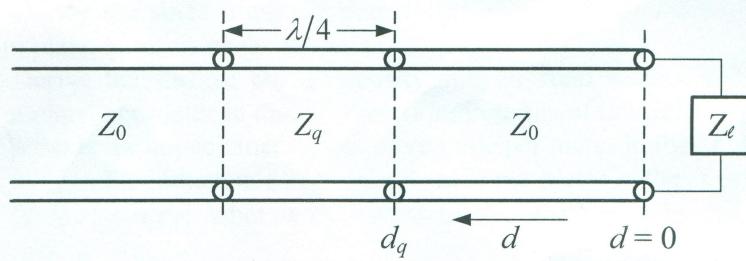


Figure 5

- (1) When the line impedance  $Z(d)$  is a real and maximum value, please find the shortest length  $d_q$  and the corresponding  $Z(d_q)$ .
- (2) When the line impedance  $Z(d)$  is a real and minimum value, please find the shortest length  $d_q$  and the corresponding  $Z(d_q)$ .
- (3) Find the corresponding  $Z_q$  for the conditions stated in (1) and (2), respectively.
- (4) Plot the standing wave patterns along the lines, i.e.,  $d > 0$ , for the conditions stated in (1) and (2), respectively.

$$P_R = \frac{Z_\ell - Z_0}{Z_\ell + Z_0}$$

6. Please determine the induced wave voltages in the secondary line of a coupled pair of lines, with length of  $\ell$ , forward-crosstalk coefficient of  $K_f$ , and backward-crosstalk coefficient of  $K_b$ . Find and sketch  $V_2^+(\ell, t)$  and  $V_2^-(0, t)$ .

