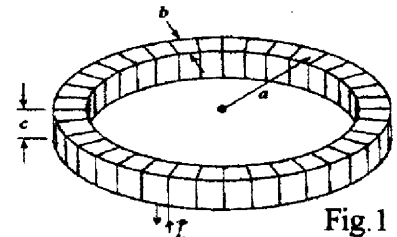



電磁學二第一次段考

註：考試時間 10:10 – 12:40 共 120 分鐘。第六到第八題中只需選擇兩題作答，若三題全答，以其中得分較高之兩題列入總分計算。


- 1) (10%) A filamentary wire carrying current I is closely wound around a toroidal magnetic core of rectangular cross section, as shown in Fig. 1. The mean radius of the toroidal core is a and the number of turns per unit length along the mean circumference of the toroid is N . Find (a) the magnetic field intensity in the core and (b) the inductance of the toroid. Assume that $b \ll a$.



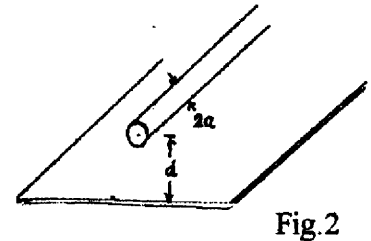- 2) (10%) Consider a wire of radius $a=0.5\text{mm}$ in a height $d=5\text{mm}$ over a ground plane in the air as shown in Fig. 2. Find the per-unit-length capacitance, inductance, and the characteristic impedance of the wire. Note that the per-unit-length capacitance between two parallel cylindrical wires of radius a and center-to-center separation $2d$ can be given by $C = \pi\epsilon_0 / \cosh^{-1}(d/a)$ where $\cosh^{-1} x = \ln(x + \sqrt{x^2 - 1})$



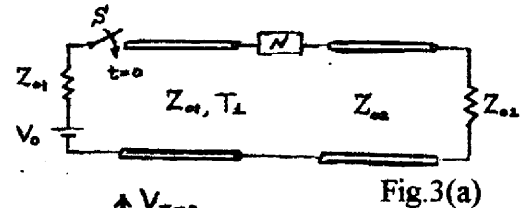
- 3) (15%) In a system shown in Fig. 3(a), the network N consists of a single circuit element (R , L , or C). The system is initially uncharged. The switch S is closed at $t=0$, and the line voltage at $z=0$ is observed to be as shown in Fig. 3(b).




(a) Determine whether the circuit element is R , L , or C .

(b) Find the value of Z_{02}/Z_{01} .

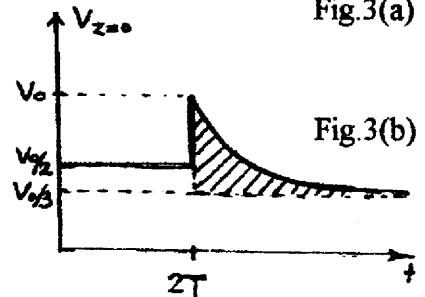(c) Find an expression for the value of the circuit element in terms of the area of the shaded region shown in the figure, Z_{01} , the reflection coefficient, and V_0 .



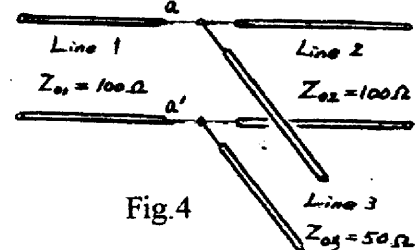- 4) (15%) In Fig. 4, a (+) wave carrying power P is incident on the junction a-a' from line 1. Find (a) the power reflected into line 1; (b) the power transmitted into line 2; and (c) the power transmitted into line 3.




- 5) (20%) In the system shown in Fig. 5, the switch is closed at $t=0$. Assume $V_g(t)$ to be a direct voltage of 100V.

(a) Draw the voltage bounce diagram.

(b) Sketch the line voltage versus t (up to $t=5\mu\text{s}$) at $z=\ell/2$

(c) What is the line voltage at $z=\ell/2$ as t tends to infinity.

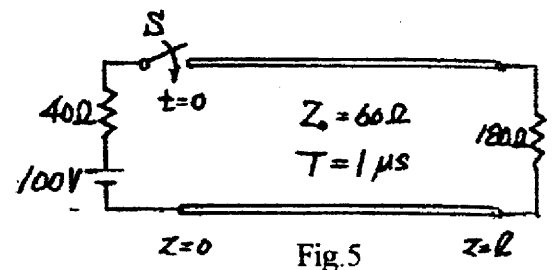(d) Sketch the line voltage versus z at $t=1.5\mu\text{s}$.



- 6) (15%) Consider a typical CMOS buffer driver circuit to a 50Ω transmission line. A simplified equivalent circuit for a high-to-low transition can be represented by Fig.6(a) where $R=0\Omega$.

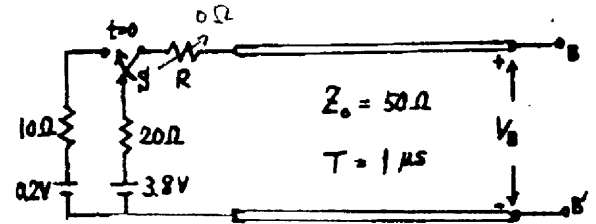


Fig.6(a)

- (a) Plot the output voltage waveform $V_B(t)$ versus time (up to $t=6\mu s$). Note that the transmission line is originally charged up to $V=3.8V$ for $t<0$.

- (b) Consider a voltage clamper D as shown in Fig.6(b) is connected to the output port. The diode D is clamped to $-0.2V$ and having the V-I characteristics shown in Fig.6(c). Repeat (a) and compare the results with those obtained in (a). Discuss how the diode can improve the transition characteristics.

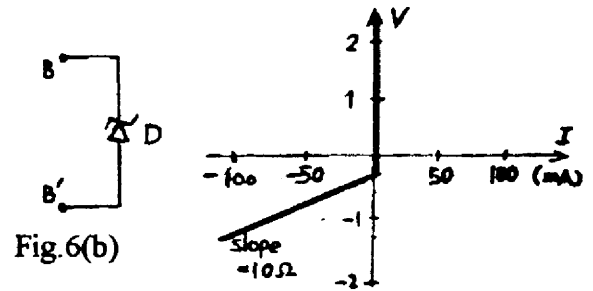


Fig.6(c)

- (c) Another way is to add a series resistor at the source end, say $R=40\Omega$ in Fig.6(a). Repeat (a) and compare the results with those obtained in (a). Discuss how the series resistance can improve the transition characteristics.
- 7) (15%) Consider coupled transmission lines of length $\ell=40cm$ as shown in Fig.7, for which the mutual capacitance $C_m=0.1C$ and mutual inductance $L_m=0.15L$ where C and L are self capacitance and self inductance, respectively, of the two isolated transmission lines. Let C and L be such that the two transmission lines have characteristic impedance $Z_0=50\Omega$ and propagation speed $v_p=20 cm/nsec$. The line 1 is excited by a source voltage which is a ramped pulse of $2V$ and with rise time $t_r=1 nsec$, i.e., $V_g(t)=2 t/t_r$ for $t<t_r$ and $V_g(t)=2$ for $t>t_r$. Find and sketch (a) $V_2(z=0, t)$ and (b) $V_2(z=\ell, t)$ when the length of lines is $\ell=40cm$. (c) Also discuss how the pulse width and pulse height will change if the transmission lines are short lines, say $\ell=5cm$.
- 8) (15%) A section of transmission line can serve as a signal generator. Consider the circuit shown in Fig.8. The switch S is closed to the shorted circuit at $t=0$.
- (a) Sketch the line voltage versus time at $z=\ell$.
- (b) Design the length to give a periodic signal of frequency $1GHz$.
- (c) Sketch the line voltage along the transmission line at $t=\ell/v_p$.

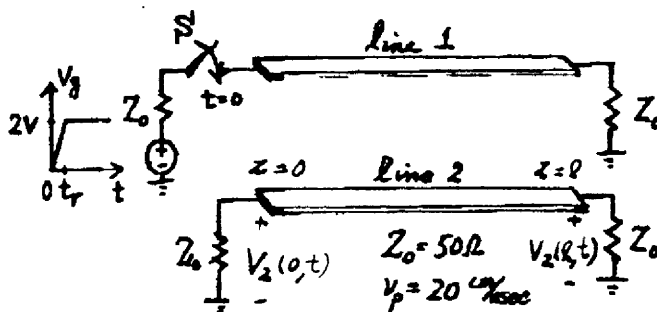


Fig.7

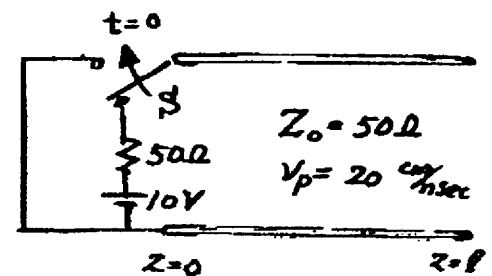


Fig.8