

1021 Microelectronic Circuits I (Midterm)

date: 2012 / 11 / 07 (Thur)

time: 15:30 ~ 17:20

$$\frac{20 - 0.7}{6.15 + 14} = 0.96 \text{ mA}$$

$$15 - 6.15 \times 0.96$$

$$I_{D2} = \frac{15 - 0.7}{6.15 + 14} = 0.99 \text{ mA}$$

$$\frac{8.16}{2 \times 10^3} = 4.08 \text{ mA}$$

ps. 試題可帶回，可使用計算機。


- The diode has a constant voltage-drop of 0.7V when conducting.

determine I_{D1} , I_{D2} , I_{D3} , and V_A for

(a) $R_3=14\text{k}$, $R_4=24\text{k}$; [5%]

(b) $R_3=3.3\text{k}$, $R_4=5.2\text{k}$; [5%]

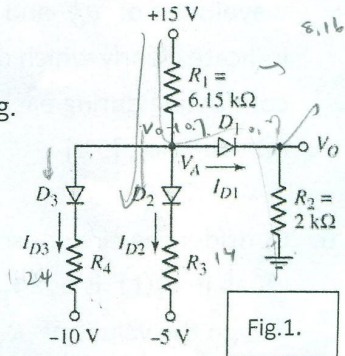(c) $R_3=3.3\text{k}$, $R_4=1.32\text{k}$. [5%]




- Consider the Zener diode circuit shown in Fig.2. The Zener has a characteristic of $V_Z=5.6\text{V}$ at $I_Z=0.1\text{mA}$. The incremental Zener resistance is $r_z=10\Omega$.

(a) Determine V_O with no load ($R_L=\infty$). [3%]

(b) Find the change in the output voltage if V_{PS} changes by $\pm 1\text{V}$. [3%]

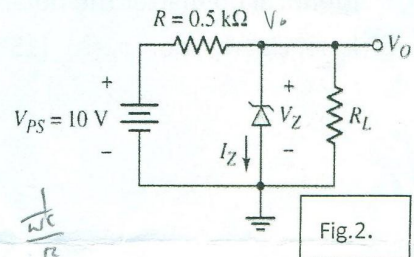(c) Find V_O if $V_{PS}=10\text{V}$ and $R_L=2\text{k}$. [4%]




- In Fig.3. the OpAmp1 is ideal. R_L represents the loading effect from next-stage circuit.

(a) Assuming $R_L=\infty$, derive the transfer function $V_O(s)/V_I(s)$. [7 %]

(b) From (a), let $R_1 \times C_1 > R_2 \times C_2$, plot the frequency response ($|V_O/V_I|$ vs. ω). [6 %]

(c) From (a), let $R_1 \times C_1 = R_2 \times C_2$, plot the frequency response ($|V_O/V_I|$ vs. ω). [6 %]

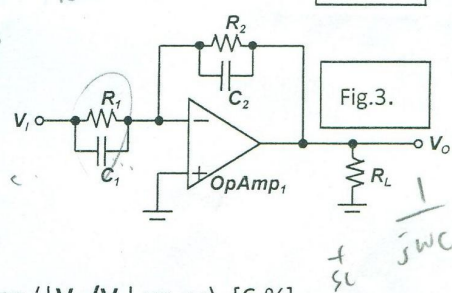(d) If R_L is finite, please derive the transfer function $V_O(s)/V_I(s)$. [6 %]




- The circuit as shown in Fig. 4 is a difference amplifier.

Assume that the op amp has a dc gain of 80 dB and a 3-dB bandwidth of 100 Hz.

(a) What's the CMRR of the difference amplifier? [5%]

(b) For $R_2 = 2R_1$, find the 3-dB frequency of the differential gain. [10%]

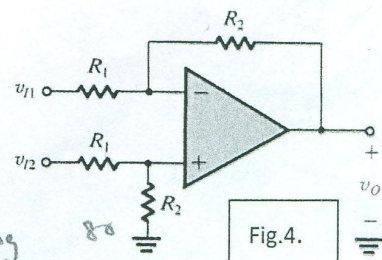(c) If a 3-dB bandwidth of 10 kHz is needed, find the maximum differential gain of the difference amplifier. [10%]



$$CMRR = \frac{A_d}{A_{cm}}$$

$$A_{cl} = \frac{R_2}{R_1}$$

$$20 \log \left(\frac{R_2}{R_1} \right) = 80$$

$$G = V_{I1} \times \left(-\frac{R_2}{R_1} \right)$$

$$+ V_{I2} \times \frac{R_2}{R_1 + R_2} \times \left(1 + \frac{R_2}{R_1} \right)$$

$$20 \log \frac{A_d}{A_{cm}}$$

$$= -2V_{I1} + 2V_{I2} = 2(V_{I2} - V_{I1})$$

5. Assume a 0.7-V drop across each conducting diode in Fig. 5.
- (a) If the magnitude of the average of each output is to be 15 V, find the required amplitude of the sine wave across the entire secondary winding. [5%]
- (b) Please sketch and label clearly the waveforms of v_O^+ and v_O^- . Also indicate clearly which diodes are conducting during each period of cycle on your plot. [5%]

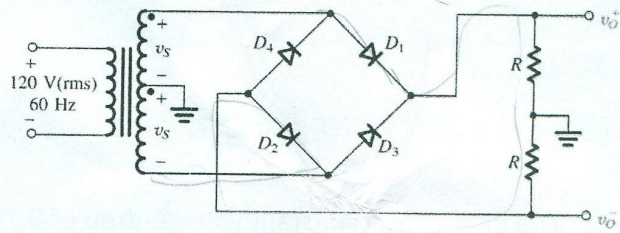


Fig.5.

6. Consider the circuit used for rectification in Fig. 6. Assume the Op-amp and diodes are ideal. If $v_i(t)$ is a $2 V_{p-p}$ sinusoidal wave, please design the values of R_1 , R_2 , and R_3 so that $v_o(t)$ is a precision rectification. (i.e. v_o is identical no matter the polarity of v_i). Sketch and label clearly your $v_o(t)$. [15%]

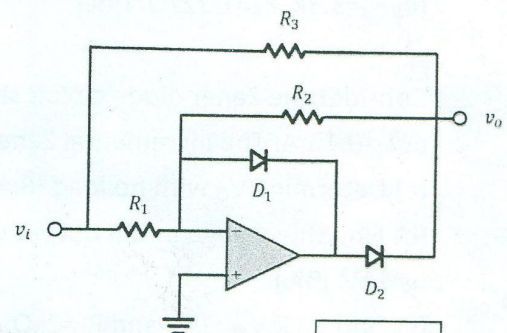


Fig.6.