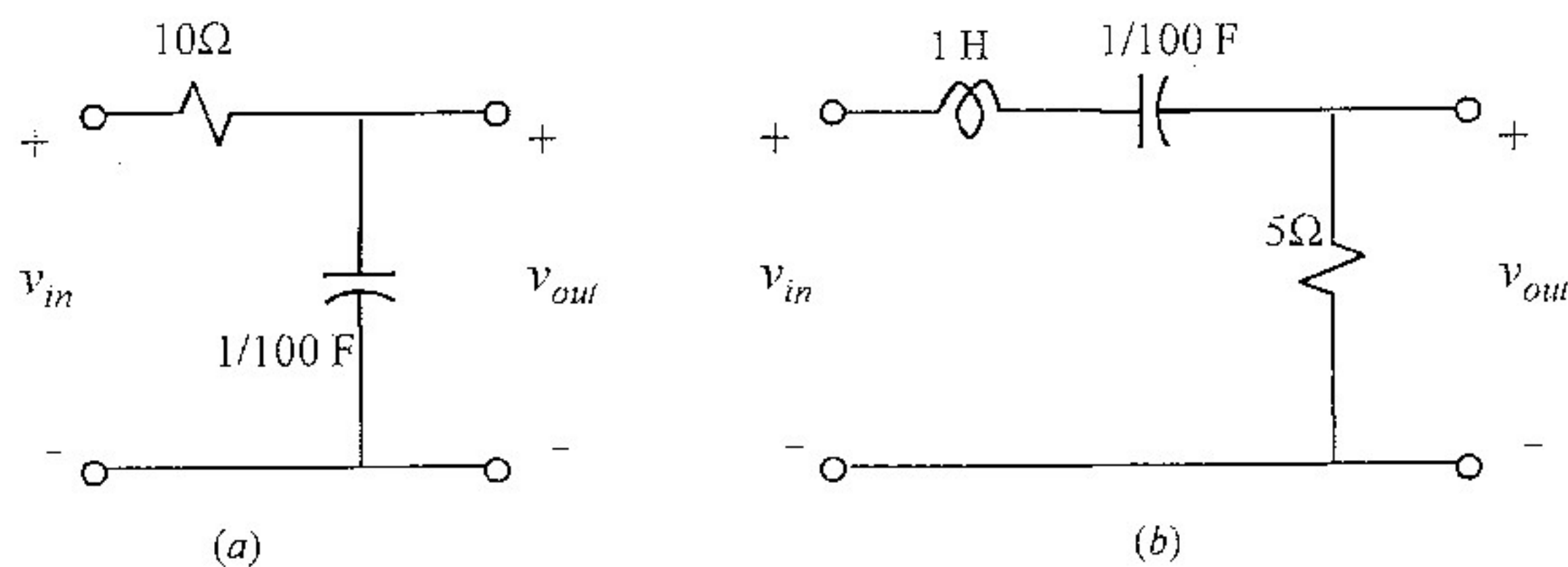


1. (40%) Consider the network shown in Figure 1(a).

- (10%) Please write the transfer function $H(s)$ from v_{in} to v_{out} . How many zeros and poles does $H(s)$ have?
- (5%) Draw the s -plane diagram of the transfer function. Mark all poles and zeros at their locations on the s -plane.
- (10%) Evaluate the network's amplitude ratio $a(\omega) = |H(j\omega)|$ and phase shift $\theta(\omega) = \angle H(j\omega)$ at $\omega = 0^+, 5, 10, 20$ and $\omega = \infty$. Sketch the frequency response curves using these results.
- (5%) What type of filter is this network? (Lowpass, highpass, bandpass, or bandstop) What is the cutoff frequency?
- (10%) Draw the asymptotic Bode plot of the gain and phase for $H(s)$.



2. (60%) Consider the network shown in Figure 1(b).

- (10%) Please write the transfer function $H(s)$ from v_{in} to v_{out} . How many zeros and poles does $H(s)$ have?
- (10%) Draw the s -plane diagram of the transfer function. Mark all poles and zeros at their locations on the s -plane.
- (20%) Use the s -plane diagram to evaluate the network's amplitude ratio $a(\omega) = |H(j\omega)|$ and phase shift $\theta(\omega) = \angle H(j\omega)$ at $\omega = 0^+, 5, 10, 20$ and $\omega = \infty$. Sketch the frequency response curves using these results.
- (10%) What type of filter is this network? (Lowpass, highpass, bandpass, or bandstop)
- (10%) Evaluate the quality factor Q . What are the cutoff frequencies?