

電子學期末考

90.1.9. (三面, 共六題)

1. A n-channel enhancement MOSFET is measured to have a drain current of 10 mA at $V_{GS} = V_{DS} = 10V$ and of 2.5 mA at $V_{GS} = V_{DS} = 6V$. Find the values of $k_n'(W/L)$ and V_t for this device. (14%)
2. For all MOSFET's as shown in Fig. P2, $\mu_n C_{ox} = 40 \text{ mA/V}^2$, $\lambda = 0$, $V_t = 1V$, $W = 30 \mu\text{m}$, and $L = 10 \mu\text{m}$. The threshold voltages for enhancement MOSFET and depletion MOSFET are 1V and -1V, respectively. Find the drain currents of Q1, Q2, Q3, and voltage V_O . (21%)

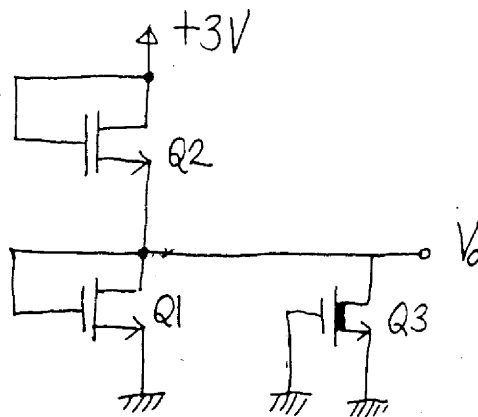


Fig. P2

3. (18%)

Consider the CMOS common-source amplifier in Fig. 5.45(a) for the case: $V_{DD} = 10\text{ V}$, $V_{in} = |V_{tp}| = 1\text{ V}$, $\mu_n C_{ox} \approx 2\mu_p C_{ox} = 20\text{ }\mu\text{A/V}^2$, $W = 100\text{ }\mu\text{m}$, $L = 10\text{ }\mu\text{m}$, and $|V_A| = 100\text{ V}$ for both the n and p devices, and $I_{REF} = 100\text{ }\mu\text{A}$. Find the small-signal voltage gain. Also find the coordinates of the extremities of the amplifier region of the transfer characteristic, that is, points A' and B'. (A' 和 B' 的座標)


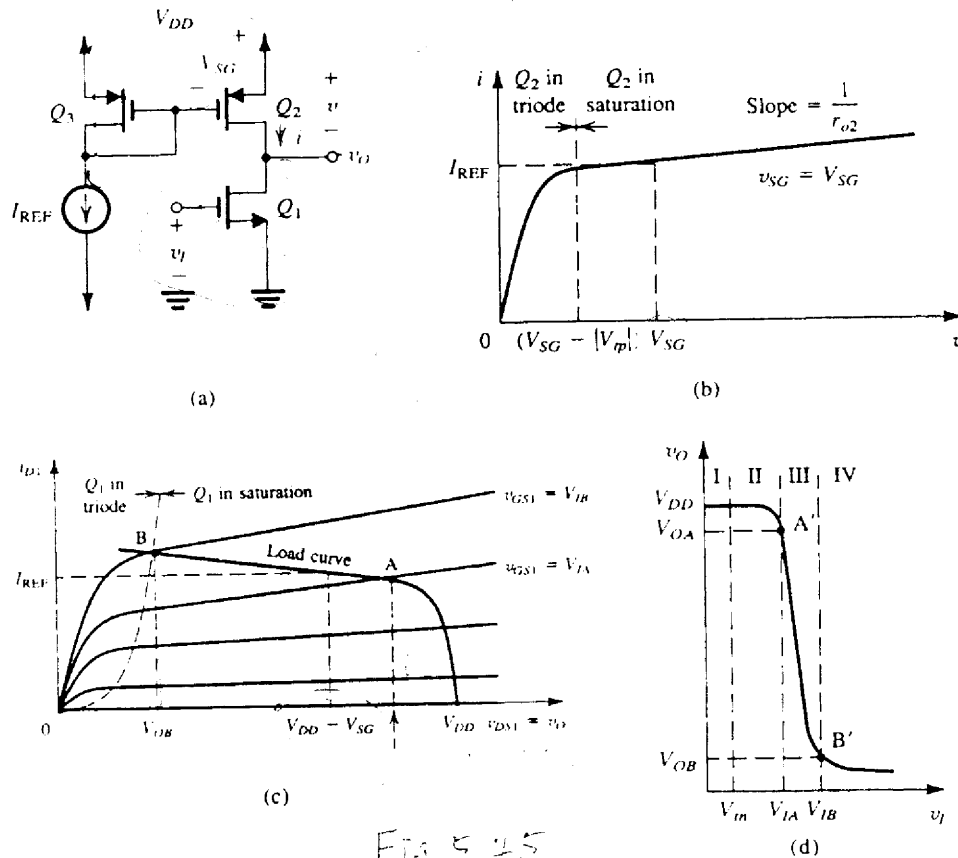


Fig 5.45

4. (15%)

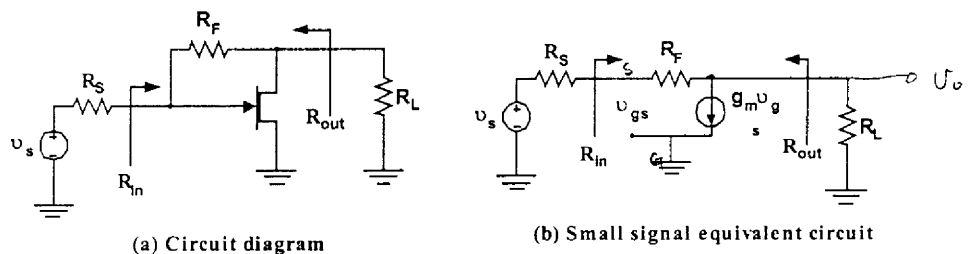


如圖(a)為 GaAs 寬頻放大器電路，常用於 Cable TV 或光纖系統，設其直流偏壓電路均已設計好（故忽略不畫出）。其小訊號等效電路如圖(b)。

- 求出 R_{in}
- 求出 R_{out}
- 若 $R_S = R_L = Z_0$ ， R_F 取為多少時，會使 $R_{in} = R_S$ ， $R_{out} = R_L$ 。


5. Simple different-pair: (see circuit below)

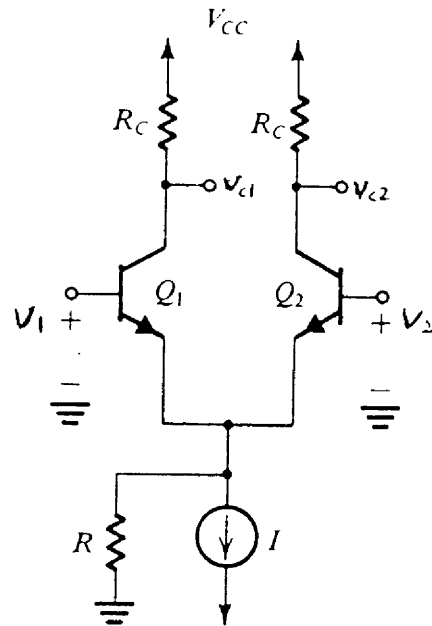- (a) For the single ended output $v_o = v_{c1}$, find the A_d and A_{cm} using half circuit method. (10%)
- (b) Let $v_o = A_1 v_1 + A_2 v_2$, please find A_1 and A_2 in terms of A_d and A_{cm} . (5%)



6. Widlar current circuits:

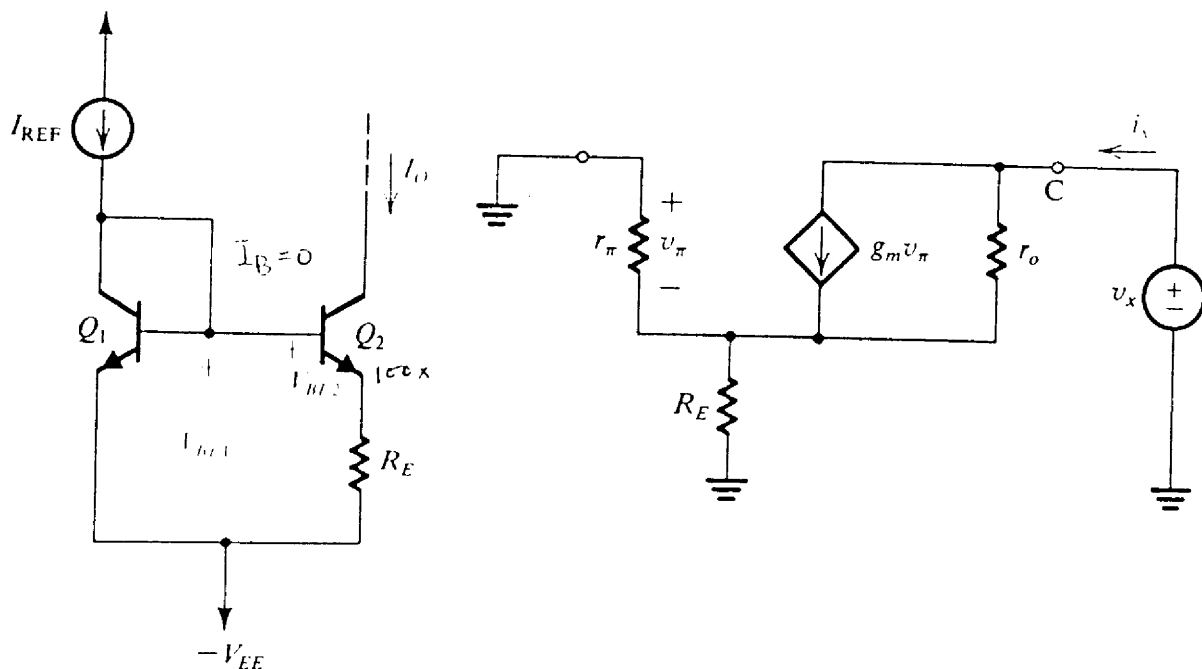- (a) The area of Q_2 is 100 times of Q_1 , please find the R_E in terms of I_{REF} , I_o , and V_T . (10%) ($I_B = 0$)
- (b) Find the output resistance using the ac equivalent circuit below. (10%)



Good luck !!