

Switching Circuits & Logic Design, Fall 2009

Quiz # 1

Problem 1:

Subtract the following pairs of 4-bit binary numbers. Assume that negative numbers are represented in 2's complement. Indicate when an overflow occurs.

$$0011 - 1011$$

(20 points)

Problem 2:

Find the minimum (product-of-sum) form of $Z = (AB \oplus C) + (EF \equiv GH)$.

(20 points)

Problem 3:

$$\text{Simplify } F = ABC'D + A'BE + ABCE + AB'C'D + ABDE$$

(reduce to a sum of three terms)

$$AC'D + A'BE + ABCE$$

(20 points)

Problem 4:

don't care (a) Please draw the Karnaugh map of $F(A,B,C,D) = \sum m(0, 1, 3, 9, 11, 12, 14, 15) + \sum d(4, 5, 6, 7, 10)$. Please note that A is the most significant bit and D is the least significant bit. That means: $ABCD=0001$ corresponds to the minterm m_1 . (10 points)

(b) Please show the minimum SOP of F . (10 points) *sum of product* $A'C' + AC + B'D + ABD'$

(c) Please show the minimum POS of F' . (10 points)

(d) Show the maxterm expansion of F' . (10 points) $\prod M(0, 1, 3, 9, 11, 12, 14, 15) \cdot \prod D(4, 5, 6, 7, 10)$