

Electronic Circuits

Final Examination

10:20am ~ 12:00pm, Jan. 16, 2009

1. Fig. 1 is the equivalent circuit of an inverting amplifier constructed with an op-amp. The op-amp's input, output resistances and gain are r_i , r_o and A . Use v_1 and v_2 as the unknown node voltages to find:
 - (a) [8] corresponding matrix equation $[M][v] = [i_s]$.
 - (b) [7] v_{out}/v_{in} as a function of A .

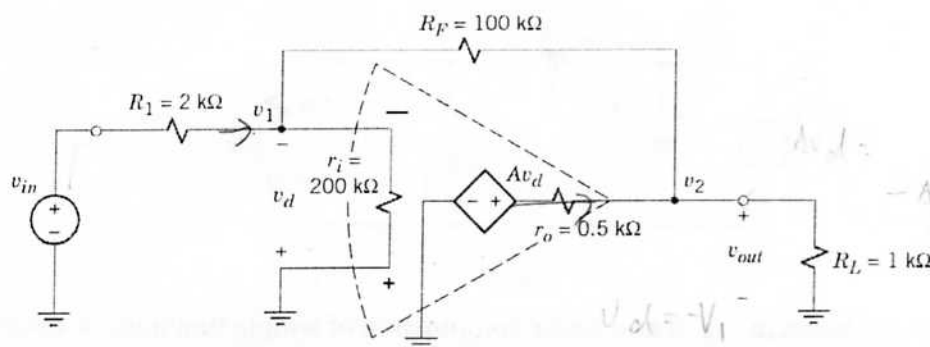


Fig. 1

2. [15] Find $v(t)$ for $t > 0$ in Fig. 2 when $C = \frac{1}{60}$ F and $v_s(t) = \begin{cases} -16V & t < 0 \\ 20 \cos 2t \text{ V} & t > 0 \end{cases}$.

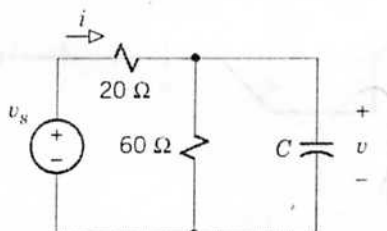


Fig. 2

3. A circuit consisting of a coil with inductance 10mH and winding resistance 20Ω is connected in parallel with a capacitor, a resistor and a generator with an rms voltage 120V. Find:
 - (a) [5] the value of the capacitance that will cause the circuit to be in resonance at 150kHz.
 - (b) [5] the current through the coil at resonance.
(Hint: it is the current through the inductor and the winding resistor.)
 - (c) [5] the Q of the circuit.
4. [7] Let the source network in Fig. 4 (see next page) have $R = 2\text{k}\Omega$, $L = 4\text{mH}$, $C = 250\text{pF}$, and $v_s = 8\cos 10^7 t \text{ V}$. Find the load impedance Z that draws maximum power, and calculate the resulting value of P_{\max} .

NOTE: There are problems in the back.

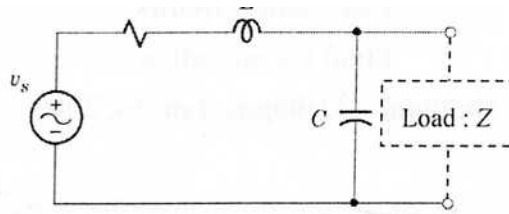


Fig. 4

[8] Find i_1 and i_2 in the circuit in Fig. 5 when $C = \frac{1}{200} \text{ F}$, $L = 0.5 \text{ H}$, $R = 20 \Omega$, $i = 4 \cos(10t + \pi) \text{ A}$, and $v = 40 \cos 20t \text{ V}$.

(Hint: the frequencies of both sources are different.)

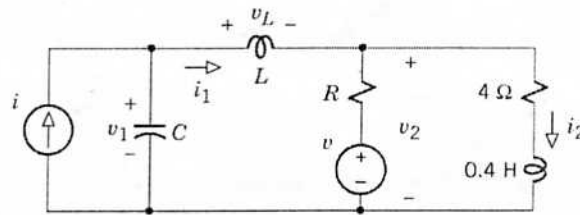


Fig. 5

[15] Express $f(t)$ shown in Fig. 6 as a linear combination of simple functions to obtain $F(s)$.

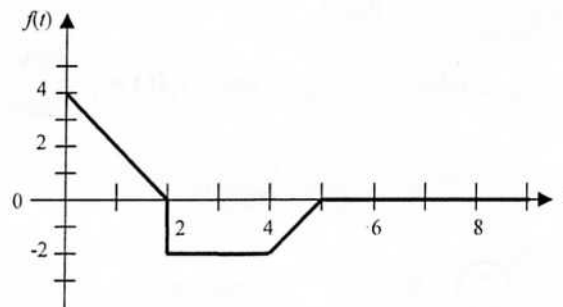


Fig. 6

For the circuit shown in Fig. 7 with $t > 0$,

- [2] find the initial values for inductor current, $i_L(0^-)$, and capacitor voltage, $v_C(0^-)$.
- [3] draw the s-domain diagram of Fig. 7 while using Thevenin's model for inductor and capacitor.
- [10] use mesh analysis to determine the output voltage in s-domain, $V_o(s)$.
- [10] obtain the output voltage in time domain, $v_o(t)$.

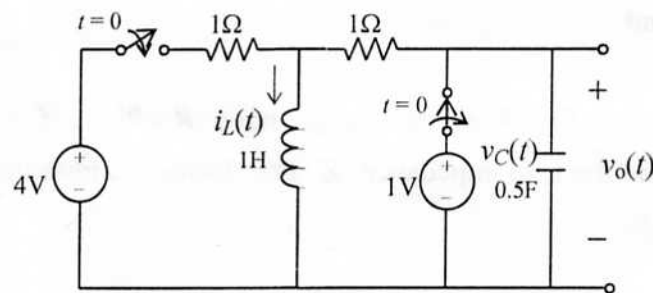


Fig. 7