 
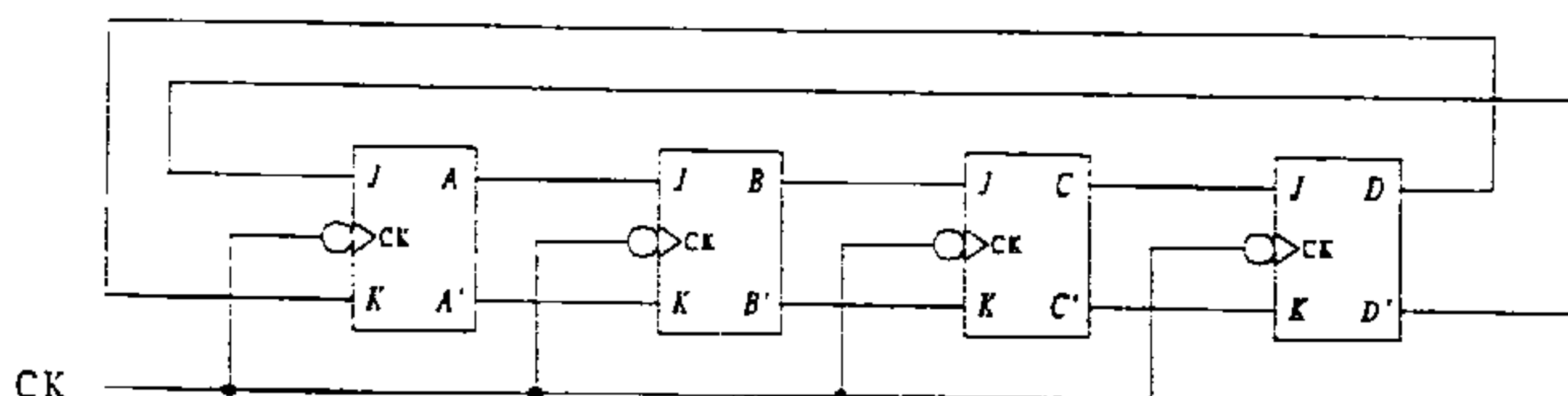


1. The circuit of a J-K latch is shown as follows



- a) Discuss whether or not this circuit is stable for the condition $J=K=C=1$. (8%)
 - b) Derive the constraint of C to make sure the circuit can operate properly. (7%)
2. A set-dominant flip-flop behaves like an S-R flip-flop except that the input $S=R=1$ is allowed, and the flip-flop is set when $S=R=1$.
- a) Derive its characteristic equation. (5%)
 - b) Construct this flip-flop by adding gates to an S-R flip-flop. (5%)
3. A gated latch (G-L flip-flop) behaves as follows:
 If $G=0$, the flip-flop does not change states.
 If $G=1$, the next state of the flip-flop is equal to the value of L .
- a) Derive its characteristic equation. (5%)
 - b) Show how an S-R flip-flop can be converted to a G-L flip-flop by adding gates to an S-R flip-flop. (5%)
4. Consider the digital circuit as follows.
- a) What function is this circuit? Is it a Moore or a Mealy machine? Why? (5%)
 - b) Draw a complete state graph showing all states. (5%)
 - c) Derive a complete state table showing all states. (5%)
 - d) What is the sequence of states starting with $ABCD = 0110$? (5%)



5. Design a counter that counts down from 5 to 0 (and then 5 to 0 ...) by using three S-R flip-flops and some two-input NAND gates.
 - a) Write down your design procedure and plot your result (circuit). (11%)
 - b) Do not forget to tell how your design sets the initial count to 5. (4%)

6. Determine and justify your answers for the following given sets of logic gates, are they functionally complete?
 - a) Exclusive-OR, NOT Gates. (3%)
 - b) Exclusive-OR, AND Gates. (3%)

7. Let a switching function be given by

$$F(A, B, C, D) = \sum m(0, 1, 3, 5, 15)$$
 - a) Design a two-level OR-AND network to realize F. (2%)
 - b) Design a two-level AND-OR network to realize F. (2%)
 - c) Design a two-level NAND-gate network to realize F. (2%)
 - d) Design a two-level NOR-gate network to realize F. (2%)

8. Consider a multiple output logic network which has three output functions given as follows:

$$F_1 = \sum m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$

$$F_2(A, B, C, D) = \sum m(2, 3, 5, 6, 7, 10, 11, 14, 15)$$

$$F_3(A, B, C, D) = \sum m(6, 7, 8, 9, 13, 14, 15)$$
 - a) Find the minimum two-level AND-OR network. (8%)
 - b) Repeat a), find the minimum NAND-gate network. (2%)

9. Consider a design of logic networks by using multiplexers. Let a logic network have four inputs A, B, C, and D, and the output given by $F(A, B, C, D) = \sum m(0, 1, 3, 6, 7, 8, 11, 12, 14)$. Find the logic network using an 8-to-1 multiplexer to realize the function F. (6%)