

Fig.1a is a fully differential multi-stage amplifier. Transistors M3-M11 compose the current sources as shown in Fig.1b conceptually.

- A. Classify each of stages I, II and III as class A, class B or class AB.
Give brief explanations. (3 %)
- B. a. Which of the input differential pairs M1-M2, Q1-Q3 or Q2-Q4 can improve the input linear range by
1. device dimensions (1 %)
 2. bias currents (1 %)
 3. almost constant (no way to be improved by the above 1 and/or 2) (1 %)
- Explain your answers analytically.
- b. 1. Which ONE of the 3 stages I, II or III that dominates the overall offset voltage? Justify your answer analytically. (2 %)
2. Derive an expression of equivalent input offset voltage due to mismatches of transistor pairs M1-M2 and M7-M8. (2 %)
- C. Fig.1c shows the half circuit of this multi-stage amplifier shown in Fig.1b.
- a. Which output node 4 or 9 has the same polarity as the input node 1? (1 %)
- b. Explain briefly that Fig.1c is the half circuit of the differential mode or the common mode (2 %)
- c. Identify notations of node numbers (a, b, c and d), biasing currents (I_x , and I_z), active (M_x , Q_y and Q_z) and passive (R_x , R_y and R_z) components in Fig.1c as those of Fig.1b. (12 %)
- (HINT: R_z is not just $2R_c$!!)
- D. a. How many possible low frequency poles along signal path ?
Give the associated node numbers (a, b, c, and d). (1 %)
- b. If pole-splitting method is asked to apply on the circuit shown in Fig.1c which of the two nodes (a, b, c, and d) can be connected by a compensation (pole splitting) capacitor. Justify your answer.
(HINT: Use Miller Theorem to explain) (2 %)
- c. GIVE the overall small signal AC low frequency voltage gain $A_v = v_o/v_i$ in terms of transistor transconductance g_m and passive components of Fig.1c. (5 %)
- (HINT: DC current sources disconnected and DC voltage sources shorted to ground.)

E. Assume the first stage I is an ideal current source i_s (ideal transconductance stage), a passive negative feedback will be designed to reduce the impedance at node a of input stage II while sample output current i_o at stage III. An additional resistor R_f can accomplish the negative feedback of this function as shown in Fig. 1d conceptually. That is, the amplifier A in Fig. 1d is composed of stages II and III shown in Fig. 1c.

- a. What type of negative feedback architecture should be employed (shunt-shunt, series-series, etc)? Explain briefly. (/ ✓)
(HINT: What connection series or shunt that will reduce the impedance at input node a? Fig. 1d and Fig. 1e should provide enough answer.)
- b. Which of the two nodes (of a, b, c, or d) of Fig. 1c that the resistor R_f should connect to form a NFB as shown in Fig. 1d conceptually?
- c. Draw the AC small signal circuit of b (with R_f connected) (/ ✓)
(HINT: DC current sources disconnected and DC voltage sources shorted to ground.) (2 ✓)
- d. Use c
 1. Give the circuit of the new amplifier A'. Amplifier A' contain equivalent passive components of the two port passive feedback composed of resistor R_f . β is the feedback ratio as shown in Fig. 1e conceptually. (2 ✓)
 2. Derive the feedback ratio β (3 ✓)
 3. Derive the gain a' of amplifier A' (3 ✓)
 4. Using 2 and 3, give close loop gain A_f (5 ✓)

3. Fig. 3 is the simplified internal circuit of the LM380 IC power amplifier. Assuming $V_s = 20$ V and $R_L = 8 \Omega$, please answer the following questions:
- What is approximately the output dc bias voltage? (you have to show how you get your answer)(5%)
 - Explain qualitatively why the dc feedback path through R_2 is negative (and therefore it can act to stabilize the output dc bias voltage.)(4%)
 - What are the function and purpose of diodes D_1 and D_2 ?(2%)
 - Which transistors consist of the output stage?(3%)
 - If a sinusoidal signal is input to this IC power amplifier, sketch the maximum possible waveform of the output signal without clipping(4%)
 - According to (e), calculate approximately the maximum average (i.e. not instantaneous) output power without clipping.(4%)
 - After replacing the second-stage common-emitter amplifier and the output stage with an inverting amplifier block with gain A and denoting the total resistance between the collector of Q_6 and ground by R , show that the voltage gain of this IC is

$$\frac{v_o}{v_i} = \frac{-2R_2 / R_1}{1 + (R_2 / AR)} \quad (8\%)$$

(assuming single-ended input signal).

 


Fig. 3 Simplified internal circuit of the LM380 IC power amplifier. (Courtesy National Semiconductor Corporation)

 


Fig. 1d

 


Fig. 1e

2. The OP AMP in the circuit of Fig.2 has a differential input resistance R_{id} , an open-loop gain μ , and an output resistance r_o . Please derive the loop gain $A\beta$ according to the given parameters.

 


Fig. 2

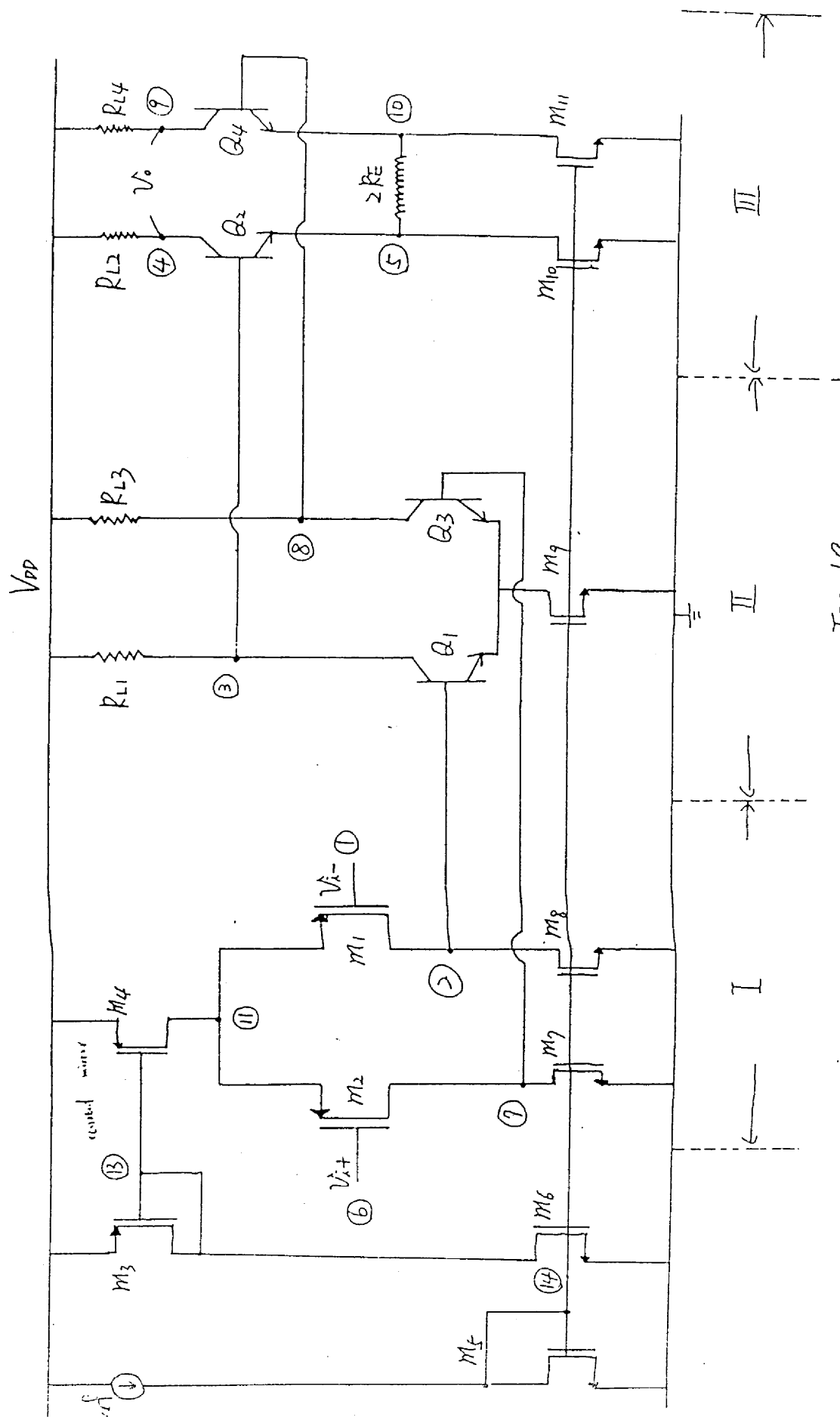


Fig. 1A

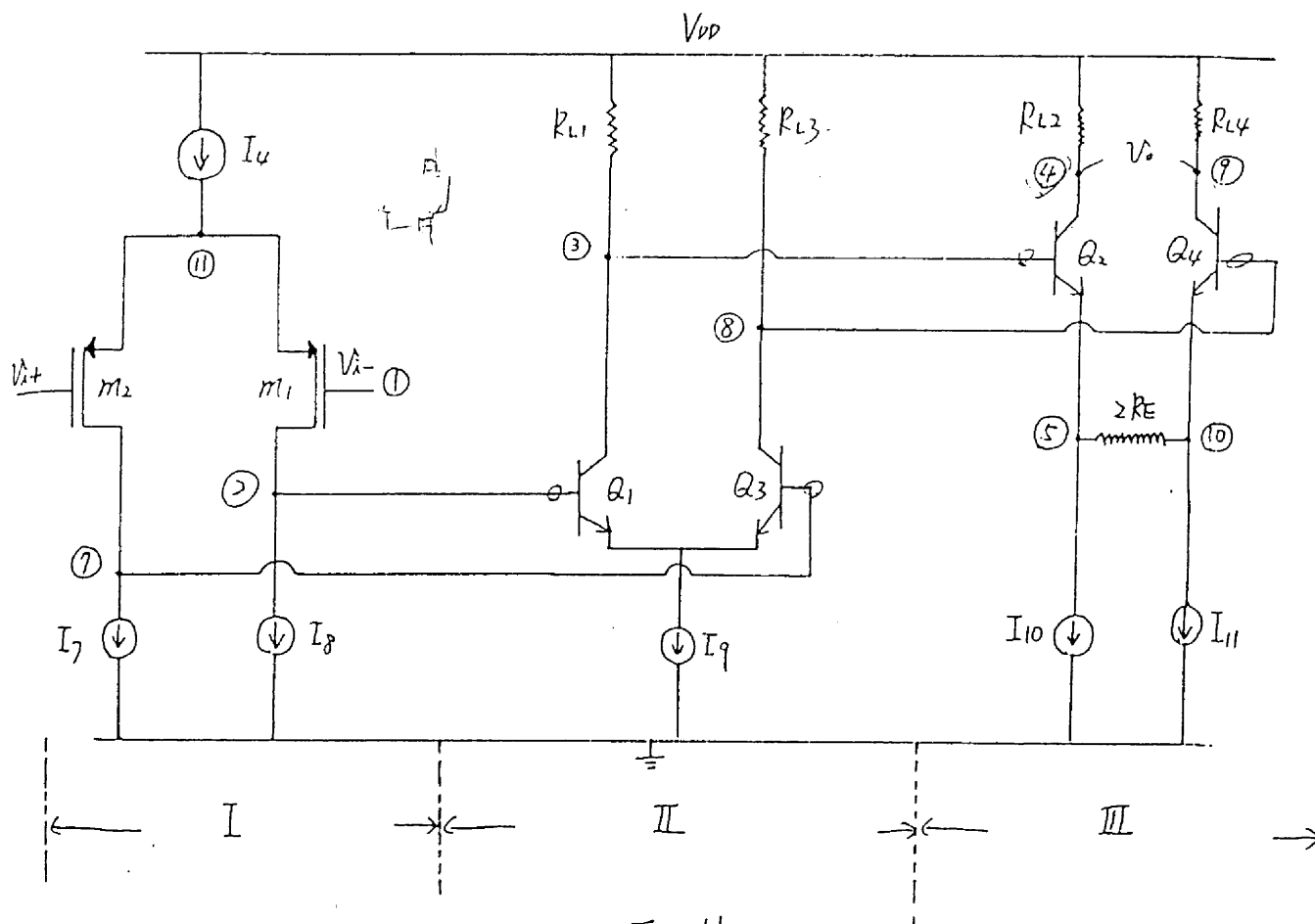


Fig. 1b

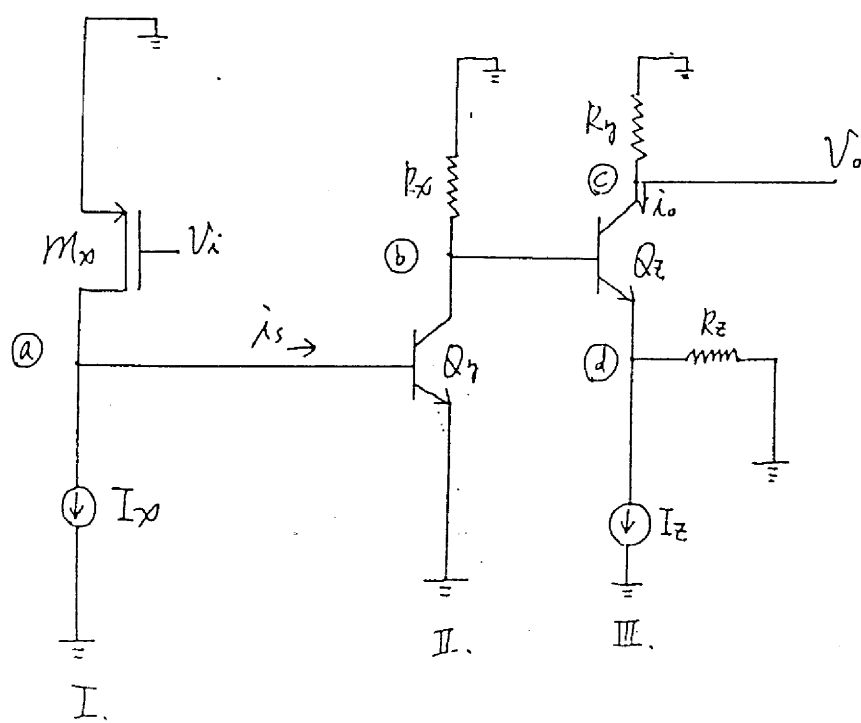


Fig. 1c