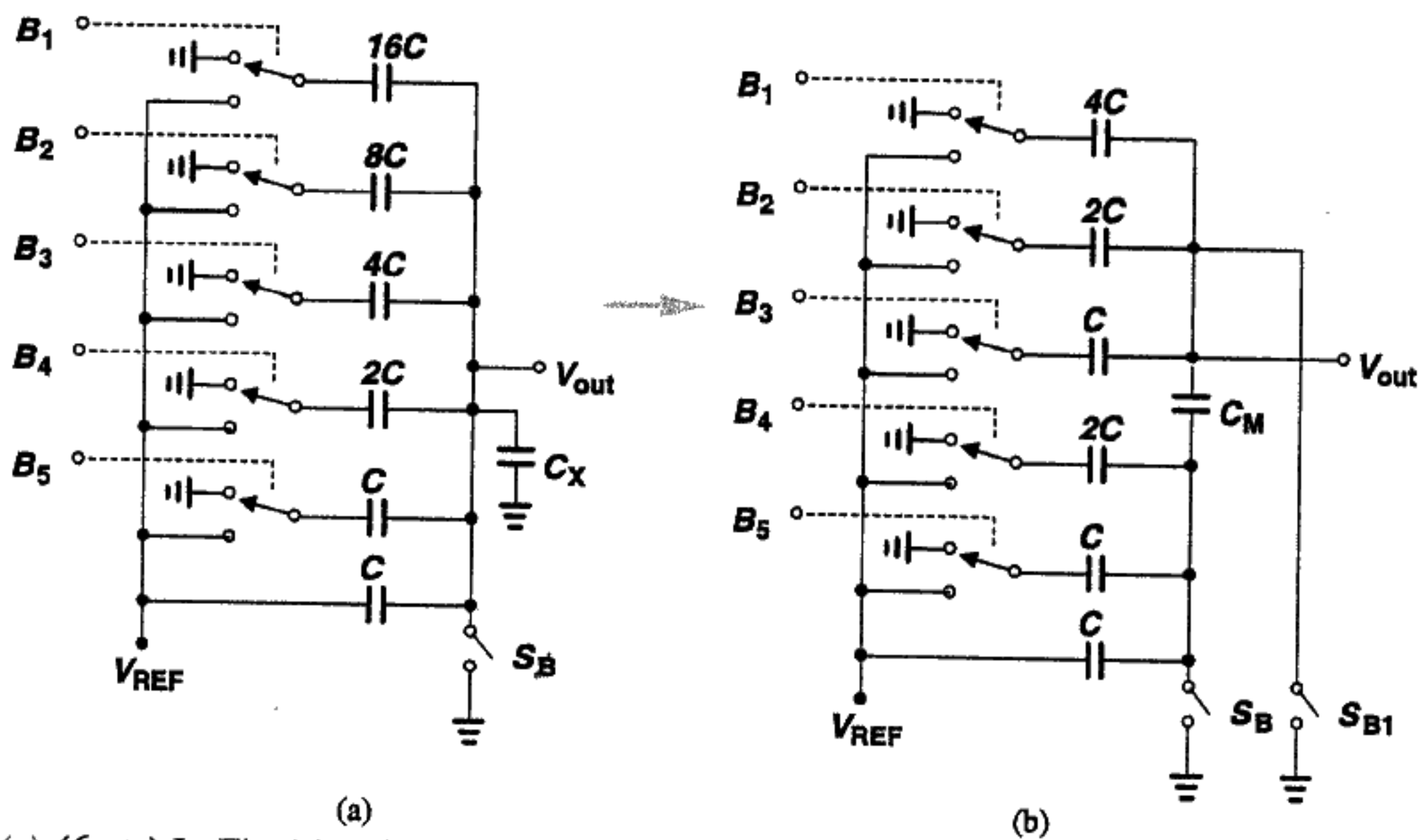


1. (16 pts) A 5-b charge-redistribution DAC, that can be modified from the charge-redistribution ADC, is shown as follows. During reset mode, SB is ON and B_{1-5} are connected to GND such that all capacitances are "emptied" (V_o is zero at this moment). During evaluation mode, B_{1-5} are connected to V_{REF} according to digital code while SB is OFF.




- (a) (6 pts) In Fig (a), what is the output voltage for the input code (B_{1-5}) 01011? ($C_x=0$ in this case)
- (b) (4 pts) In Fig (a), what happens if the DAC is loaded a output capacitance C_x ? Repeat prob. (a).
- (c) (6 pts) In Fig (b), One decides to modify the capacitor array to avoid the exponential increasing of the capacitance array. Determine the C_M such that it has the same conversion property. (Note that SB_1 is ON during reset mode as switch SB)

2. (14pts) A 10-bit dual-slope ADC of the type in the textbooks utilizes a 1-MHz clock and has $V_{ref}=10V$. Its analog input voltage is in the range 0 to $-10V$. The fixed interval T_1 is the time taken for the counter to accumulate a count of 2^N .


(a) (4pts) What is the time required to convert an input voltage equal to the full-scale value?

(b) (4pts) If the peak voltage reached at the output of the integrator is $10V$, what is the integrator time constant?

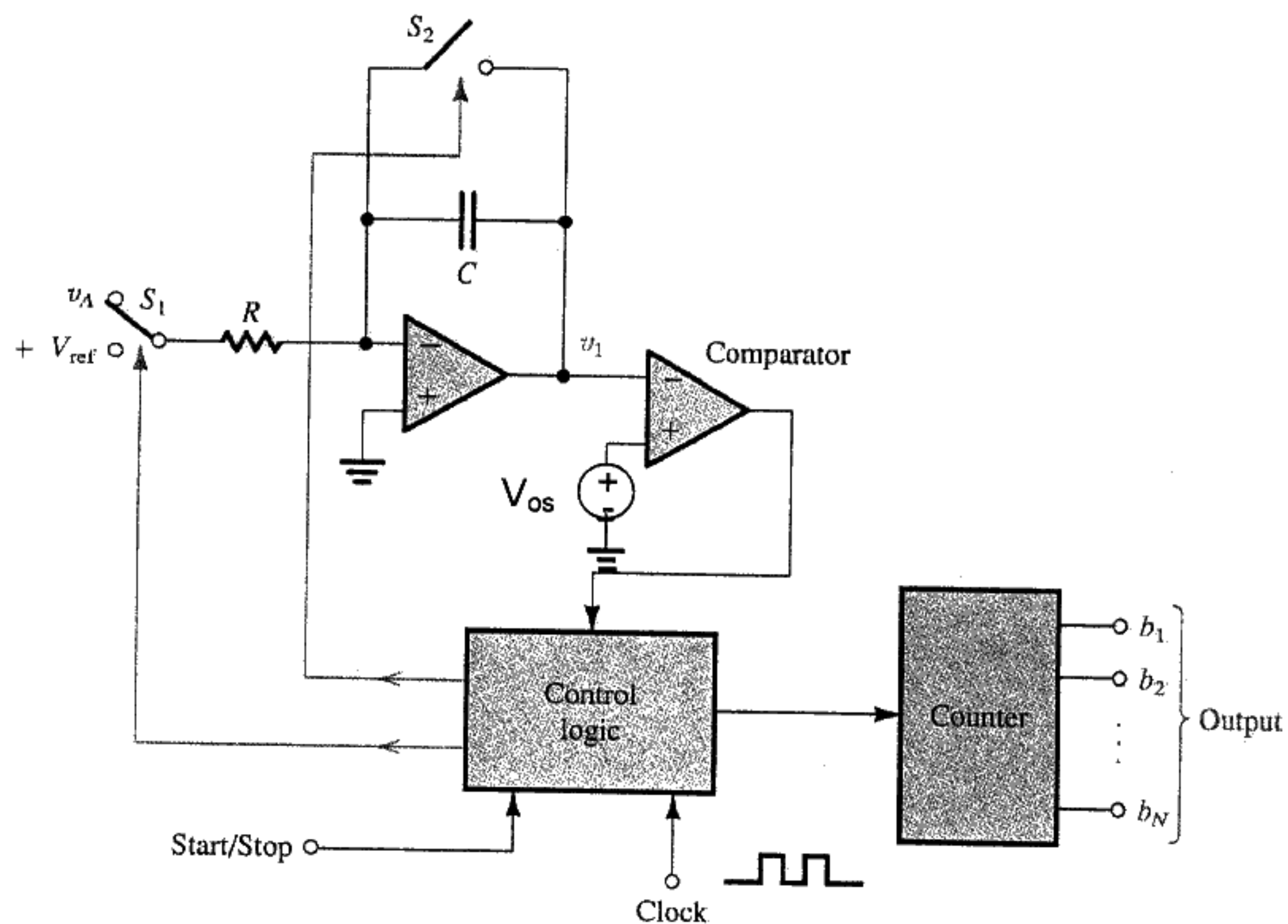(c) (6pts) Now, the comparator has offset, v_{os} , with 100 mV . If V_A is $-10V$, what is the variable time (T_2)? What happens to the ADC characteristics?



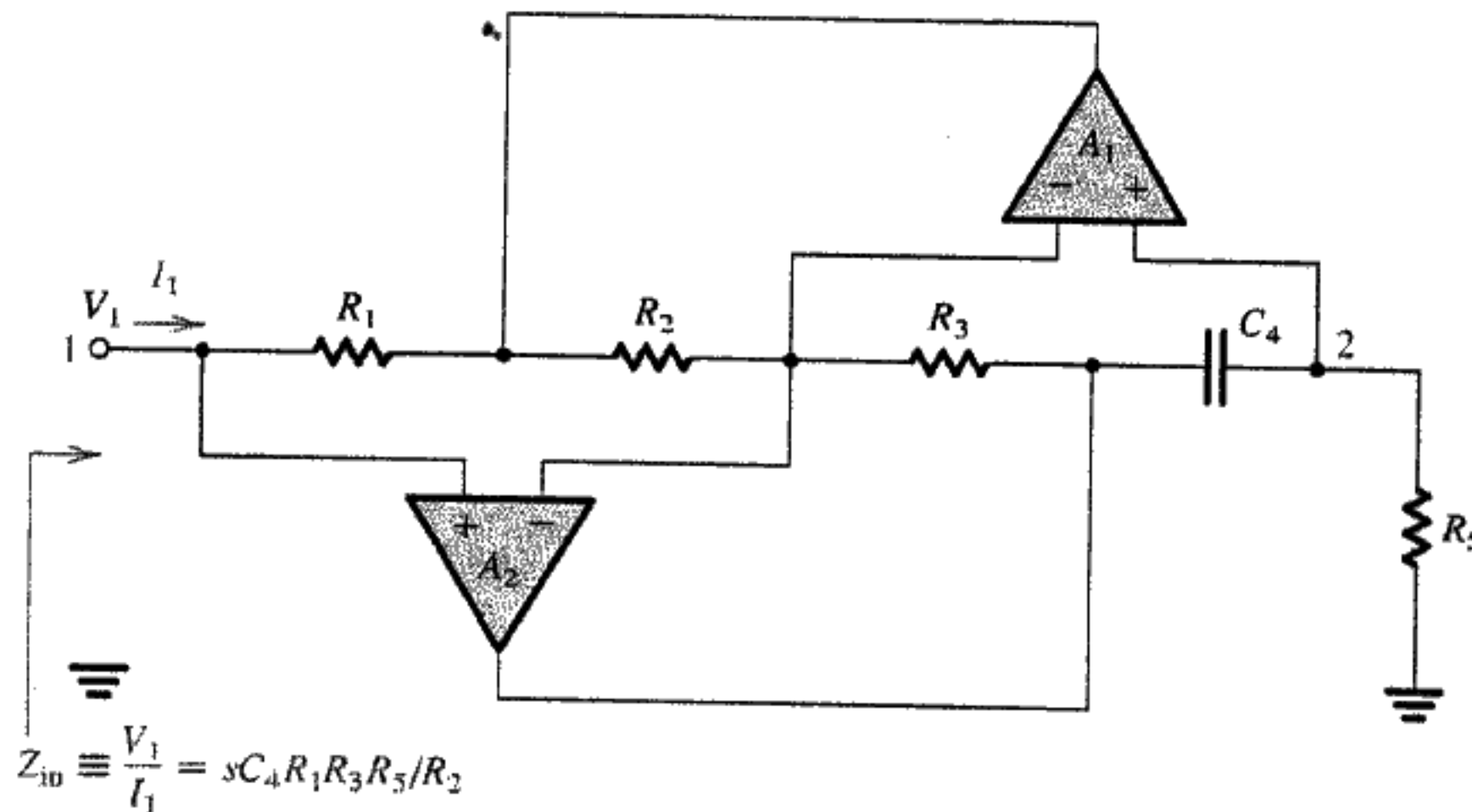3. (20 pts) An inductor emulator is described in the textbook and redrawn as shown below:




(a) (6 pts) Prove that the equivalent inductance looking into node V1 is equal to $C_4R_1R_3R_5/R_2$.

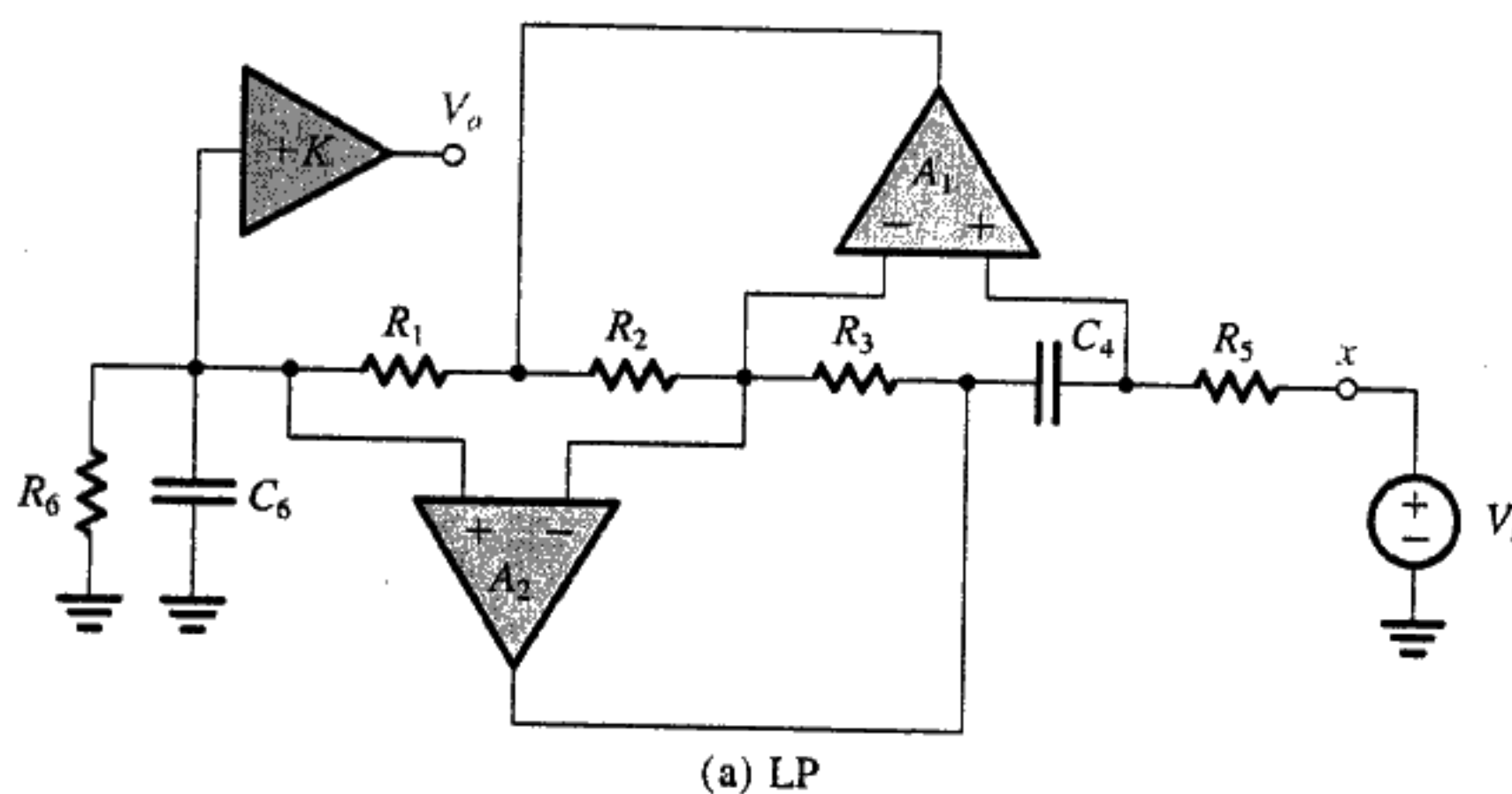(b) So, we now decide to use this emulated inductor to construct a second-order RLC low-pass filter.

(7 pts) First, derive the transfer function $V_o/V_i(s)$. You have to write the KVL/KCL to prove the low-pass characteristics. (no point will be given if you just plug in some number).

(7 pts) Second, all R are 1 KOhm. Determine C2 and C4 such that it behaves the maximally flat type low-pass filter with a 3-dB frequency of 1 MHz.



4. (17pts) Refer to Fig. 4(a), and Fig. 4 (b).

 


Fig. 4(a)

 


Fig. 4(b)

- Derive the voltage transfer function V_a/V_b of the bridged-T RC network shown in Fig. 4(a). (5pts)
- What is the equivalent feedback loop generated by applying the complementary transformation to the loop in Fig. 4.(b). (4pts)
- Consider the bridged-T network of Fig. 4(b) with $R_1 = R_2 = R$, $C_4 = C$, and $C_3 = C/16$. Let the network be placed in the negative-feedback path of an infinite-gain op amp and let C_4 be disconnected from ground and connected to the input signal source V_i . Analyze the resulting circuit to determine its transfer function $V_o(s)/V_i(s)$, where $V_o(s)$ is the voltage at the op amp output. (8pts)

5. (13pts) We wish to replace the two-integrator-loop active-RC biquad Fig. 5(b) by its switched capacitor (SC) counterpart, whose basic unit is shown in Fig. 5(a) without showing the phase-clock. Answer the following questions:

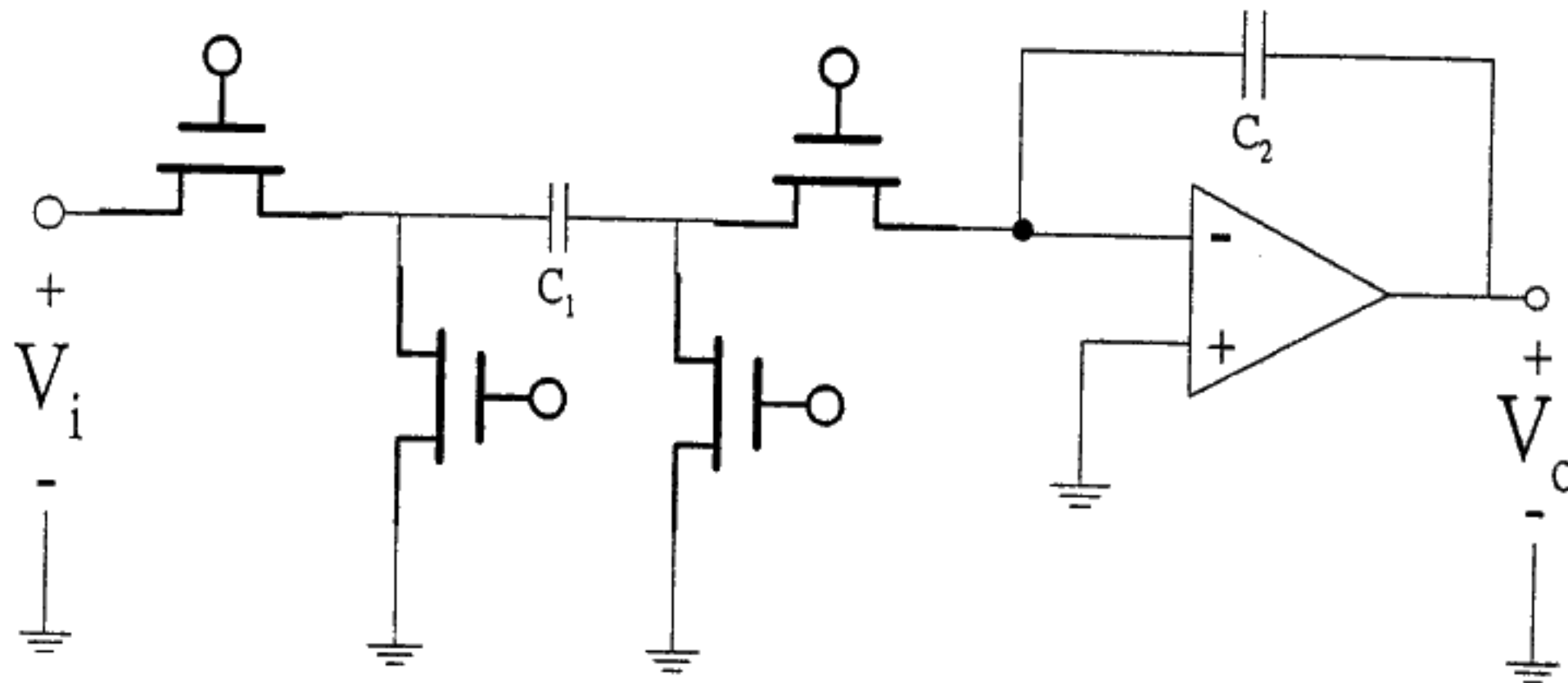


Fig. 5(a)

- Let $R_{eq} = f(T_c, C_1, C_2)$, derive the function f for inverting SC (you need to show the current path during the operation of each phase clock) (5%)
- Plot the switch-capacitor counterpart of Fig. 5(b). In each replacement of R_i by its SC equivalent, give the reasoning why you choose an inverting SC or a non-inverting SC. (8%)


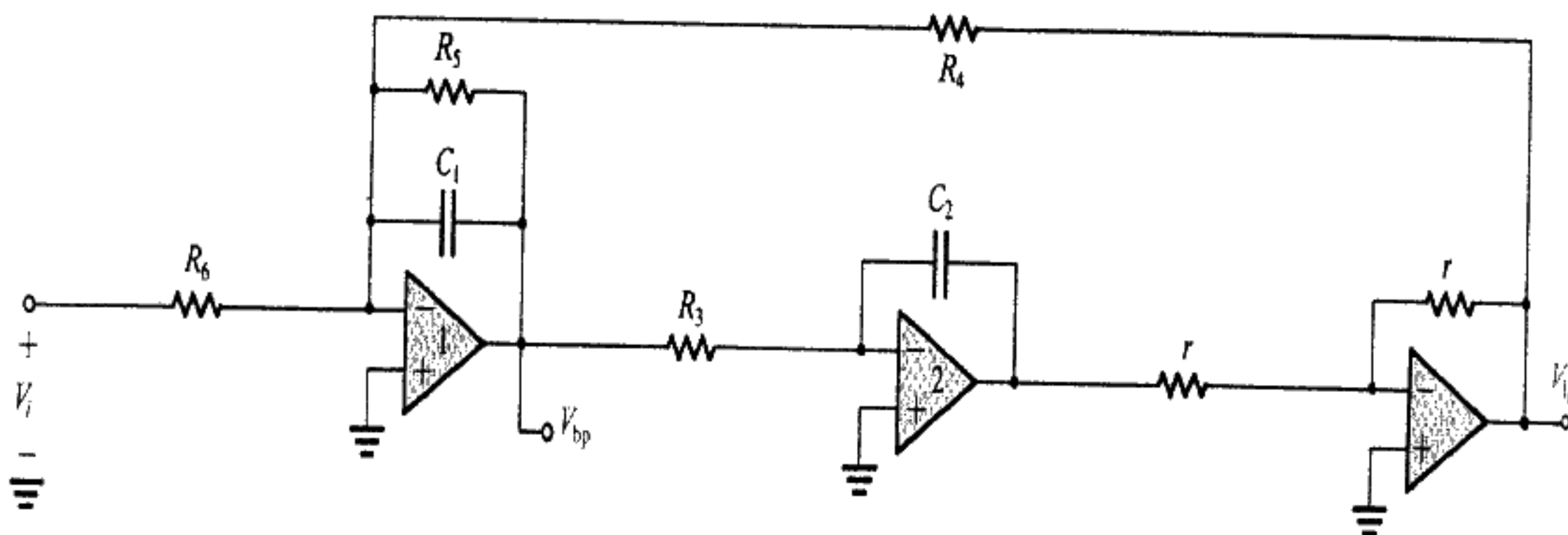


Fig. 5(b)

6. (20pts)

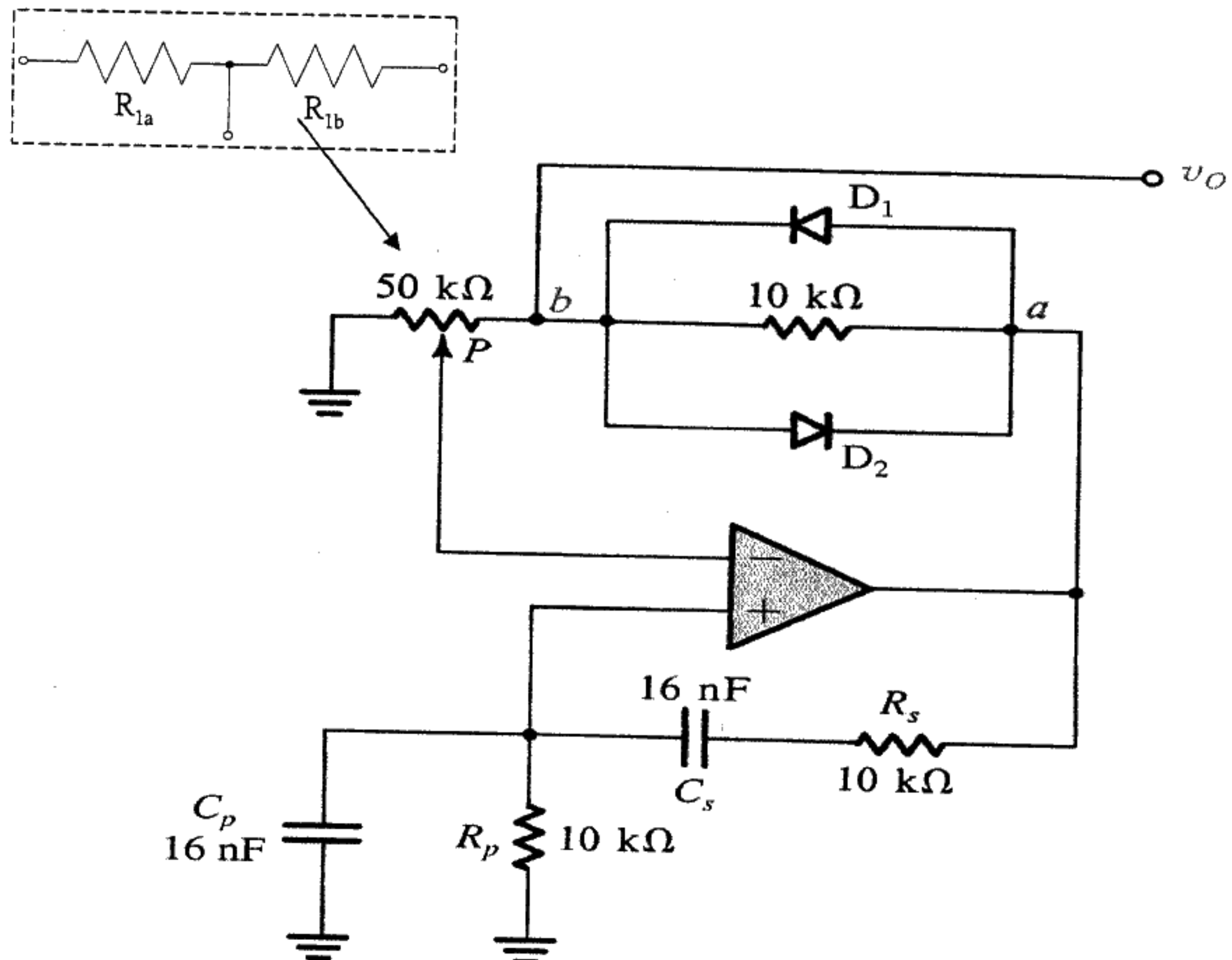

In text, p. 977, L.9 states "To ensure that oscillation will start, one designs the circuit such that $A\beta$ is slightly greater than unit. This corresponds to designing the circuit so that the poles are in the right half of the s -plane. Thus, as the power supply is turned on, oscillation will grow in amplitude."

In text, p. 982, L. 9 also states "The output amplitude can be varied by adjusting the potentiometer P."

We wish to examine the above statement by solving the following questions.

- when $R_{1b} = 32 \text{ k}\Omega$, $R_{1a} = 18 \text{ k}\Omega$, what is the $A\beta$ value and the corresponding pole positions of this circuit?(6pts)
- Derive the relationship of V_a versus V_o in terms of (R_{1a}, R_{1b}) , you may assume the diode turn-on voltage is 0.5V. (6pts)
- When the power supply is turned on, we can assume there is a wide spectrum of white noise whose amplitude is estimated to be $1 \text{ }\mu\text{V}$. Following (a), (b), evaluate the time of elapse before this circuit to reach its steady state output voltage V_o at the sustained oscillations, and what will be the oscillation frequency.(8pts)

7. (30pts) Given that $R_1 = 10\text{k}\Omega$, $R_2 = 90\text{k}\Omega$, $C_1 = 0.1\mu\text{F}$, $V_D = 0.7\text{V}$, and $L_+ = -L_- = 12\text{V}$, analyze the bistable and monostable circuits.
- For the bistable circuit as shown in Fig. 7-1, calculate V_{TH} , V_{TL} and plot the transfer characteristic of the circuit. (5pts)
 - If the bistable circuit is used to construct the monostable circuit as shown in Fig. 7-2, what is the minimum negative step needed for the triggering signal? (5pts)
 - Find the value of R_3 that will result in a $100\text{-}\mu\text{s}$ output pulse. (10pts)
 - What is the minimum time interval required between two consecutive triggering signals? (10pts)
- ($R_1 = 10\text{k}\Omega$, $R_2 = 90\text{k}\Omega$, $C_1 = 0.1\mu\text{F}$, $V_D = 0.7\text{V}$, and $L_+ = -L_- = 12\text{V}$)

 


Fig. 7-1

 


Fig. 7-2

8. (20pts) The node in the 555 timer at which the voltage is V_{TH} (that is, the inverting input terminal of comparator 1) is usually connected to an external terminal. This allows the user to change V_{TH} externally (that is, it no longer remains $\frac{2}{3}V_{CC}$). Note, however, that whatever the value of V_{TH} becomes, V_{TL} always remains $\frac{1}{2}V_{TH}$.

- For the astable circuit of Fig. 2, rederive the expressions for T_H and T_L , expressing them in terms of V_{TH} and V_{TL} . (6pts)
- For the case $C = 1\text{nF}$, $R_A = 7.2\text{k}\Omega$, $R_B = 3.6\text{k}\Omega$, and $V_{CC} = 5\text{V}$, find the frequency of oscillation and the duty cycle of the resulting square wave when no external voltage is applied to the terminal V_{TH} . (6pts)
- For the design in (b), let a sine-wave signal of a much lower frequency than that found in (b) and of 1-V peak amplitude be capacitively coupled to the circuit node V_{TH} . This signal will cause V_{TH} to change around its quiescent value of $\frac{2}{3}V_{CC}$, and thus T_H will change correspondingly – a modulation process. Find T_H , and find the frequency of oscillation and the duty cycle at the two extreme values of V_{TH} . (8pts)

