

## Microelectronic Circuits I (Quiz 2)

date: 2009/12/18 (Fri)

time: 14:20~15:10

1. (50%) Consider an n-channel MOSFET with  $t_{ox}=20\text{nm}$ ,  $\mu_n=650\text{cm}^2/\text{V}\cdot\text{s}$ ,  $V_t=0.8\text{V}$ , and  $W/L=10$ . Find the drain current in the following cases:

- (a)  $v_{GS}=5\text{V}$  and  $v_{DS}=1\text{V}$      $4.18\text{mA}$
- (b)  $v_{GS}=2\text{V}$  and  $v_{DS}=1.2\text{V}$      $0.87\text{mA}$
- (c)  $v_{GS}=5\text{V}$  and  $v_{DS}=0.2\text{V}$      $0.919\text{mA}$
- (d)  $v_{GS}=v_{DS}=5\text{V}$      $9.887\text{mA}$

2. (50%) Figure below shows a discrete-circuit CS amplifier employing the classical biasing scheme studied in Section 4.5. The input signal  $v_{sig}$  is coupled to the gate through a very large capacitor (shown as infinite). The transistor source is connected to ground at signal frequencies via a very large capacitor (shown as infinite). The output voltage signal that develops at the drain is coupled to a load resistance via a very large capacitor (shown as infinite).

- (a) If the transistor has  $V_t=1\text{V}$ , and  $k_n'W/L=2\text{mA/V}^2$ , verify that the bias circuit establishes  $V_{GS}=2\text{V}$ ,  $I_D=1\text{mA}$ , and  $V_D=+7.5\text{V}$ . That is, assume these values, and verify that they are consistent with the values of the circuit components and the device parameters..

- (b) Find  $g_m$  and  $r_o$  if  $V_A=100\text{V}$ .     $2\text{mA/V}$ ,  $100\text{k}\Omega$

- (c) Draw a complete small-signal equivalent circuit for the amplifier assuming all capacitors behave as short circuit at signal frequencies.

- (d) Find  $R_{in}$ ,  $v_{gs}/v_{sig}$ ,  $v_o/v_{gs}$ , and  $v_o/v_{sig}$ .

