

2012 Fall Electromagnetics II – Quiz I

Date: 22/10/2012

Problem 1

In the system shown in Fig. 1, assume that V_g is a constant voltage source of 80 V and the switch S is closed at $t = 0$. Find and sketch: (a) the line voltage versus z for $t = 0.2 \mu\text{s}$; and (b) the line current versus z for $t = 0.4 \mu\text{s}$; (c) the line voltage versus t for $z = 30 \text{ m}$; and (d) the line current versus t for $z = -40 \text{ m}$. $R_S = 60 \Omega$.



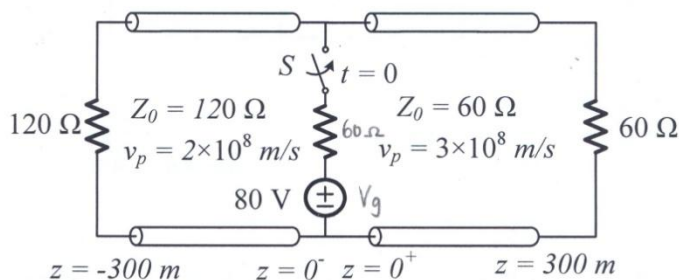


Fig. 1

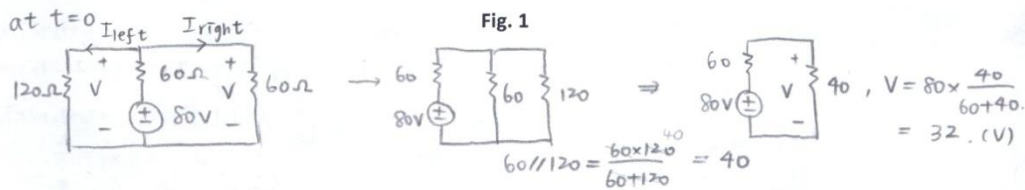


$$T_{d, \text{left}} = \frac{300}{2 \times 10^8} = \frac{3}{2} \times 10^{-6} = 1.5 \mu\text{s}. \quad T_{d, \text{right}} = \frac{300}{3 \times 10^8} = 1 \mu\text{s}.$$

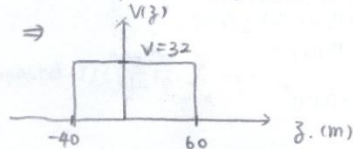(a) $t = 0.2 \mu\text{s} \rightarrow$ left wave 走 $300 \times \frac{0.2 \mu\text{s}}{1.5 \mu\text{s}} = 40 \text{ m}$, right wave 走 $300 \times \frac{0.2 \mu\text{s}}{1 \mu\text{s}} = 60 \text{ m}$



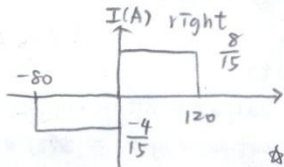(b) $t = 0.4 \mu\text{s} \rightarrow$ left wave 走 $300 \times \frac{0.4 \mu\text{s}}{1.5 \mu\text{s}} = 80 \text{ m}$

right wave 走 $300 \times \frac{0.4 \mu\text{s}}{1 \mu\text{s}} = 120 \text{ m}$




$$I_{\text{left}} = \frac{V}{120 \Omega} = \frac{4}{15} \text{ (A)}$$

$$I_{\text{right}} = \frac{V}{60 \Omega} = \frac{8}{15} \text{ A}$$

★ 定义向+z方向的电流为+

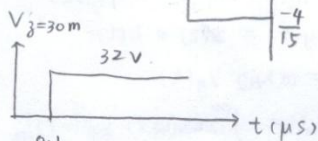
(c) $z = 30 \text{ m}$.

$$\frac{30}{3 \times 10^8} = 10^{-7} = 0.1 \mu\text{s}$$



(d) $z = -40$

$$\frac{40}{2 \times 10^8} = 0.2 \mu\text{s}$$

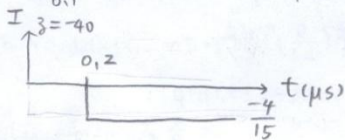

Problem 2

In the system shown in Fig. 2: (a) find the output voltage V_o across the 150Ω resistor for $V_g(t) = \delta(t)$; and (b) find ~~and sketch~~ the amplitude of $V_o(t)$ versus ω for $V_g(t) = \cos \omega t$.

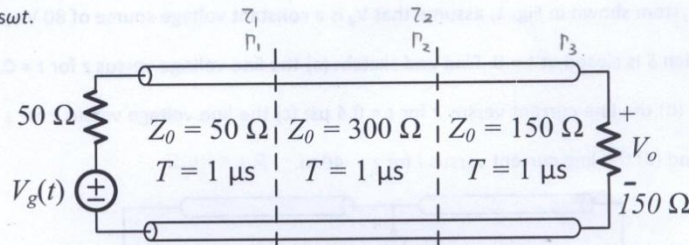


Fig. 2

(a) $V_g(t) = \delta(t)$

$$\Gamma_1 = \frac{300-50}{300+50} = \frac{250}{350} = \frac{5}{7}, \quad \Gamma_2 = \frac{150-300}{150+300} = \frac{-150}{450} = -\frac{1}{3}$$

$$\Gamma_3 = \frac{150-150}{150+150} = 0.$$

$$\rightarrow \tau_1 = 1 + \Gamma_1 = \frac{12}{7}, \quad \tau_2 = 1 + \Gamma_2 = 1 - \frac{1}{3} = \frac{2}{3}, \quad \tau_3 = 1 + \Gamma_3 = 1.$$

$$V^+ = V_g \times \frac{50}{50+50} = \frac{1}{2} V_g. \Rightarrow V_g = A \delta(t - (\tau_1 + \tau_2 + \tau_3)) + (-\Gamma_1 \Gamma_2) A \delta(t - (\tau_1 + \tau_2 + \tau_3 + 2\tau_2)) + A (\Gamma_1 \Gamma_2)^2 \delta(t - (\tau_1 + \tau_2 + \tau_3 + 2 \times 2\tau_2))$$

$$= \sum_{n=0}^{\infty} A (\Gamma_1 \Gamma_2)^n \delta(t - (\tau_1 + \tau_2 + \tau_3 + 2n\tau_2))$$

$$\left\{ \begin{array}{l} A = \frac{1}{2} \times \frac{12}{7} \times \frac{2}{3} \times 1 = \frac{4}{7} \\ -\Gamma_1 \Gamma_2 = -\frac{5}{7} \times -\frac{1}{3} = \frac{5}{21} \\ \tau_1 + \tau_2 + \tau_3 = 3 \mu s \\ 2\tau_2 = 2 \mu s \end{array} \right.$$

$$\Downarrow$$

$$V_g = \sum_{n=0}^{\infty} \frac{4}{7} \left(\frac{5}{21}\right)^n \delta(t - (3+2n)\mu s)$$

(b) $V_g(t) = \cos(\omega t)$

If input = $\delta(t) \rightarrow$ output = $h(t)$ = impulse response.

then input = $x(t) \rightarrow$ output = $y(t) = x(t) * h(t)$

Now $x(t) = \cos(\omega t)$, $h(t) = (a) \& (b) V_g(t)$

$$\Rightarrow y(t) = \cos \omega t * V_g(t)|_{(a)} = \int_{-\infty}^{\infty} \cos(\omega \tau) V_g(t-\tau)|_{(a)} d\tau.$$

$$= \int_{-\infty}^{\infty} \cos(\omega \tau) \sum_{n=0}^{\infty} \frac{4}{7} \left(\frac{5}{21}\right)^n \delta(t-\tau - (3+2n)\mu s) d\tau.$$

$$= \sum_{n=0}^{\infty} \frac{4}{7} \left(\frac{5}{21}\right)^n \cos[\omega(t - (3+2n)\mu s)]$$

$$\Rightarrow \text{phasor } Y(\omega) = \sum_{n=0}^{\infty} \frac{4}{7} \left(\frac{5}{21}\right)^n e^{-j\omega(3+2n)\mu s} = \frac{4}{7} e^{-j3\omega\mu s} \sum_{n=0}^{\infty} \left(\frac{5}{21}\right)^n e^{-j2\omega\mu s n}$$

$$\frac{\frac{4}{7} e^{-j3\omega\mu s}}{1 - \frac{5}{21} e^{-j2\omega\mu s}}$$

$$\frac{4}{7} e^{-j3\omega\mu s} \frac{1}{1 - \frac{5}{21} e^{-j2\omega\mu s}}$$

小考

$$3. (a) \frac{V_0}{Z_0} + V^- = L \frac{d(\frac{V_0}{Z_0} - \frac{V^-}{Z_0})}{dt} + (\frac{V_0}{Z_0} - \frac{V^-}{Z_0}) Z_0$$

$$\frac{V_0}{Z_0} + V^- = -\frac{L}{Z_0} \frac{dV^-}{dt} + \frac{V_0}{Z_0} - V^-$$

$$\underline{\underline{V^- + \frac{L}{Z_0} \frac{dV^-}{dt} = 0}}$$


(b) at $t=T$ L open $[I]_{t=T} = 0$

$$\frac{V_0}{Z_0} - \frac{V^-}{Z_0} = 0 \quad \underline{\underline{[V^-]_{t=T} = \frac{V_0}{Z_0}}}$$

$$(c) V^- = A \cdot e^{-\frac{Z_0}{L}(t-T)}$$


$$\& [V^-]_{t=T} = \frac{V_0}{Z_0} \Rightarrow \underline{\underline{V^- = \frac{V_0}{Z_0} e^{-\frac{Z_0}{L}(t-T)} \quad t > T}}$$

4

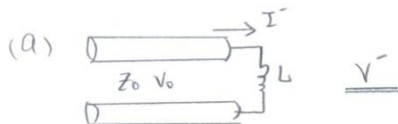


$$(b) V_0 + V^- = L \cdot \frac{d(I^-)}{dt} = L \frac{d(-\frac{V^-}{Z_0})}{dt} = -\frac{L}{Z_0} \frac{dV^-}{dt}$$
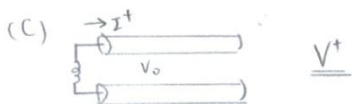
$$\underline{\underline{\frac{L}{Z_0} \frac{dV^-}{dt} + V^- = -V_0}}$$







$$(d) V_0 + V^+ = L \cdot \frac{d(I^+)}{dt} = -\frac{L}{Z_0} \frac{dV^+}{dt} \quad \therefore \underline{\underline{\frac{L}{Z_0} \frac{dV^+}{dt} + V^+ = -V_0}}$$

Problem 5.

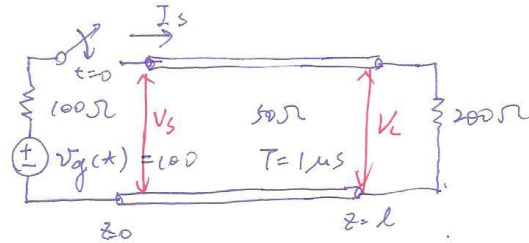

Characteristic at $z=0$ is $V_s = 100 - 100 I_s$

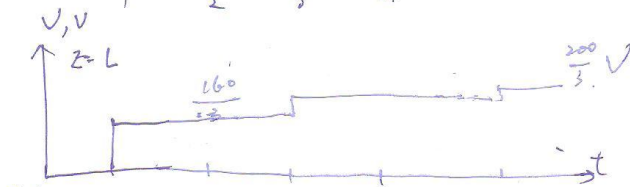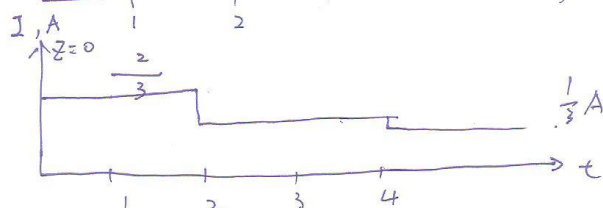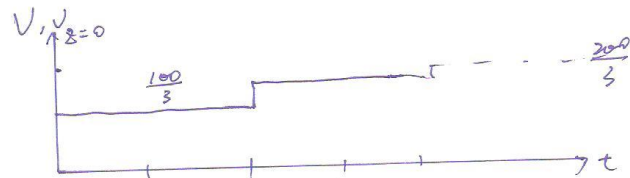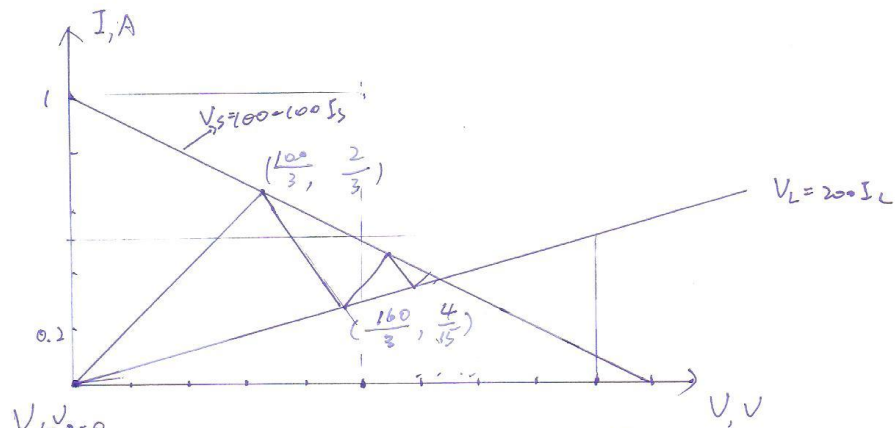Characteristic at $z=l$ is $V_L = 200 I_L$



$$V_{SS} = \frac{200}{3} \text{ V}$$

$$I_{SS} = \frac{1}{3} \text{ A}$$

Problem 6.

(a)

$$\Delta I_{c2}(\xi, t) = C_m \Delta \xi \frac{\partial V_1(\xi, t)}{\partial t}$$

$$\Delta V_{c2}(\xi, t) = L_m \Delta \xi \frac{\partial I_1(\xi, t)}{\partial t}$$

$$\Delta V_2^+ = \frac{1}{2} Z_0 \Delta I_{c2} - \frac{1}{2} \Delta V_{c2}$$

$$\Delta V_2^- = \frac{1}{2} Z_0 \Delta I_{c2} + \frac{1}{2} \Delta V_{c2}$$

$$\begin{aligned} \Delta V_2^+(\xi, t) &= \left[\frac{1}{2} C_m Z_0 \frac{\partial V_1(\xi, t)}{\partial t} - \frac{1}{2} L_m \frac{\partial I_1(\xi, t)}{\partial t} \right] \Delta \xi \\ &= \frac{1}{2} \left(C_m Z_0 - \frac{L_m}{Z_0} \right) \frac{\partial V_1(\xi, t)}{\partial t} \Delta \xi \end{aligned}$$

$$\Delta V_2^-(\xi, t) = \frac{1}{2} \left(C_m Z_0 + \frac{L_m}{Z_0} \right) \frac{\partial V_1(\xi, t)}{\partial t} \Delta \xi$$


$$\begin{aligned} V_2^+(z, t) &= \int_0^z \frac{1}{2} \left(C_m Z_0 - \frac{L_m}{Z_0} \right) \frac{\partial}{\partial t} \left[V_1 \left(t - \frac{z}{v_p} - \frac{z-\xi}{v_p} \right) \right] d\xi \\ &= \frac{1}{2} \left(C_m Z_0 - \frac{L_m}{Z_0} \right) \int_0^z \frac{\partial V_1(t - z/v_p)}{\partial t} d\xi \end{aligned}$$

$$\therefore V_2^+(z, t) = z k_f V_1'(t - z/v_p)$$

$$\text{for } k_f = \frac{1}{2} \left(C_m Z_0 - \frac{L_m}{Z_0} \right)$$

(b)

Line 1

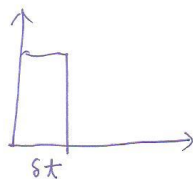

Line 2

